

# Amplifiers in systems

---

- **Amplification**

- single gain stage rarely sufficient

- add gain to avoid external noise eg to transfer signals from detector

- practical designs depend on detailed requirements

- constraints on power, space,... cost in large systems

- e.g. ICs use limited supply voltage which may constrain dynamic range

- **Noise will be an important issue in many situations**

- most noise originates at input as first stage of amplifier dominates

- often refer to Preamplifier = input amplifier

- may be closest to sensor, subsequently transfer signal further away

- **In principle, several possible choices**

- V sensitive

- I sensitive

- Q sensitive

# Voltage sensitive amplifier

- As we have seen many sensors produce current signals but some examples produce voltages - thermistor, thermocouple,...  
op-amp voltage amplifier ideal for these  
especially slowly varying signals - few kHz or less
- For sensors with current signals voltage amplifier usually used for secondary stages of amplification

•Signal  $V_{out} = Q_{sig}/C_{tot}$

$C_{tot}$  = total input capacitance

$C_{tot}$  will also include contributions from wiring and amplifier

$V_{out}$  depends on  $C_{tot}$


not desirable if  $C_{det}$  is likely to vary

eg with time, between similar sensors, or depending on conditions

- Noise to be discussed more later

contribution from amplifier, and possibly sensor

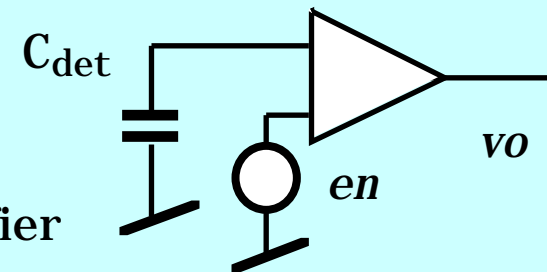$S/N = Q_{sig}/(C_{tot} \cdot v_{noise})$  can it be optimised?



# Current sensitive amplifier

- Common configuration, eg for photodiode signals

$$V_{out} = -AV_{in}$$

$$V_{in} - V_{out} = i_{in}R_f$$

$$V_{out} = -[A/(A+1)] \cdot i_{in}R_f \quad -i_{in}R_f$$

- Input impedance

$$V_{in} = i_{in}R_f/(A+1) \quad Z_{in} = R_f/(A+1)$$

- Effect of C &  $R_{in}$  - consider in frequency domain

$$v_0 = i(1/j \quad C \parallel R_{in})$$

$$= i( \quad )R/(1 + j \quad )$$

input signal convoluted with falling exponential




increasing  $R_f$  to gain sensitivity will increase

fast pulses will follow input with some broadening

- Noise

will later find that feedback resistor is a noise source

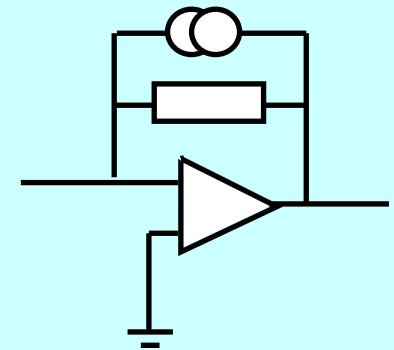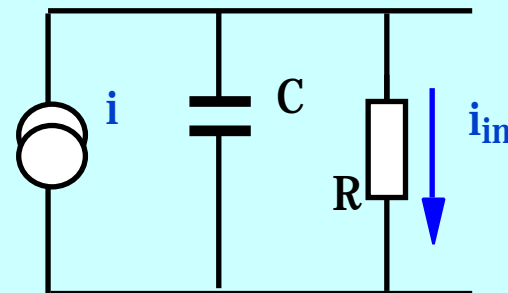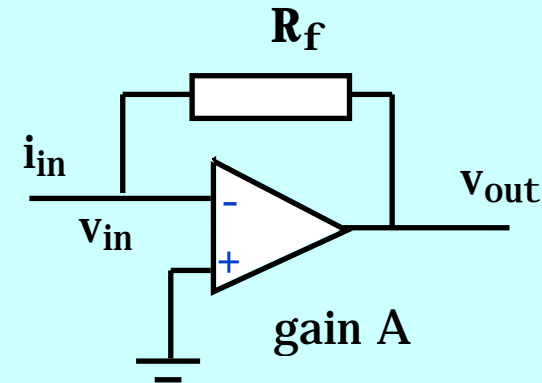contributes current fluctuations at input  $\sim 1/R_f$



# Charge sensitive amplifier

- Ideally, simple integrator with  $C_f$   
but need means to discharge capacitor - large  $R_f$
- Assume amplifier has  $Z_{in}$  very high (usual case)

$$V_{out} = -AV_{in}$$

$$V_{out} - V_{in} = i_{in}/j \omega C_f$$

$$V_{out} = -[A/(A+1)] \cdot i_{in}/j \omega C_f \approx -i_{in}/j \omega C_f$$

$$\Rightarrow -Q/C_f$$

- Input impedance

$$v_{in} = i_{in}/(A+1)j \omega C_f \quad C = (A+1)C_f \text{ at low } f$$

so amplifier looks like large capacitor to signal source




low impedance but some charge lost

$$Q_A = Q/[1 + C_{tot}/(A+1)C_f]$$

e.g.  $A = 10^3 \quad C_f = 1\text{pF}$

$C_{tot} = 10\text{pF} \quad Q_A/Q = 0.99$

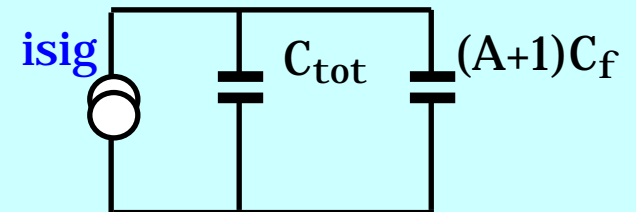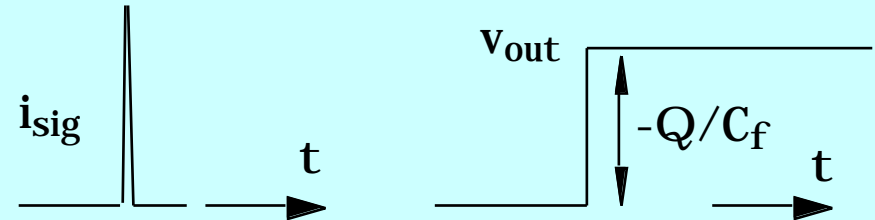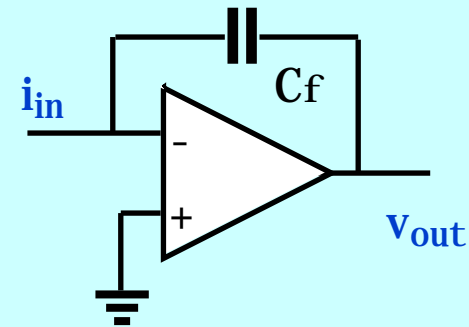$C_{tot} = 100\text{pF} \quad Q_A/Q = 0.90$



# Feedback resistance



- Must have means to discharge capacitor so add  $R_f$

$$Z_f = R_f || 1/j \omega C_f$$

$$V_{out} = -[A/(A+1)] \cdot i_{in} Z_f$$

$$= i_{in} R_f / (1 + j \omega R_f C_f) \quad \tau = R_f C_f$$

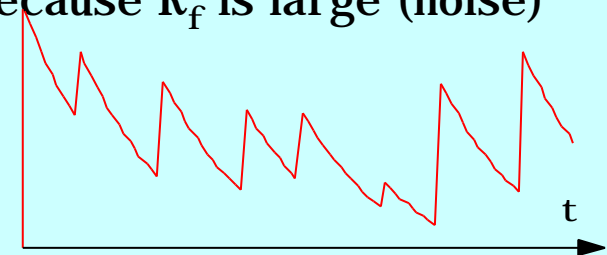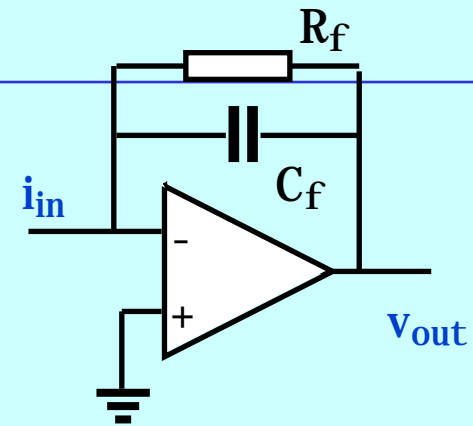step replaced by decay with  $\sim \exp(-t/R_f C_f)$  is long because  $R_f$  is large (noise)  
 easiest way to limit pulse pileup - differentiate  
 ie add high pass filter



- Pole-zero cancellation

exponential decay + differentiation => unwanted baseline undershoot

introduce canceling network

$$v_0 = 1/(1 + j \omega \tau_f)$$


$$v_1 = 1/(1 + j \omega \tau_f)(1 + j \omega \tau_1)$$

$$\tau_1 = RC < \tau_f$$

add resistor  $R_p$  so  $R_p C = \tau_f$

then

$$v_1' = 1/(1 + j \omega \tau_3) \quad \text{with} \quad \tau_3 = (R || R_p)C < \tau_f$$

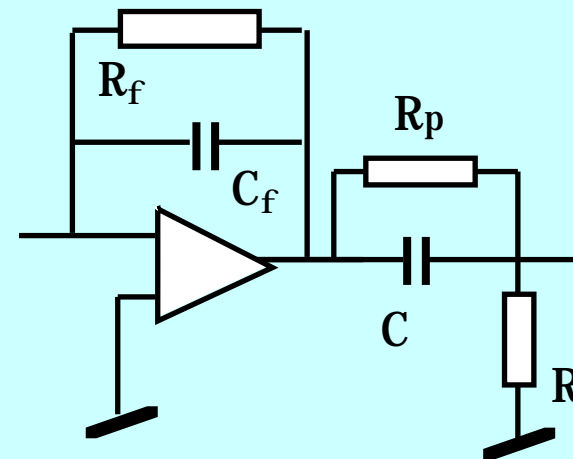

# Effect of finite bandwidth

## • Realistic input stage of amplifier



$$v_{out} = i_d(R_L || C_L) \quad i_d = g_m v_{in}$$

$$A = g_m R_L \quad \text{low } f$$

$$A = g_m / j \omega C_L \quad \text{high } f$$

(NB phase change)

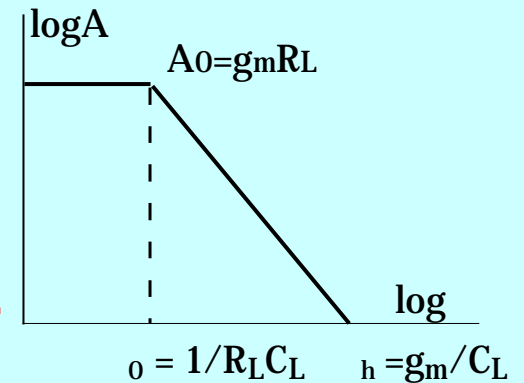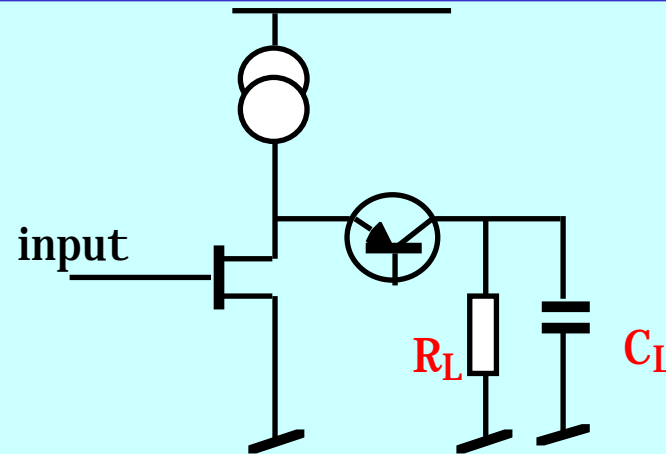
$$Z_{in} = 1/A \quad C_f = C_L / g_m \quad C_f \text{ resistive!}$$



Irrespective of detailed design

$$A = A_0 \frac{h}{j\omega} \quad h = \text{gain-bandwidth product}$$
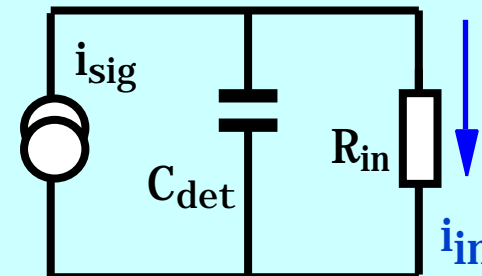
$$= 1/A_0 \frac{C_f}{h} \quad \omega = 1/C_f$$




## • Effect of $R_{in}$

signal current shared between  $R_{in}$  &  $C_{det}$

$$v_{out} = i_{in} Z_f \quad i/[j\omega C_f(1 + j\omega \text{ rise})]$$

$$\sim 1 - \exp(-t/\tau)$$

high frequencies in leading edge

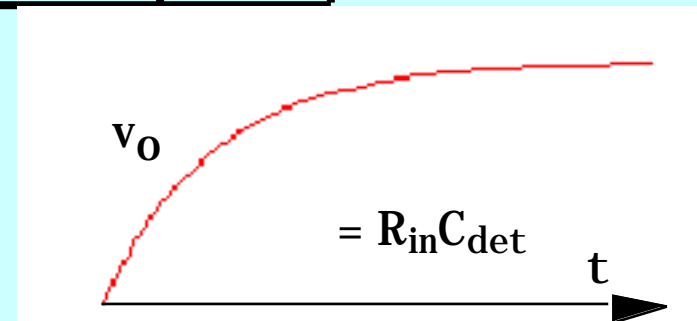

leading edge of output pulse

# Output impedance

- Usual method of varying  $v_{out}$  and finding  $i_{out}$  - generally messy algebra
- Current sensitive amplifier, open loop gain = A

$$v_{out} = i_2(R_2 + R_{in})$$

$$v_{in} = i_2 R_{in}$$


$$v_o = -A v_{in} = -A i_2 R_{in}$$

$$i_o = (v_{out} - v_o) / R_o = (v_{out} - A i_2 R_{in}) / R_o$$

$$Z_{out} = v_{out} / i_{out} = R_o (R_2 + R_{in}) / [R_o + R_2 + R_{in}(A+1)]$$

$$R_o / (A+1)$$

since  $R_{in} \gg R_2, R_o$

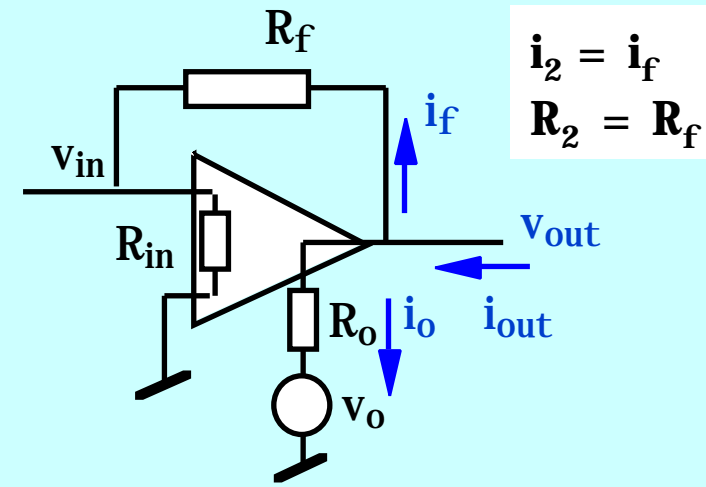

$R_o$  = open loop output impedance

- In general

$$Z_{out} = R_o / (1+Ab) \quad \text{if voltage is sampled at output} \quad b = \text{feedback fraction}$$

$$Z_{out} = R_o (1+Ab) \quad \text{if current is sampled at output}$$

# Comparators

- Frequently need to compare a signal with a reference

eg temperature control, light detection, DVM,...

basis of analogue to digital conversion -> 1 bit

- Comparator

high gain differential amplifier,

difference between inputs sends output to saturation (+ or -)

could be op-amp - without feedback - or purpose designed IC

Sometimes ICs designed with open-collector output so add pull-up R to supply

also available with latch (memory) function

- NB


no negative feedback so  $v_- = v_+$

saturation voltages may not reach supply voltages - check specs

speed of transition

- Potential problem

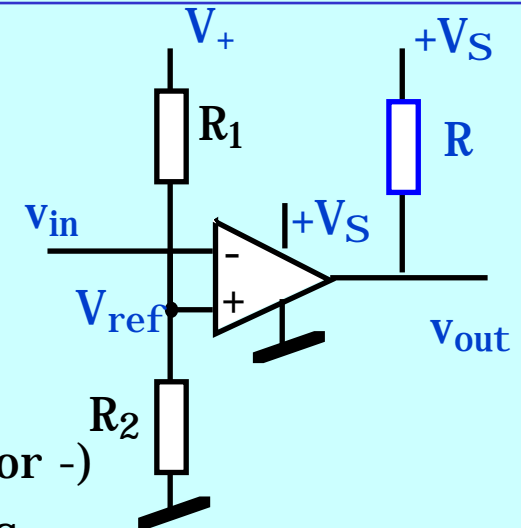multiple transitions as signal changes near threshold





# Hysteresis

- Add positive feedback (Schmitt trigger)

$V_{ref}$  changes as  $v_{out} \rightarrow +V_S$

ie threshold falls once transition is made

preventing immediate fall

positive feedback speeds transition

$$v_{out} = A(V_{ref} - v_-)$$

$$V_{ref} > v_- \Rightarrow v_{out} = V_S \quad V_{ref} = V_{high}$$

$$V_{ref} < v_- \Rightarrow v_{out} = 0V \quad V_{ref} = V_{low}$$

here, signal  $\Rightarrow$  logical "1":  $v_{out} = 0V$

- Output depends on history



eg  $V_+ = 10V$ ,  $V_S = +5V$ ,  $0V$

$$R_1 = 10k \quad , \quad R_2 = 10k \quad , \quad R_3 = 100k$$


$$V_{out} = 0V, \quad V_{ref} = 4.76V$$

$$V_{out} = 5V, \quad V_{ref} = 5V$$

$$\text{hysteresis} = V_{ref} = 0.24V$$

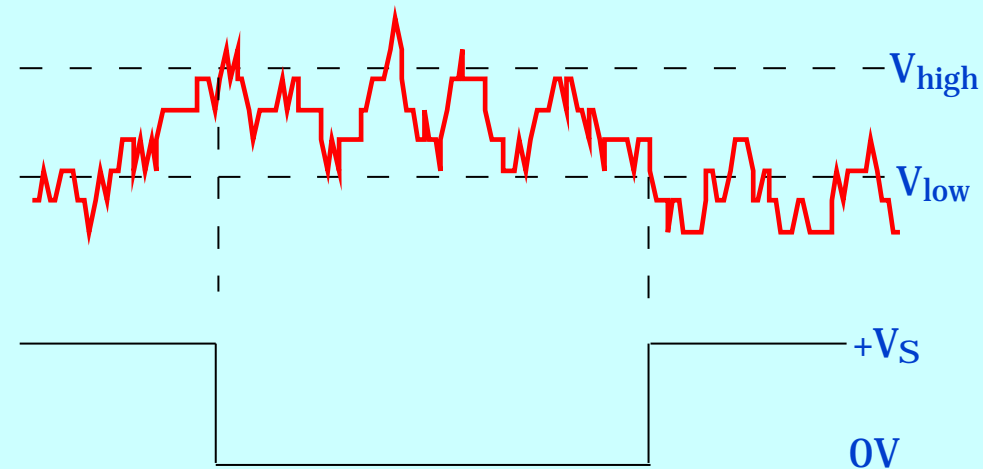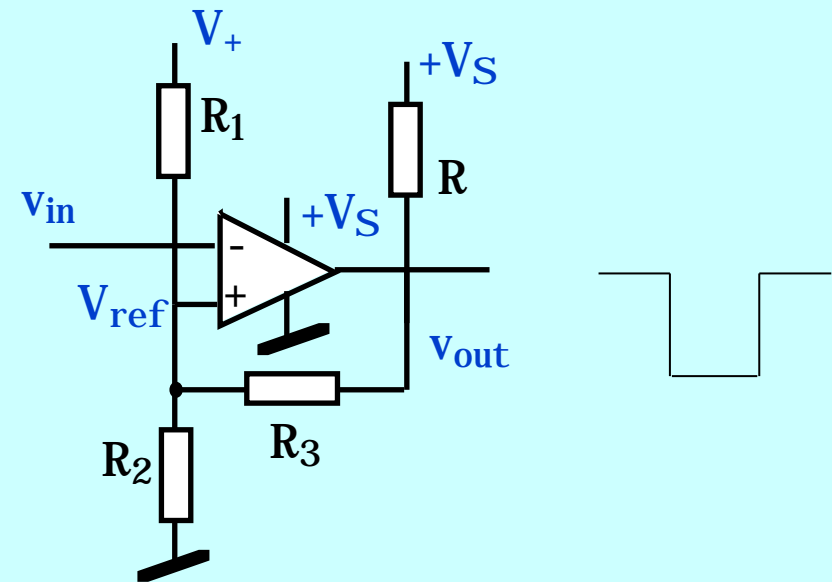

# Example - alarm

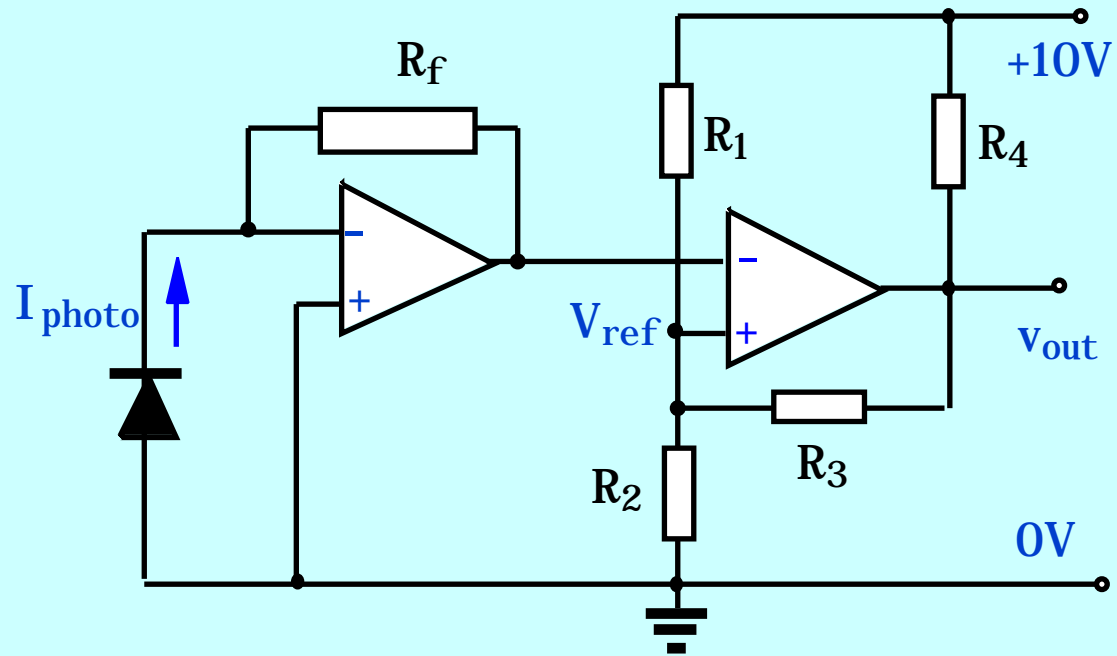

# Oscillators

- **Basic building block of many systems**

clock or timer, signal generators, function generators, ...  
can exploit positive feedback

- **Relaxation oscillator**

charge capacitor  $C$  through  $R \sim \exp(-t/RC)$

$v_-$  crosses threshold at  $V_{ref}$ ,  $V_{out} \Rightarrow \pm V_S$

$V_{ref}$  changes sign

etc, etc...


square wave output:  $[\pm V_S]$

Period  $T = 2.2RC$

- **many more types of oscillator design available**

IC classic = 555 (many versions)

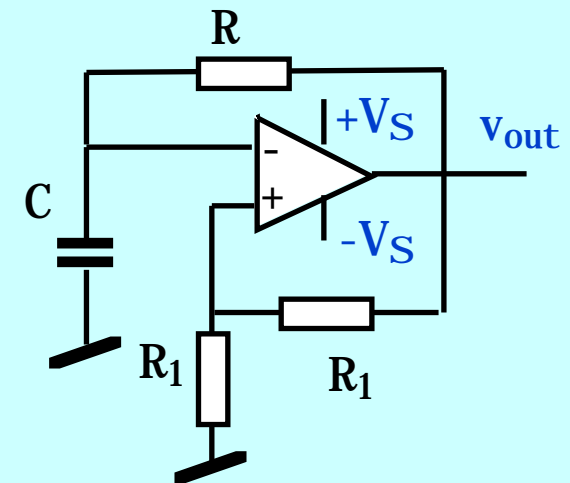external components set period and duty cycle



# Wien bridge oscillator

- **Sine wave oscillators also often required**

favourite circuit for audio test applications:  
low harmonic distortion at  $f \sim$  few kHz


Gain = real at  $\omega_0 = 1/RC$

so positive feedback

Lamp provides temperature dependent resistor  
so negative feedback controls amplitude


What values to choose for lamp resistance and  $r$ ?

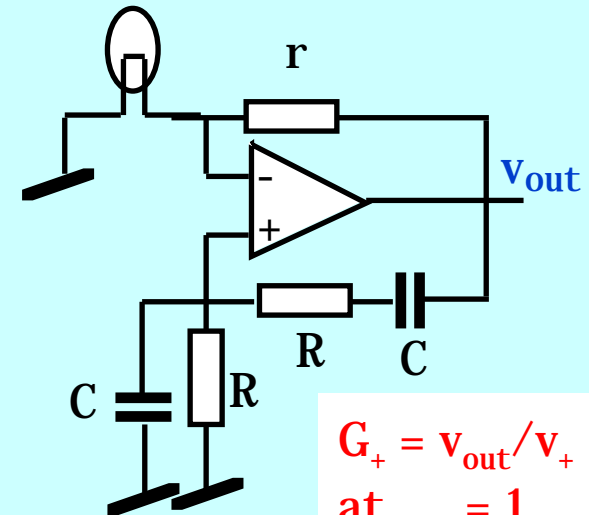What determines amount of harmonic distortion?



$$G_+ = v_{out}/v_+ = 3$$

at  $\omega = 1/RC$

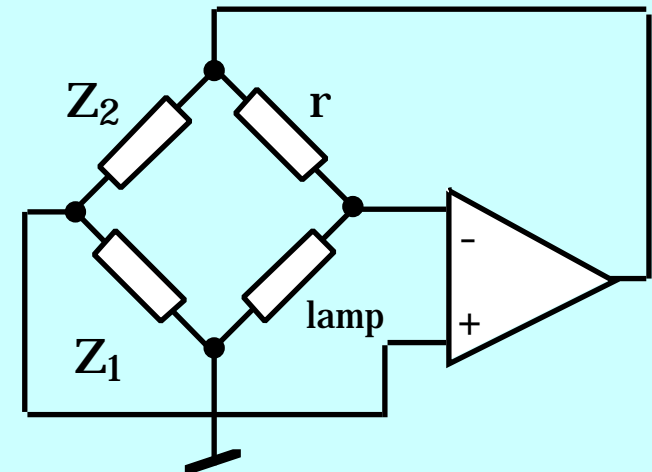

# Temperature controller

- A frequent requirement - similar to many other control applications

eg cryostat with stable temperature maintained by resistive heater, or oven, ...

- On-Off control

$$T < T_0$$

set heater to maximum power


add hysteresis ( $T_{01}$ ,  $T_{02}$ )

to prevent noise from switching too rapidly

ok for central heating or

domestic oven but not good

for stable measurements - try to improve

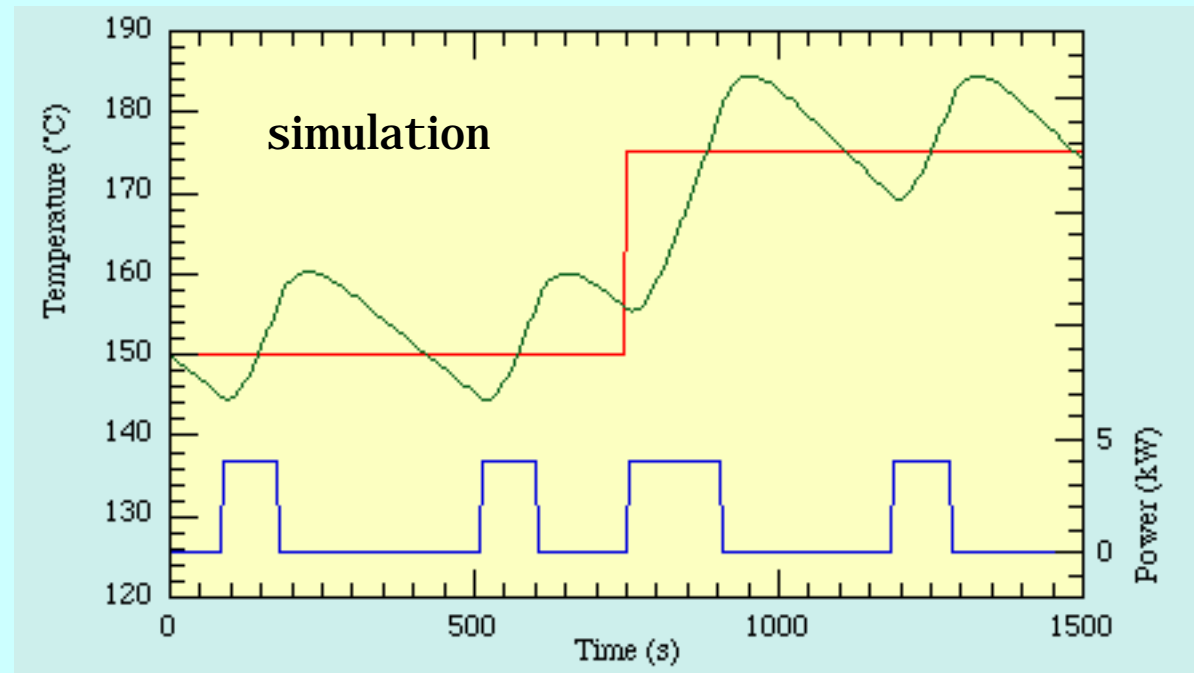

# P & PD Temperature control

- Set heater power, proportional to temperature difference (P)



$$W = P(T_{\text{meas}} - T_0)$$

T still oscillates and  
undershoots desired value  
unstable if heat too fast

- Add control term proportional to rate of change (PD)

$$W = P[(T_{\text{meas}} - T_0) + Dd(T_{\text{meas}} - T_0)/dt]$$

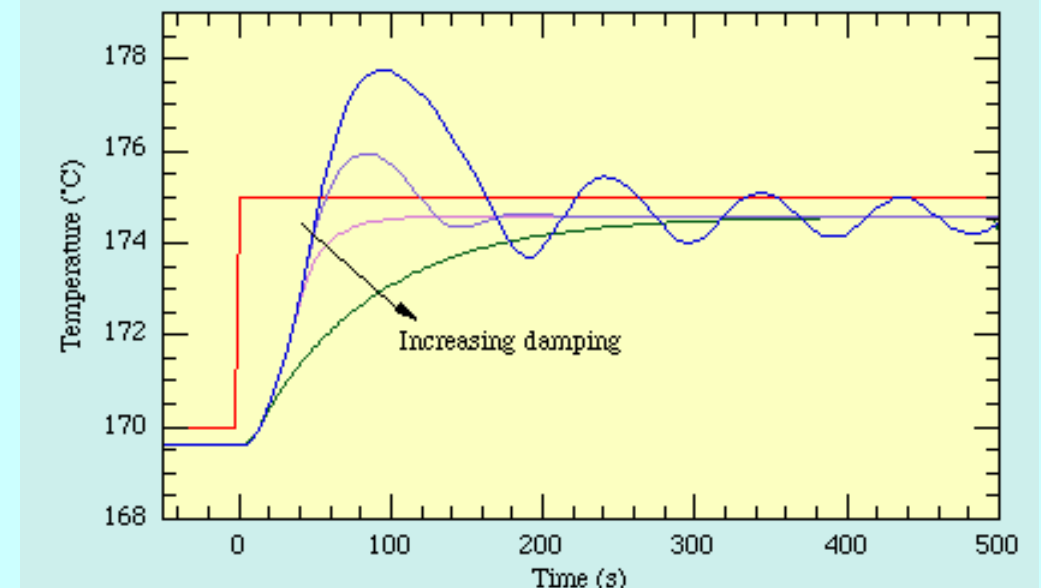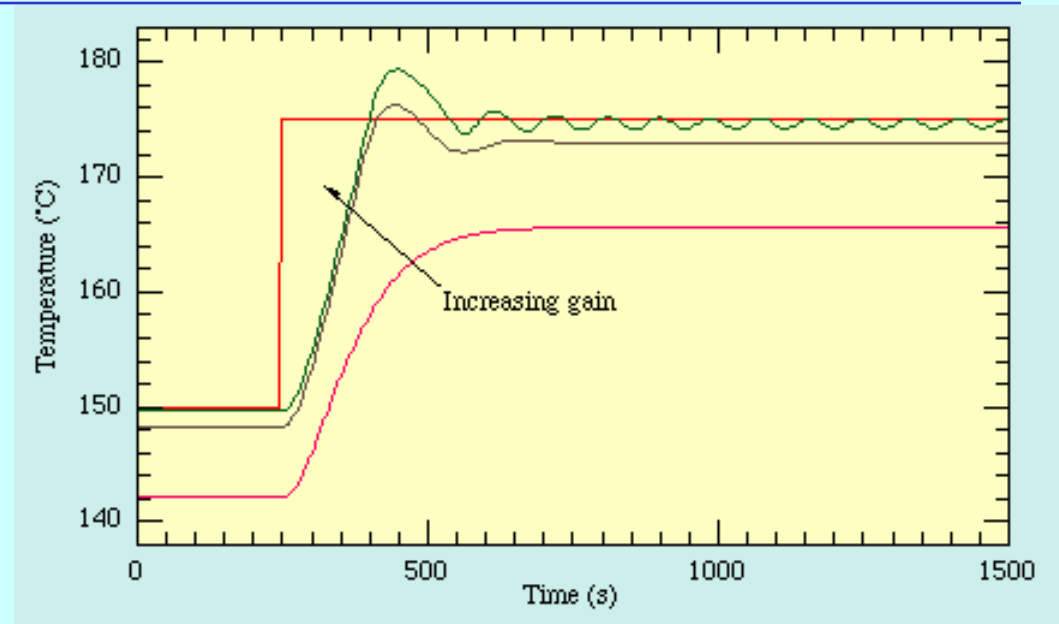D too large: overshoot & ringing  
D too small: slow response



# PID Temperature control

- PD can eliminate ringing & overshoot but undershoot error remains


add integral term

- PID control

$$W = P[(T_{\text{meas}} - T_0) + Dd(T_{\text{meas}} - T_0)/dt + I \int (T_{\text{meas}} - T_0) dt]$$

good results but  
need to choose coefficients  
P, D, I empirically to ensure  
stability

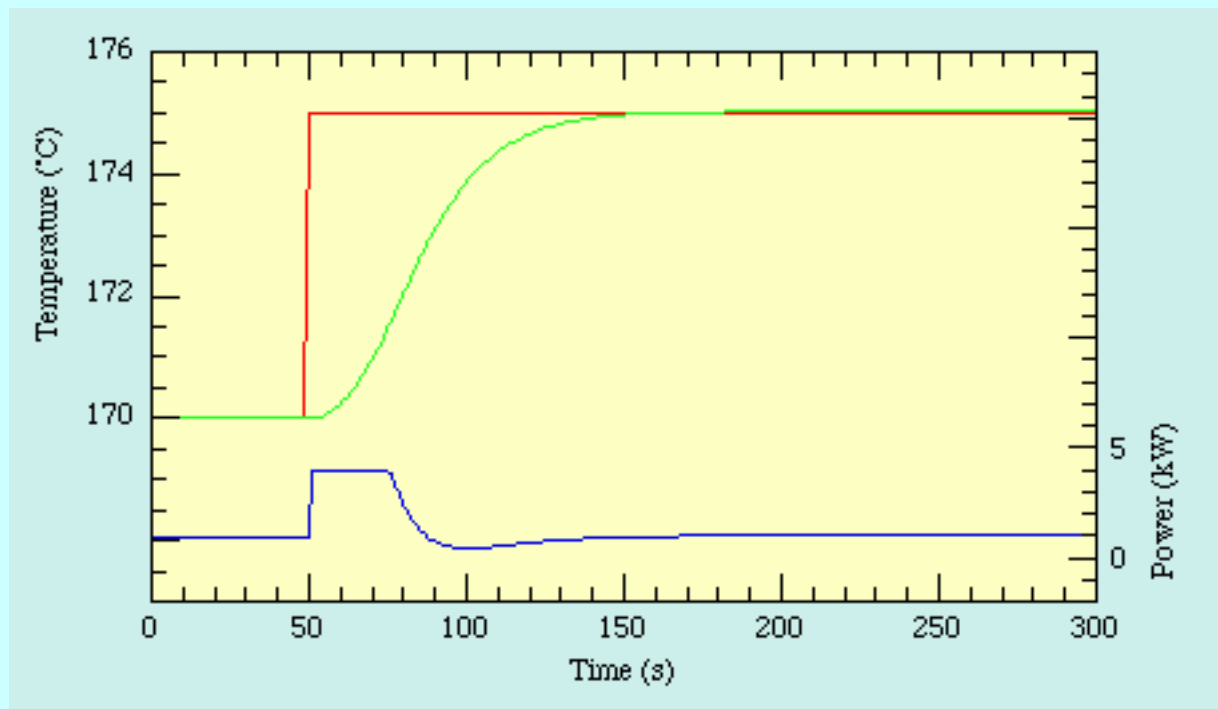we'll later look at methods  
to solve such system  
equations using transforms



# Temperature control circuit

- Notes

- $R_1 \gg R_2$  to avoid loading

- still need heating circuit

want  $W \propto V_{out}$

- Diode ensures  $W \geq 0$

$V_{diode}?$


- Time constants to be selected

depend on appliance chosen

commercial devices will recommend values

- Need to consider offset currents and voltages

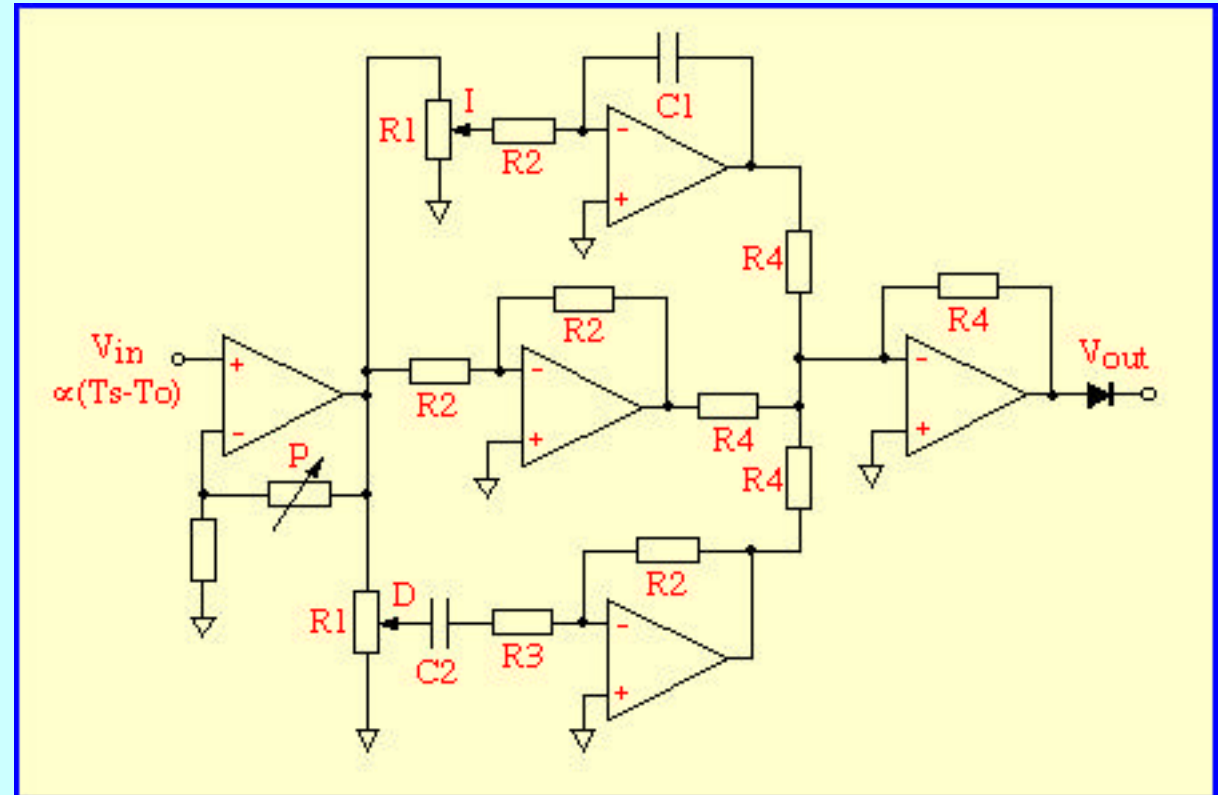null, or consider more complex circuit design





# Instrumentation amplifier

- **High gain, dc-coupled differential amplifier**

single ended output

high input impedance


high CMRR

use to amplify small differential signals where large CM signal may be present

but small normal mode

eg strain gauge, other bridge circuits

"weak" voltage source

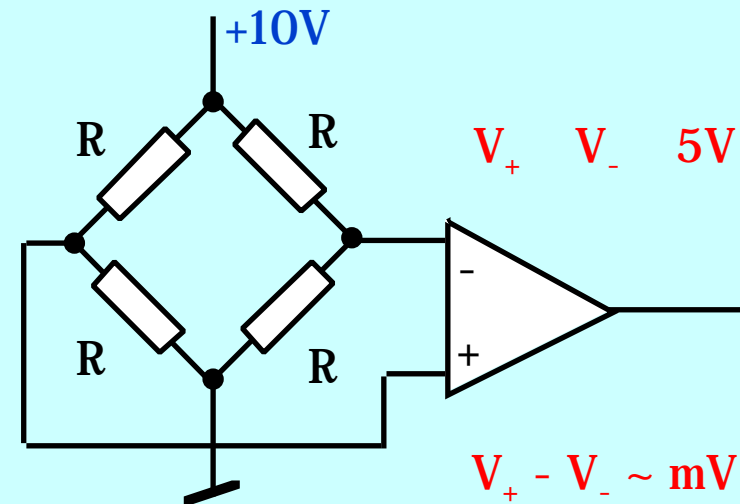

To measure 5mV signal with  
1% error

$$CMRR = 0.05/5000 = 100dB$$

- **Drawback of differential amplifier**

relatively low input impedance

CMRR relies on excellent resistor matching

cheap op-amps may have CMRR ~80dB

# Improved differential amplifier

- Add voltage buffers and choose precise resistors

improves input impedance

0.1% resistors available


careful nulling of circuits

still need high CMRR from output amplifier

big demands on R precision

often find restrictions on driving circuit

ie source

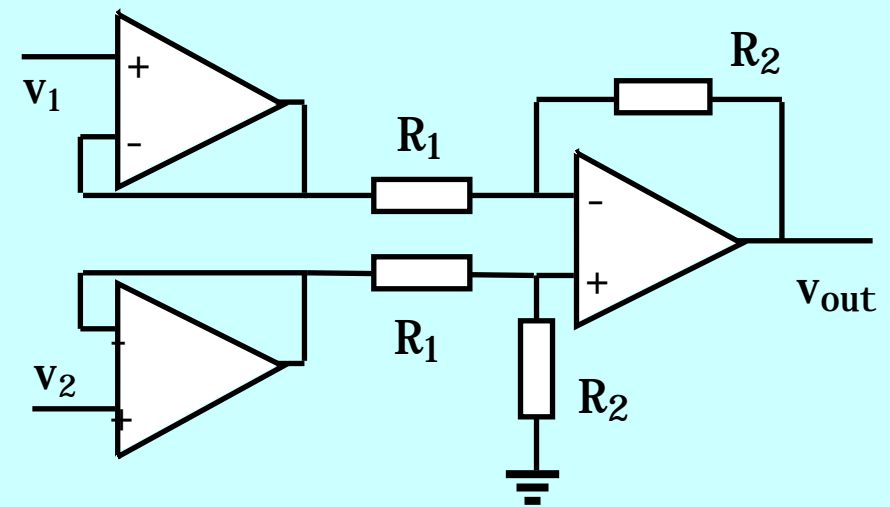

# Classic instrumentation amplifier

## • Input stage differential gain

$$v_{10} - v_1 = iR_2 = v_2 - v_{20} \quad (1)$$

$$iR_1 = v_1 - v_2$$

$$(v_{10} - v_{20}) - (v_1 - v_2) = 2iR_2$$

$$(v_{10} - v_{20}) = 2iR_2 + iR_1$$

$$= (v_1 - v_2)(2R_2 + R_1)/R_1$$

$$G_{\text{diff}} = 1 + 2R_2/R_1$$

## • Input stage common mode gain

$$v_1 = v_{\text{CM}} + u_1$$

$$v_2 = v_{\text{CM}} + u_2$$


$$2v_{\text{CM}} = v_1 + v_2 \text{ with signal } u_1 = u_2 = 0$$

$$\text{From (1) } v_{10} + v_{20} = v_1 + v_2$$

$$G_{\text{CM}} = 1$$

## • Remainder is normal differential amplifier, ( $G = 1$ in this case)

Instrumentation ICs available

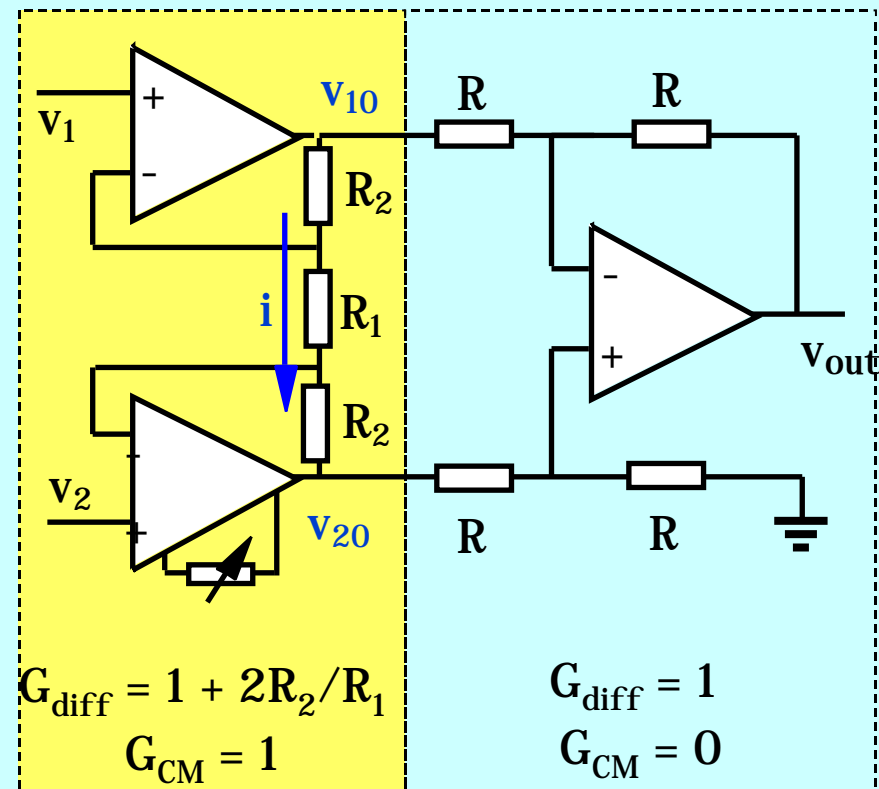

Reduce requirements on second stage  
still choose input amps for good CMRR  
and null carefully

# The Instrumentation Amplifier in practice

- Can add some more useful features

feed common mode level back as guard

*connect to cable shield*

*reduce effects of cable capacitance, leakage currents*

sense voltage at load

*allows feedback to correct for losses in wiring*

*or offset of DC conditions*

