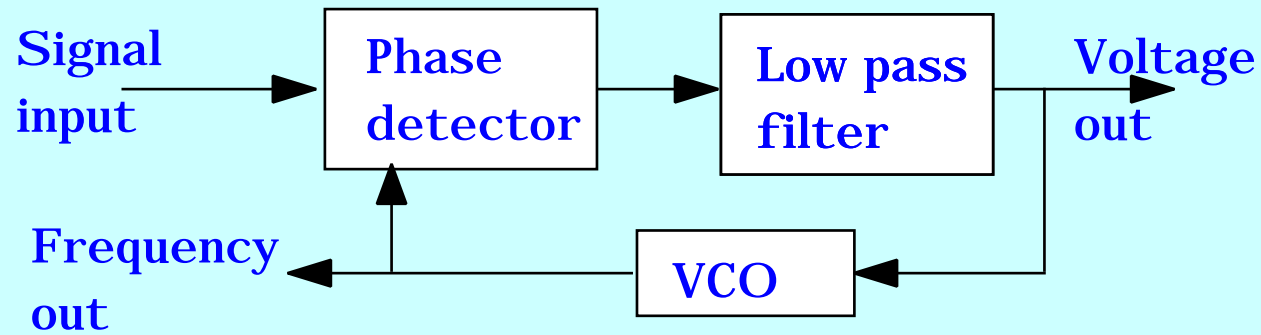


Phase Locked Loops - PLL

- **frequency selective feedback system**

wide use in FM detectors, stereo demodulators, tone decoders, frequency synthesisers, frequency synchronisation,...



- **Voltage Controlled Oscillator**

in feedback loop

reference oscillation, with frequency dependent on DC voltage

- **Phase detector**

compares periodic input signal with output of VCO and adjusts in response

- **Low pass filter**

generates correction voltage from phase detector output

PLL operation

- **No signal present**

error voltage = 0

VCO "free runs" at f_0

- **Apply periodic signal at f_s**


f_s f_0

phase comparison with VCO generates error voltage...

...which forces VCO to synchronise with f_s

PLL "locks" onto input frequency

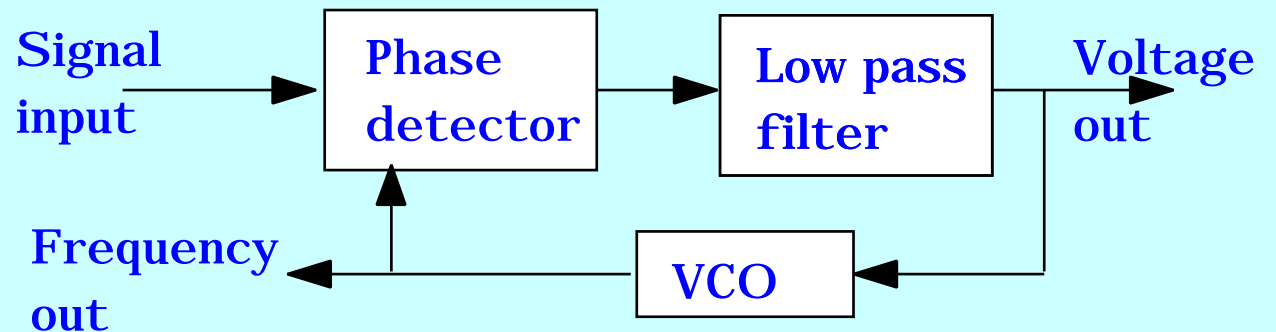VCO frequency identical to input frequency, but with phase difference



- **If input frequency varies slowly, PLL will remain locked**

will track input frequency

eg input clock with jitter (phase noise), PLL will "clean up" clock

FM radio: audio signal much lower frequency than carrier

voltage output will follow audio

Phase sensitive detection

- Mix input and reference signals

$$V \sim \sin \omega_0 t \cdot \sin \omega_s t$$

produces two components

$$f \sim 2f_0$$

$f = f$ ie low frequency

- pass through low pass filter


$$\gg 1/f$$

produces error voltage


- actual method different

$$V_{\text{error}} = A \cos \theta$$

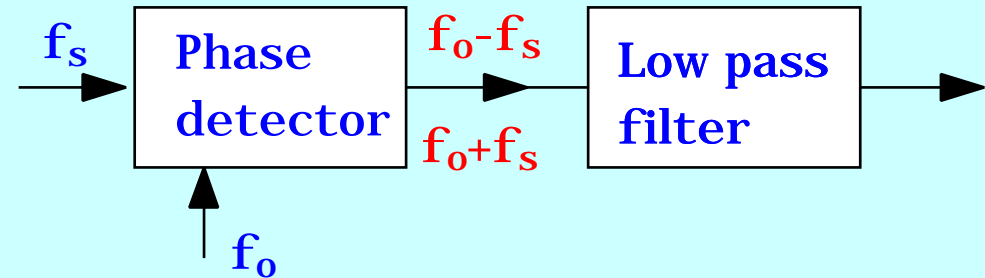cos dependence not ideal for real applications



VCO output

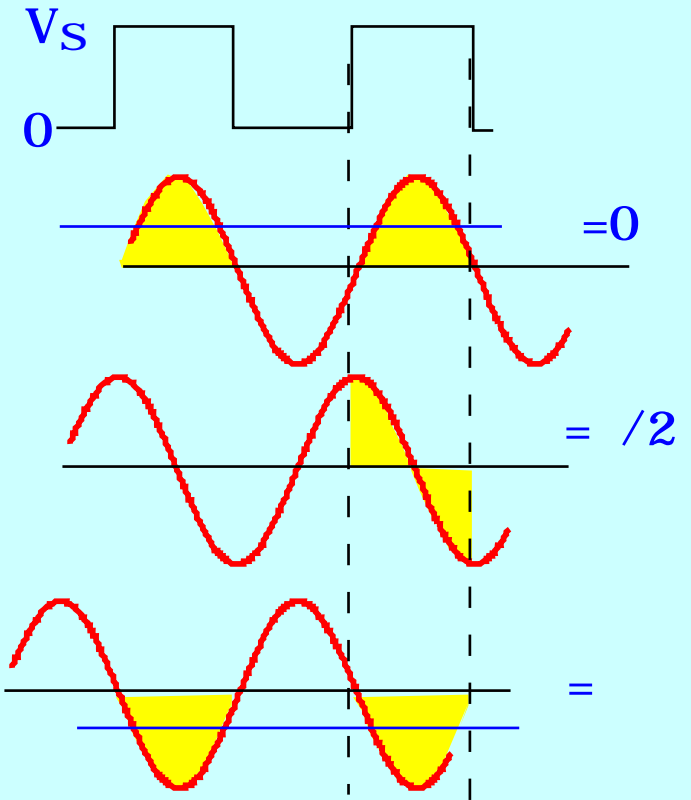


error voltage > 0

error voltage = 0

error voltage < 0


Improved phase detector

- Transform sine wave to square wave

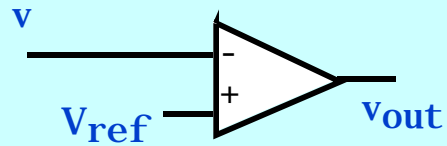

$$V_{ref} = (v_{max} - v_{min})/2$$

or input may already be pulsed


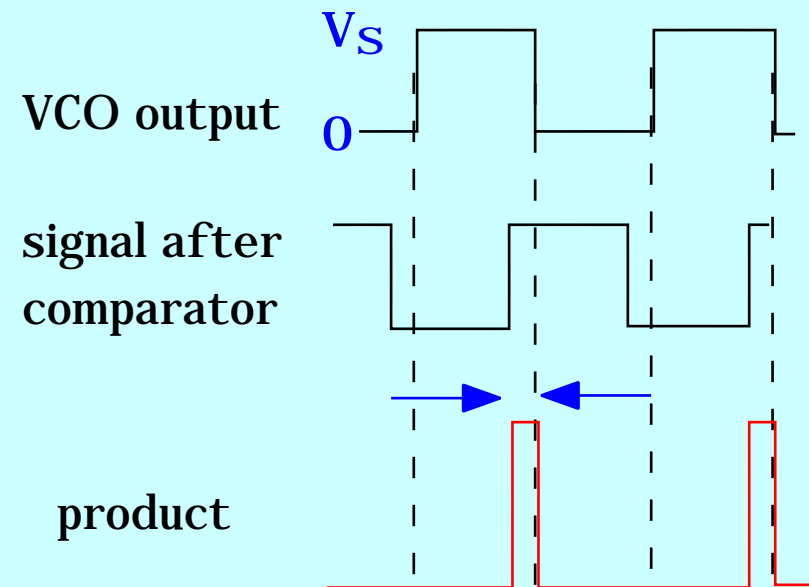


Voltage Controlled Oscillator VCO

- ideal VCO behaviour

- moderate frequency example

nMOS = switch

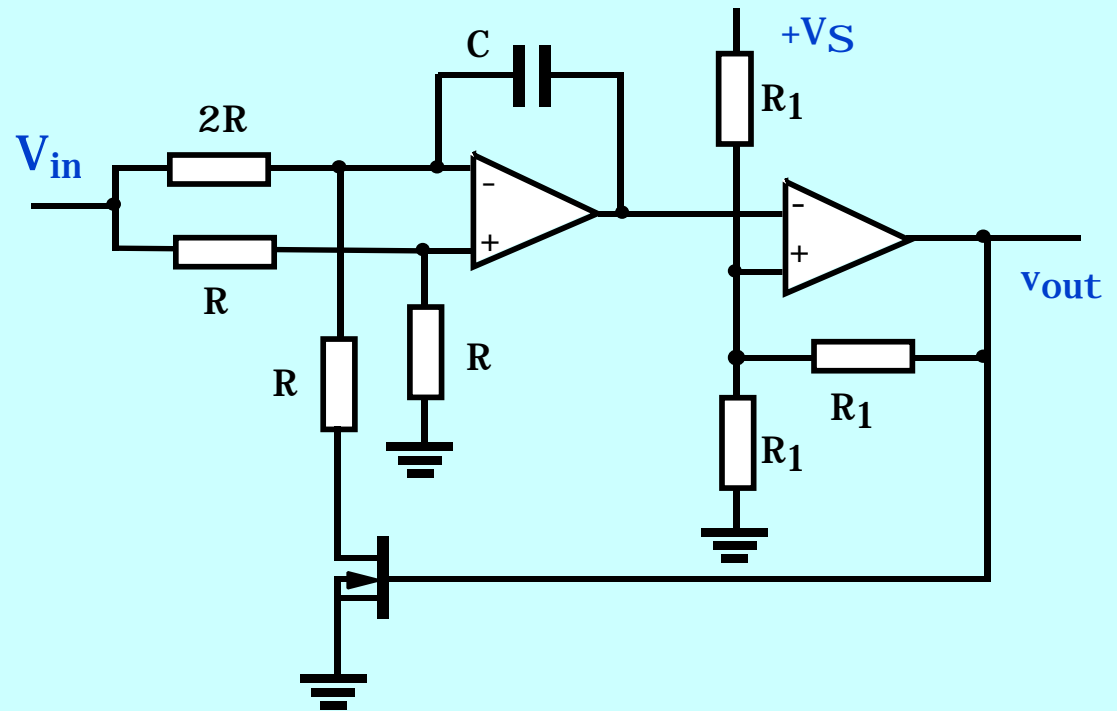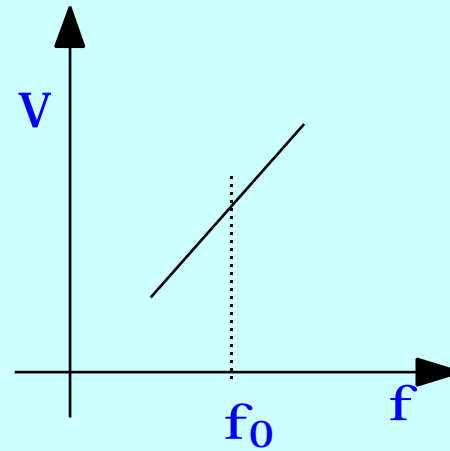


PLL operation

- For phase locking, require $f_s \approx f_0$
=> sensitive to finite range of frequencies
- Capture range
frequency range over which PLL can lock on signal
- Lock range
frequency range over which PLL can track input variation
- Role of low pass filter - decreasing bandwidth (increasing τ)
slows capture process, increases time to lock
decreases capture range
once locked, greater immunity to high frequency interference
transient response to sudden changes in frequency within capture range becomes underdamped

PLL applications (i)

- **FM demodulation**


PLL tracks variation in frequency

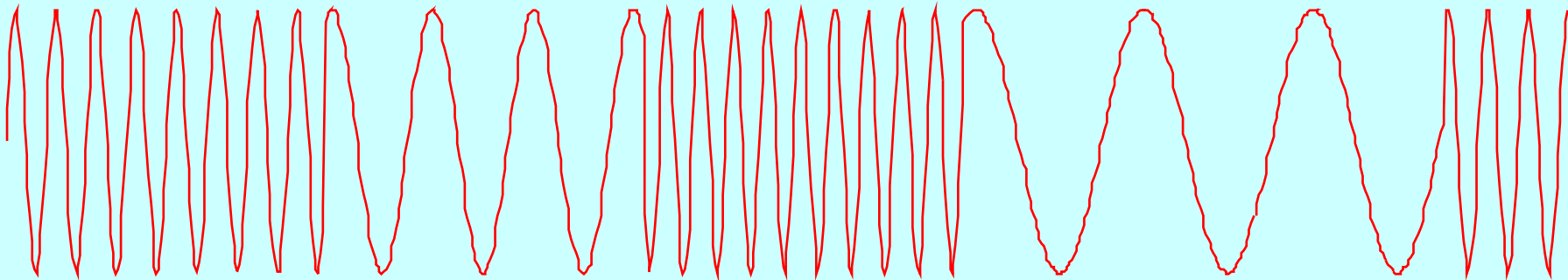

also used in Frequency-shift keying - where mark/space ratio changes, not f

- **AM detection**

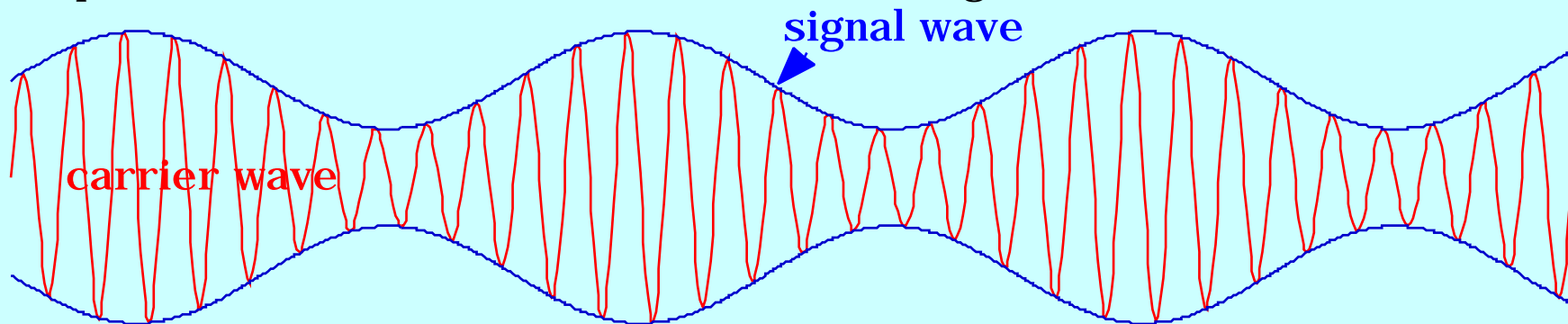if input is sinusoidal, then PLL can demodulate signal from carrier




PLL applications (ii)

- **Frequency synchronisation and signal conditioning**

a poor oscillator can be locked to good reference signal - eg colour TV
remove out-of-range interference, ie phase jitter

- **Synchronisation for control**

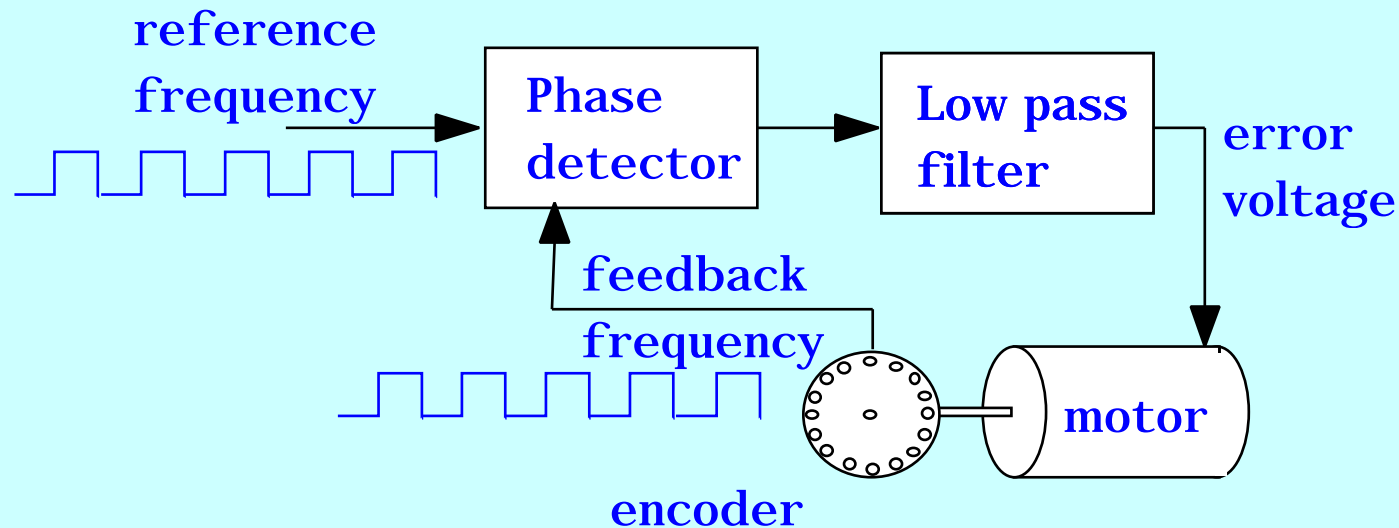eg motor speed - required for many applications
eg CD player



PLL applications (iii)

- **Frequency synthesis**

multiply reference frequency by N, by dividing output in feedback loop

- **Frequency translation**

by adjusting response to out of phase signal at input, can offset by small Δf

- **Tone or carrier detection**

simply detect if a given frequency is present with magnitude above threshold
useful eg in stereo decoders, modem