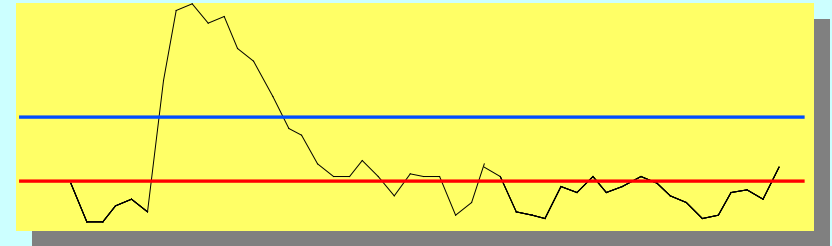


Noise

- **What is NOISE?** A definition:

Any unwanted signal obscuring signal to be observed

two main origins



- **EXTRINSIC NOISE** examples...

pickup from external sources unwanted feedback

RF interference from system or elsewhere, power supply fluctuations

ground currents

small voltage differences => currents can couple into system

may be hard to distinguish from genuine signals *but* **AVOIDABLE**

Assembly & connections, especially to ground, are important

- **INTRINSIC NOISE**

Fundamental property of detector or amplifying electronics

Can't be eliminated but can be MINIMISED

Origins of noise in amplifying systems

•1. Thermal noise

Quantum-statistical phenomenon

Charge carriers in constant thermal motion

macroscopic fluctuations in electrical state of system

•2. Shot noise

Random fluctuations in DC current flow

originates in quantisation of charge

non-continuous current

•3. 1/f noise

Characteristic of many physical systems

least well understood noise source

commonly associated with interface states in MOS electronics

Thermal noise (i)

- Einstein (1906) , Johnson, Nyquist (1928)

e.g. resistor: $\sim 10^{23}$ possible states

macroscopic statistical average over micro-states

- Experimental observation

Mean voltage $\langle v \rangle = 0$

Variance $\langle v^2 \rangle = 4kT.R. f$ $f =$ observing bandwidth

$(v) = \langle v^2 \rangle = 1.3 \cdot 10^{-10} (R. f)^{1/2}$ volts at 300K

e.g. $R = 1M$ $f = 1Hz$ $(v) = 0.13\mu V$

**gaussian distribution
of fluctuations in v**

Noise power = $4kT. f$

independent of R & q independent of f - WHITE

- Quantum effects



Normal mode energies: kT $hf / (e^{hf/kT} - 1)$ $kT \gg hf$

at $300^\circ K$ $kT = 0.026$ eV $hf = kT$ at $f = 6.10^{12}$ Hz

Thermal noise (ii)

- **Circuit representations**

Noise generator + noiseless resistance R

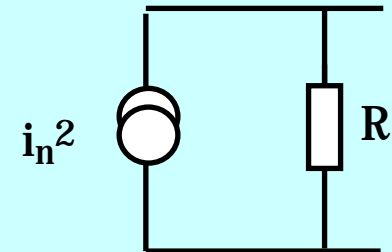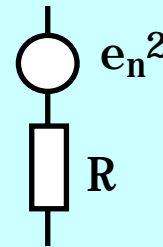

- **Spectral densities**

mean square noise voltage or current per unit frequency interval


$$w_V(f) = 4kTR \quad (\text{voltage})$$

$$w_I(f) = 4kT/R \quad (\text{current})$$

- **Why not infinite fluctuation in infinite bandwidth?**

A-1: QM formula $\rightarrow 0$ at high f

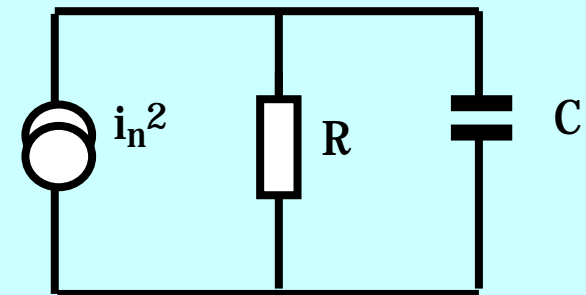A-2: real components have
capacitive behaviour (high f)
or inductive (low f).




with R and C in parallel $\langle v^2 \rangle = kT/C$

Shot noise

- **Poisson fluctuations of charge carrier number**

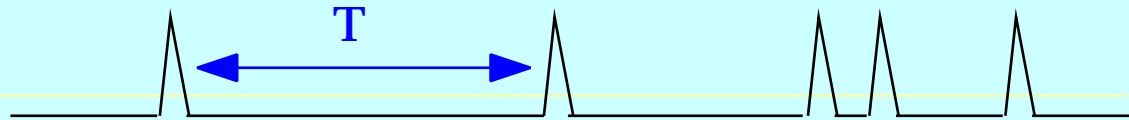eg arrival of charges at electrode in system - induce charges on electrode



quantised in amplitude and time

- **Examples**

electrons/holes crossing potential barrier in diode or transistor

electron flow in vacuum tube

$$\langle i_n^2 \rangle = 2qI \cdot f \quad \text{WHITE} \quad (\text{NB notation } e = q)$$

I = DC current

gaussian distribution
of fluctuations in i

1/f noise

- White noise sources frequently dominate in many real systems

however frequency dependent noise is also common

- 1/f noise is a generic term for a wide range of phenomena, possibly not always related

Power spectral density


$$w(f) = A_f / f^n \quad n \sim 0.8-1.5 \text{ typical}$$

- Most important for MOS FET devices,

often dominates

but can also arise in other circumstances

e.g. dielectrics,...

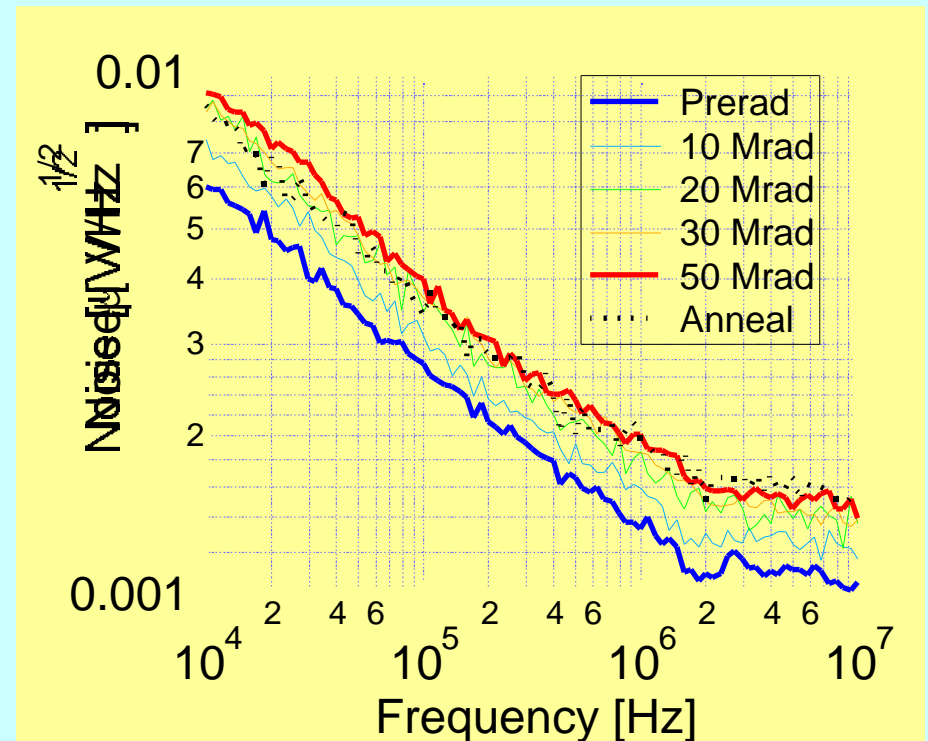

pMOS transistor noise spectrum

An explanation for 1/f noise

- Silicon MOS transistors are very sensitive to oxide interface

typically populated by band-gap energy levels (traps)

traps exchange charge with channel - ie. emit and capture electrons or holes

- Traps have lifetime to retain charge $h(t) \sim e^{-t/\tau}$

Expect a range of traps with different time constants, distributed with $p(\tau)$

in frequency domain $H(\omega) \sim 1/(1+j\omega\tau)$

Deduce frequency spectrum by integrating over all values of

$$w(f) \sim \int_0^\infty p(\tau) |H(\omega)|^2 d\tau$$

If $p(\tau) = \text{constant}$, ie all time constants equally probable

$$w(f) \sim \int_0^\infty d\tau / (1 + \omega^2 \tau^2) \quad [\text{standard integral, put } \tan \theta = \omega\tau]$$
$$= A/f$$

Many other real-life processes have $e^{-t/\tau}$ time distributions -

typical of random, Poisson-type processes

Campbell's theorem - time domain

- Most amplifying systems designed to be linear

$$S(t) = S_1(t) + S_2(t) + S_3(t) + \dots$$

- Impulse response $h(t)$ = response to




- In a linear system, if random impulses occur at rate n

$$\text{average response } \langle v \rangle = n \int_0^{t_{\text{obs}}} h(t) dt \quad (\text{A})$$

$$\text{variance } \sigma^2 = n \int_0^{t_{\text{obs}}} [h^2(t)] dt \quad (\text{B})$$

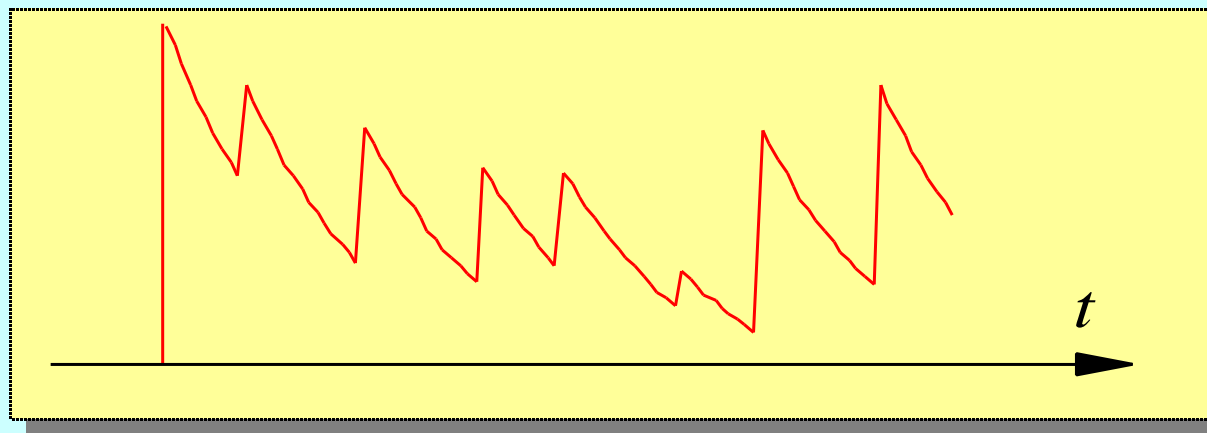i.e. sum all pulses preceding time, t_{obs} , of observation



Campbell's theorem - frequency domain

- Recall relationship between impulse response $h(t)$ and transfer function $H(\omega)$

$$H(\omega) = \int_{-\infty}^{\infty} h(t) \cdot e^{-j\omega t} dt \quad h(t) = \int_{-\infty}^{\infty} H(\omega) e^{j\omega t} d\omega \quad H(\omega) = v_{\text{out}}(\omega) / v_{\text{in}}(\omega)$$

- Rewrite (B) using Parseval's Theorem

$$\int_{-\infty}^{\infty} h^2(t) dt = \int_{-\infty}^{\infty} |H(\omega)|^2 d\omega = 2 \int_0^{\infty} |H(\omega)|^2 d\omega$$

$h(t)$ is real and thus
 $H(-\omega) = H^*(\omega)$

$$\text{so } S^2 = n \int_{-\infty}^{\infty} h^2(t) dt = n \int_{-\infty}^{\infty} |H(\omega)|^2 d\omega$$

This relates noise spectral densities at input and output:

$$w_{\text{out}}(f) = w_{\text{in}}(f) |H(\omega)|^2 \quad \text{can use theorem to calculate system response to noise}$$

- eg. shot noise Consider impulse response to be impulse (ie unchanged!)


$$h(t) = \delta(t) \Rightarrow H(\omega) = 1$$

$$S^2 = n e^2 \int_{-\infty}^{\infty} \delta^2(t) dt = n e^2 \int_{-\infty}^{\infty} |H(\omega)|^2 d\omega = 2 n e^2 \int_0^{\infty} d\omega$$

$$\text{but } n = I/e \Rightarrow S^2 = \underline{2eI} \int_0^{\infty} d\omega$$

Amplifier systems for spectroscopy

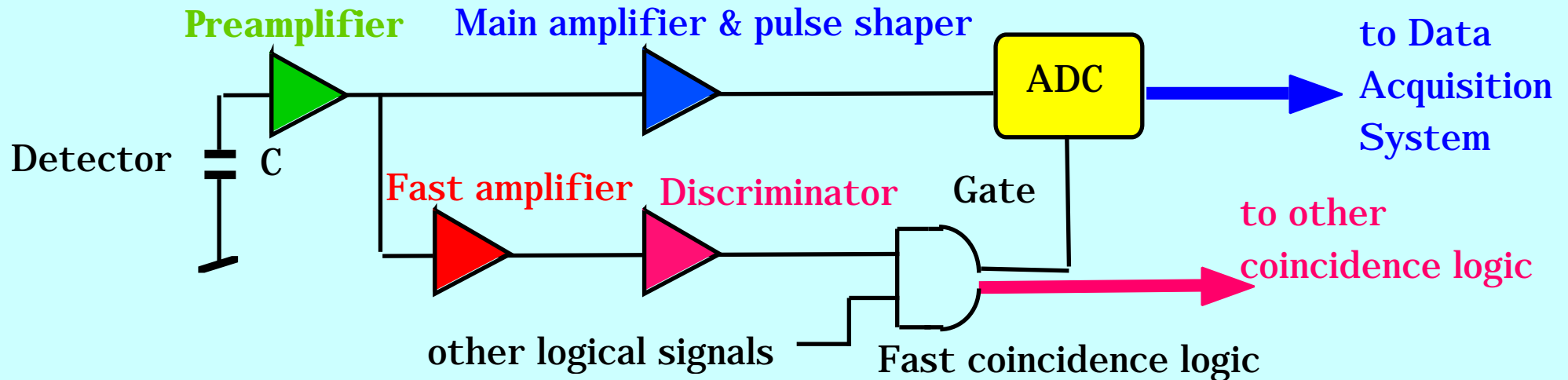- typical application - precise measurements of x-ray or gamma-ray energies



- pre-amplifier *first stage of amplification*

- main amplifier - *adds gain and provides bandwidth limiting*

ADC - analogue to digital conversion - *signal amplitude to binary number*

- fast amplifier and logic -

start ADC ("gate") and flag interesting "events" to DAQ system

- most signals arrive randomly in time.

Other logic required to maximise chance of "good" event, eg second detector

"Rules" of low noise amplifier systems

- **Combine uncorrelated noise sources in quadrature**

$$e_{\text{tot}}^2 = e_1^2 + e_2^2 + e_3^2 + \dots + i_n^2 R^2 + \dots$$

follows from Campbell's theorem

consider as combinations of gaussian distributions

- **First stage of amplifier dominates**

noise originates at input


- **Noise is independent of amplifier gain or input impedance**

so noise can be referred to input

- **In real systems both are approximations - but normally good ones**

so often sufficient to focus on input device

Amplifiers - dominance of input stage

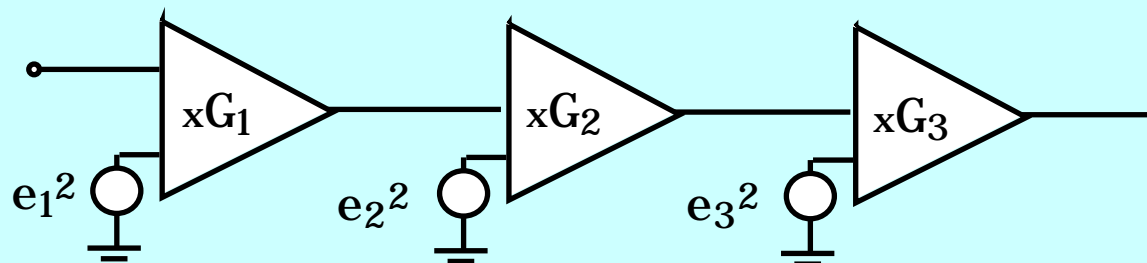

- Amplifier systems (and amplifiers!) usually consist of several stages

impractical to put all gain at one location - power, heating, material, size,...

- Calculate signal and noise at output

$S_{\text{out}} = G_1 \cdot G_2 \cdot G_3 S_{\text{in}}$ for 3 stage system, but can easily extend to N

$$(e_{\text{out}})^2 = G_1^2 \cdot G_2^2 \cdot G_3^2 e_1^2 + G_2^2 \cdot G_3^2 e_2^2 + G_3^2 e_3^2$$


$$(e_{\text{out}} / S_{\text{out}})^2 = (e_1^2 + e_2^2 / G_1^2 + e_3^2 / G_1^2 \cdot G_2^2) / S_{\text{in}}^2$$

- Desirable to maximise gain at input stage


eg stage 1 boosts signal enough for transmission down cable and should be large enough that environmental noise is not significant

Amplifiers - location of noise sources

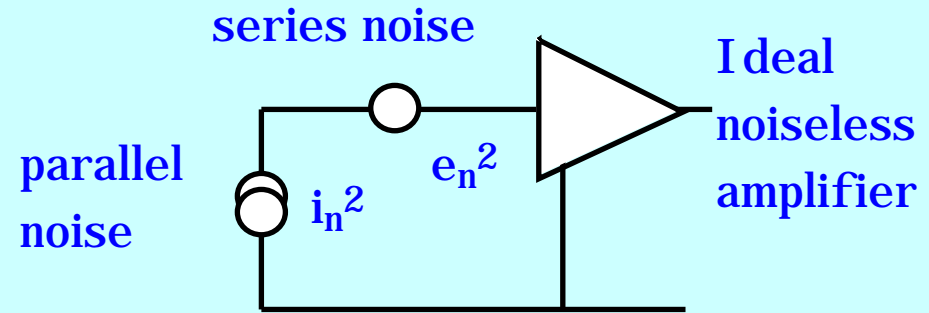
- **Normal to partition noise sources**
not fundamental to calculations
but can simplify!



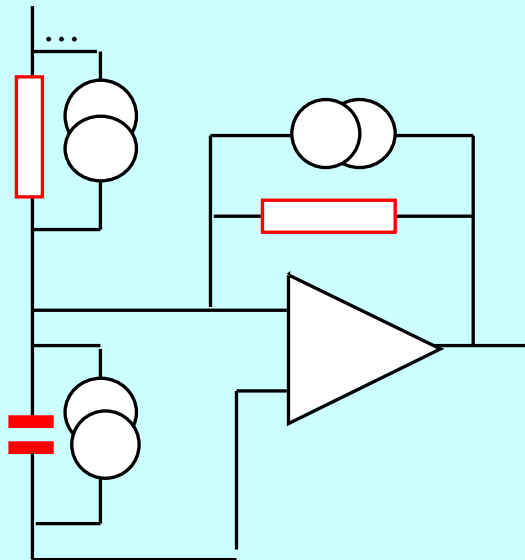
- **Parallel noise sources** appear as currents at input
detector leakage current
bias resistors
feedback resistor



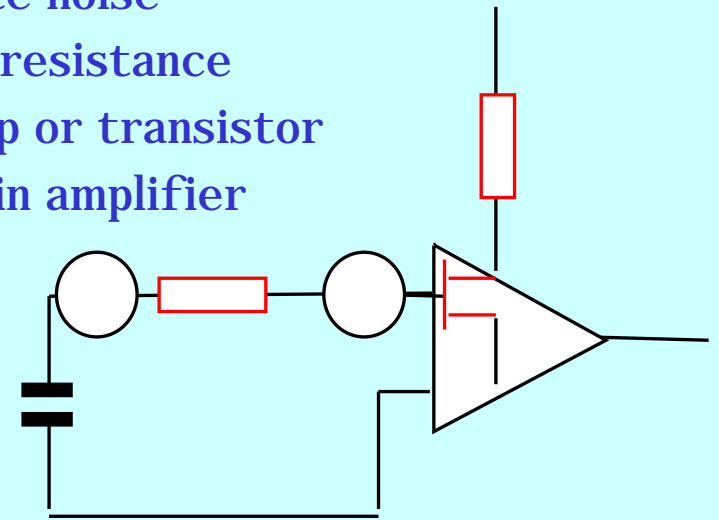- **Series noise sources** appear as voltage at input
transistor gate noise
device series resistance
microstrip or transistor
load resistor in amplifier
...



Amplifiers - reference to input

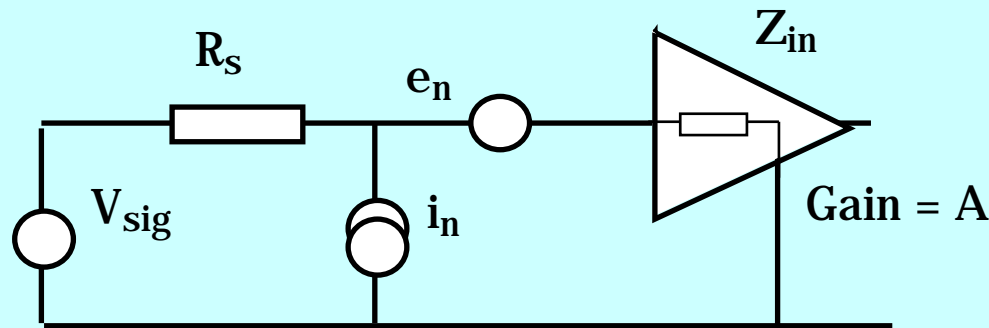

assume:
 signal source and associated impedance
 noise sources
 amplifier with gain & input impedance

• noise at output

$$E_{no}^2 = A^2 \{ e_n^2 Z_{in}^2 / (Z_{in} + R_s)^2 + i_n^2 R_s^2 Z_{in}^2 / (Z_{in} + R_s)^2 \}$$

• transfer function

$$K = V_{out} / V_{in} = A \cdot V_{sig} \cdot Z_{in} / (Z_{in} + R_s) V_{sig} = A Z_{in} / (Z_{in} + R_s)$$

• noise at input

$$E_{ni}^2 = E_{no}^2 / K^2 \Rightarrow E_{ni}^2 = e_n^2 + i_n^2 R_s^2 \quad \underline{\text{no } Z_{in} \text{ or } A \text{ dependence}}$$

easy to show analogous result $I_{ni}^2 = i_n^2 + e_n^2 / R_s^2$ choice is for convenience


in most detector systems, there is a current signal source and a parallel capacitance

• then the spectral distribution of noise at the input is affected

$$I_{ni}^2 = i_n^2 + e_n^2 \omega^2 C^2 \quad \underline{\text{no longer white}}$$

Real amplifiers

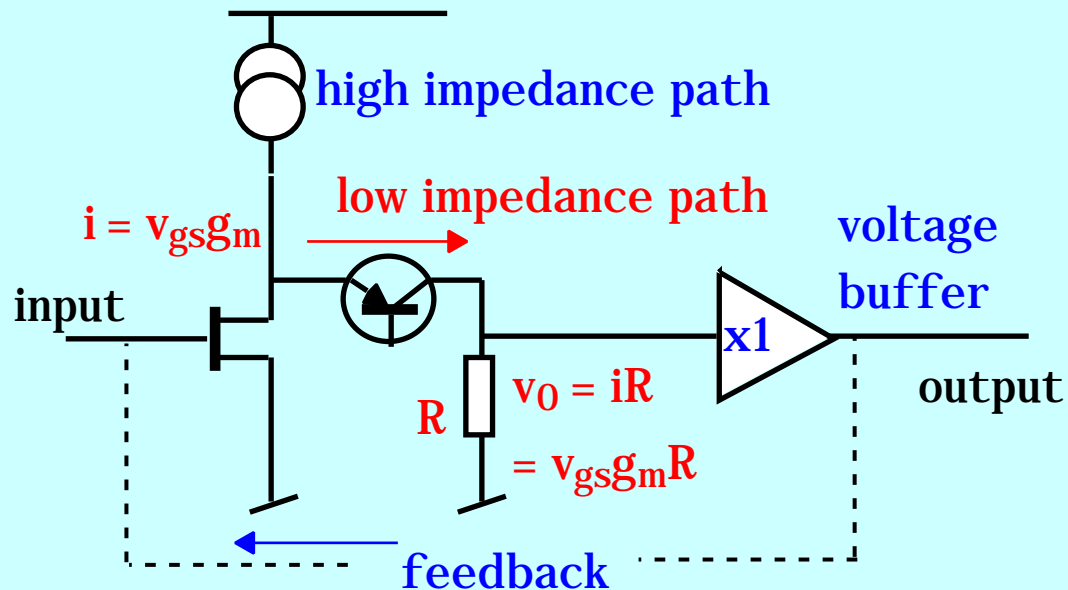- The first amplifier stage dominates - reason for distinction of pre-amplifier
most low-noise amplifiers are based on very simple concepts



voltage amplifier
 $G = g_m R$

add feedback to define type
eg. charge or current sensitive

within the preamplifier we expect the input device to be the most important

- To understand noise performance we need to study input device
bipolar or FET

Bipolar transistor noise

- **Two shot noise sources**

Fluctuations in I_C $i_c^2 = 2eI_C f$

Fluctuations in I_B $i_b^2 = 2eI_B f$

but these are correlated since $I_B = I_C/\beta$

- **Thermal noise in base & contacts** $e_b^2 = 4kTr_b f$

r_b = base spreading resistance



- **Transfer noise sources to input**

use $v_{be} = i_c r_e = (kT/qI_c)i_c$

$e_n^2 = (4kTr_b + 2qI_c r_e^2) f = [4kTr_b + 2(kT)^2/qI_c] f$

$i_n^2 = 2eI_B f$

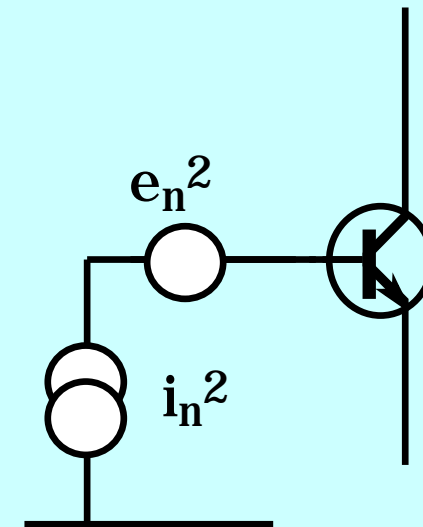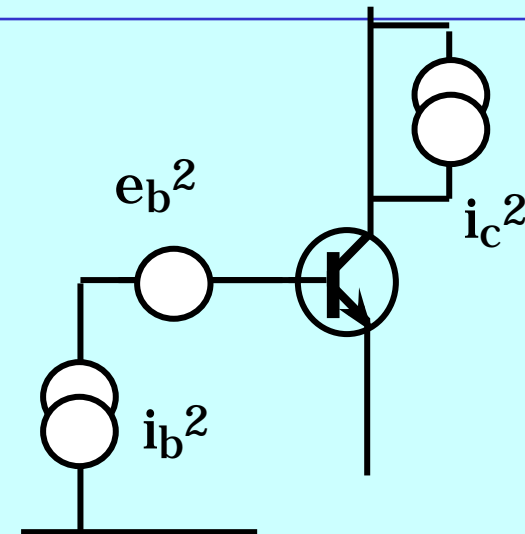- **The constraint that i_n^2, e_n^2 are correlated gives a limited range of noise with best performance for high speed applications**



Some useful numerical values

$$kT/e \quad 0.025 \text{ V} = 25\text{mV} \quad \text{at } 293\text{K} \quad (\text{Room temperature})$$

$$e = 1.6 \cdot 10^{-19} \text{ coulomb}$$

- Parallel noise - what resistor is equivalent to given current?

$$4kT/R_p = 2eI$$

$$I = 2(kT/e)(1/R_p) = 50\text{mV}/R$$

$$\text{eg, } 1\text{M} \quad 50\text{nA}$$

- Parallel noise spectral density - units and magnitudes

$$i_n = [2eI_B]^{1/2} = [32e^{-18}I_B]^{1/2} = 0.6I_B^{1/2} \text{ nA}/\sqrt{\text{Hz}}$$

$$\text{eg, } 3\text{A} \quad 1\text{nA}/\text{Hz} \quad 3\mu\text{A} \quad 1\text{pA}/\text{Hz}$$

- Series noise spectral density - units and magnitudes

$$e_n = [4kTR_s]^{1/2} = [4(kT/e)eR]^{1/2} = [1.6 \cdot 10^{-20}R]^{1/2} = 0.13R^{1/2} \text{ nV}/\sqrt{\text{Hz}}$$

$$\text{eg, } 60 \quad 1\text{nV}/\text{Hz}$$

Bipolar noise example

• r_b is often small so neglect

	$I_C = 1\text{mA}$ $I_B = 10\mu\text{A}$	$I_C = 100\mu\text{A}$ $I_B = 1\mu\text{A}$
$\beta = 100$		
$e_n = [2(kT)^2/qI_C]^{1/2}$ $= [2(kT/q)^2(q/I_C)]^{1/2}$	0.45 nV/ Hz	1.4 nV/ Hz
$i_n = [2qI_B]^{1/2}$	1.8 pA/ Hz	0.6 pA/Hz
$i_n R_S$ for $R_S = 1\text{k}$	1.8 nV/ Hz	0.6 nV/Hz
$[4kTR_S]^{1/2}$ for $R_S = 1\text{k}$	4.0 nV/ Hz	4.0 nV/ Hz
NF for $R_S = 1\text{k}$	0.84 dB	0.59 dB

• Noise figure - often used to characterise voltage amplifier performance

$$\text{NF [dB]} = 10\log_{10}(\text{Total noise power at input}/\text{Source noise power})$$

$$= 10\log_{10}\left(\frac{e_n^2 + i_n^2 R_s^2 + 4kTR_s}{4kTR_s}\right) = 10\log_{10}\left(1 + \frac{e_n^2 + i_n^2 R_s^2}{4kTR_s}\right)$$

MOSFET Noise

- Gate current shot noise

$$i_g^2 = 2eI_G f \quad \text{negligibly small for most applications}$$

high impedance of gate oxide (insulator) to substrate

- Thermal noise inside the transistor

thermal current fluctuations in channel (- but **not** shot)

$$i_d^2 = (4kT/R_n) f = 4kT(2/3)g_m f$$



$$1/f \text{ noise} \quad e_n^2 \quad A/f$$

- Transfer noise sources to input

$$i_d = g_m v_{gs} \Rightarrow e_n^2 = i_d^2 / g_m^2$$

$$e_n^2 = [4kT(2/3g_m) + A/f] f$$

$$i_n^2 = 0$$

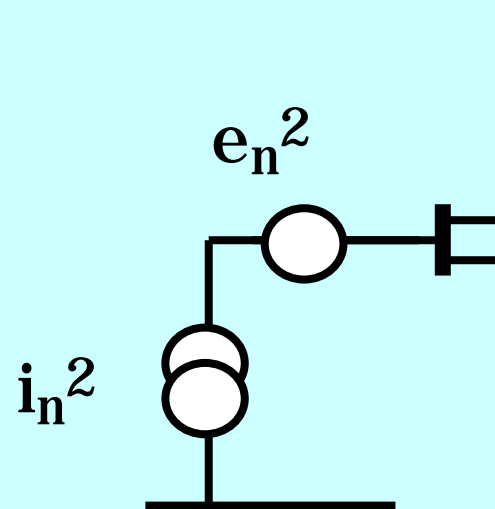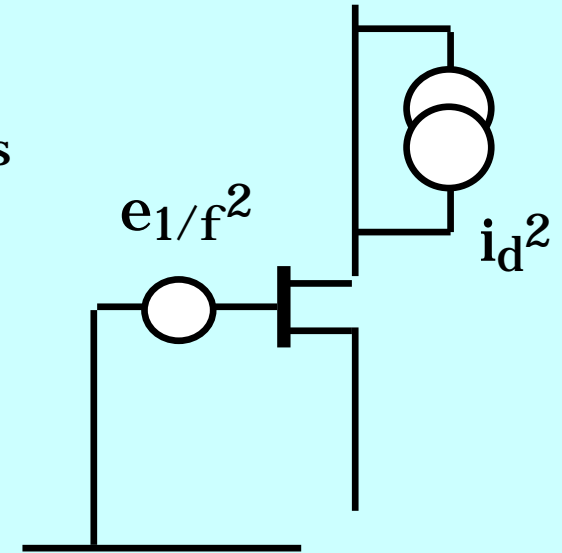

MOSFET thermal noise

- Parameters are (almost) controlled by geometry and current alone

$$g_m = [2\mu C_{ox}(W/L)I_{DS}]^{1/2} \quad C_{ox} = \epsilon_{ox}/t_{ox}$$

$$e_n^2 = 4kT(2/3g_m) \quad f \sim 1/g_m$$

- How to get large g_m ?

Increase I_{DS} - but $e_n \sim I^{-1/4}$ power is a concern

Increase C_{ox} - it scales with technology feature size so modern processes help

1980 $\sim 10\mu\text{m}$ 2000 $\sim 0.25\mu\text{m}$ for L_{\min} $0.25\mu\text{m}$ $t_{ox} \sim 5\text{nm}$

Make W/L large

W can be made very large, eg 2-3mm

L can be minimum feature size

Cooling - can gain small amount - but device heats

- Caveat carrier mobility μ - unfortunately not a constant

carriers typically approach saturation velocity at high electric fields

$1\text{V}/0.25\mu\text{m} = 4 \times 10^4 \text{ V/cm}$ so $\mu = v/E$ falls as transistors shrink

MOSFET 1/f noise

- $e_{1/f}^2 = A_f/f$

$$A_f = K_f/[WL(C_{ox})^2]$$

K_f is technology dependent $K_f \sim 10^{-30} - 10^{-32} \text{ C.cm}^{-2}$

PMOS transistors are significantly better than NMOS

- **Corner frequency**

f_{corner} where $e_{\text{thermal}} = e_f$ typically $\sim 10\text{-}1000\text{kHz}$

dependent on technology details, device dimensions

JFET Noise

- Almost identical to MOSFET

- - differences are

Negligible $1/f$ noise - channel is buried below surface

Small gate current - gate is p-n diode

both can be reduced by cooling

- JFET is interesting for high resolution spectroscopy

allows to employ long shaping time constants (low f)

because of the very low $1/f$ noise

- Noise sources referred to input

$$e_n^2 = 4kT(2/3g_m) f$$

$$i_n^2 = 2eI_g f$$

