 


Instrumentation Problem Sheet 4 Amplifiers


(1) An amplifier has an open loop voltage gain of 140dB at $f=0\text{Hz}$ and a single pole at $f = 100\text{Hz}$. What is the gain-bandwidth product (GBW)?

(2) The amplifier in the figure is designed with $R_1 = 10\text{k}$, $R_2 = 91\text{k}$. The open loop voltage gain is 100dB at $f=0\text{Hz}$ and the amplifier has one pole at $f = 100\text{Hz}$ and a second at 100kHz. What value of capacitor will ensure stability without affecting the gain too much at high frequencies where is it intended to operate?



(This problem is best solved starting with a graph.)

 
(3) Calculate the gain of the op-amp configuration shown in the figure.



 (4) A general version of the differential amplifier is shown in the figure. Show the output voltage is

$$v_{out} = v_2(R_3/R_1)[(R_1+R_f)/(R_2+R_3)] - v_1(R_f/R_1)$$


For a non-zero common mode signal v_{CM} , what is the resulting value of v_{out} ? Show that this reduces to $v_{out} = 0$ for $R_1 = R_2$ and $R_f = R_3$




The amplifier is built with $R_1 = R_2$ and $R_f = R_3$. If the resistor values have a 5% tolerance, what is the accuracy in the required gain? (Assume an ideal op-amp)

(5) Show that at high frequencies a current sensitive amplifier with a single low frequency pole has an input impedance which is inductive, instead of purely resistive. Calculate the value of L for an amplifier with DC gain = 60dB, GBW = 10^7 Hz and $R_f = 1\text{M}$. At what frequency would this become significant if the input load capacitance is 100pF?

 (6) What is the transistor current, the DC level at the output and the input impedance of the circuit of the circuit illustrated?



(10)

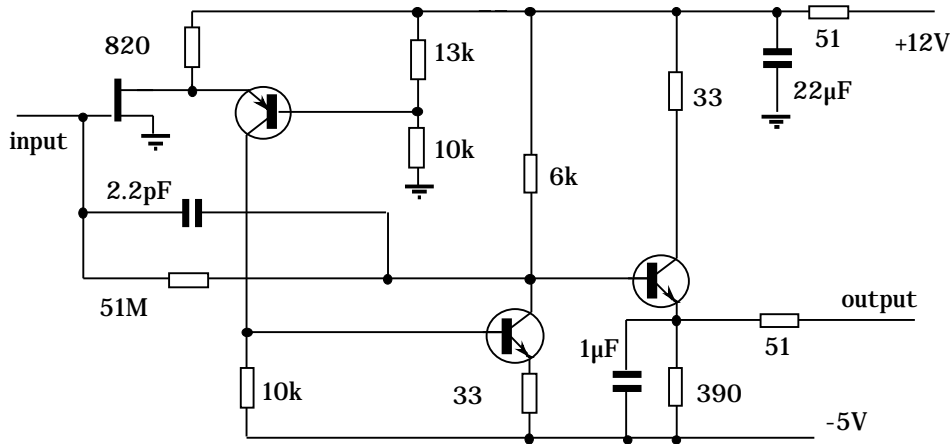

The figure above shows a slightly simplified charge sensitive amplifier. The parts of the circuit omitted ensure that the DC level at the output is approximately 0V. What is the impulse response and its time constant? What is the output impedance? What current flows in the input transistor? What are the advantages of this amplifier compared to the one in the previous problem? Identify the buffers and gain stages. Try to work out the DC bias conditions and power consumption. What is the gain if the transconductance of the input transistor is 10mA/V or 10mS? (Siemens = A/V)


(11) Show that a charge integrator followed by a differentiation stage produces a unipolar impulse response, ie with no baseline crossing. Show that two stages of differentiation produce a pulse shape which has an undershoot below the baseline. For differentiator time constants τ_1 and τ_2 , what is the relative magnitude of the undershoot? [Use transfer functions and work in frequency, then convert to time.]

(12) Show that the charge sensitive amplifier and high pass filter network in the figure has an output which is given by

$$v_o = A(Q/C_f)\exp(-t/\tau)$$

where $\tau = R_p R_f C / (R_p + R_f)$

 Find the condition on R_p which ensures this and the value of A.



(13) The charge sensitive amplifier of the previous problem is combined with further stage as shown in the figure to build an bandpass filter with two equal time constants. $R_f = 10M$ and $C_f = 1pF$. $C = 220pF$, $R = 12k$, $R_2 = 100k$ and $R_1 = 4.7k$. Suggest suitable values for R_p and C_2 . A 47 resistor is placed in series with the output. Can you suggest a reason?

