

Amplifiers

- This is a large and important part of this course

amplifiers are needed for many instruments

- inescapable in electronic instruments

even if not used to boost signals, amplifiers are the basis of most important functional blocks

- in many circumstances amplification, in the sense of “boosting” signals, is vital

signals to be measured or observed are often small

defined by source - or object being observed

and sensor - it is not usually easy to get large signals

data have to be transferred over long distances without errors

safest with “large” signals

System block diagrams

- Introduction to...

- Points to note

summing node

output from node = sum of signals entering


note signs at entry

pick-off node

all outgoing signals = incoming signal

functional blocks & directions of signals

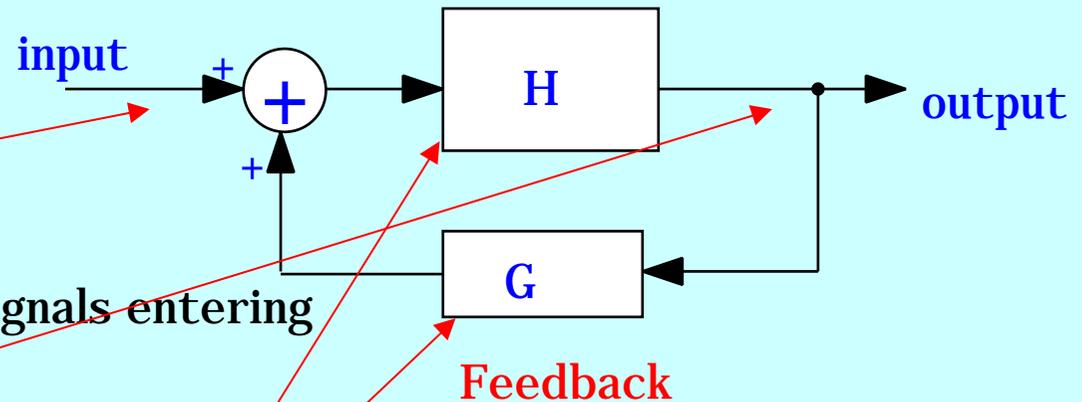usually label with transfer function of block



don't always distinguish summing nodes from others in diagrams - but only if it's very clear

- What kind of system?

electronic - but also mechanical, acoustic, optical,..

- How to manipulate?

label with signals, then follow rules

Feedback


- After summing node

$$u(t) = x(t) + Gy(t)$$

- At output

$y(t)$, but also $Hu(t)$

$$\text{so } y(t) = H[x(t) + Gy(t)]$$

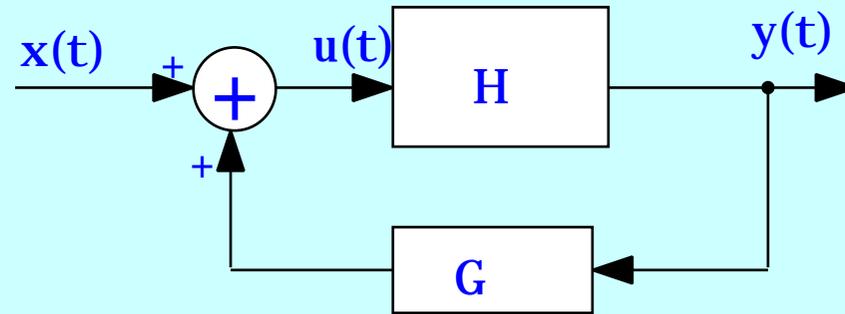

$$H_{\text{system}} = y(t)/x(t) = H/(1 - GH)$$

- Why is this useful?

suppose $H \gg 1$ then $H_{\text{system}} = -1/G$ ie. system transfer function independent of H

eg $0 < G < 1$ system provides constant amplification

$G =$ feedback fraction

- Problems -

perhaps $G \rightarrow 1/H$ $H_{\text{system}} \Rightarrow$ unstable - positive feedback

system will always be stable with negative feedback

- Applications...

Operational amplifier

- **A good starting point for analogue electronics**

will later consider devices and components used to build real amplifiers but the op-amp is a convenient idealisation

- **building block**

much electronics consists in recognising building blocks which perform specific functions

a large circuit can appear quite complex but can often be reduced to much simpler functional elements

- **First questions to ask in analysing amplifying system**

what quantity is being amplified? - eg. current, charge or voltage

what type of signals? eg. fast pulses or slow waveforms?

what is the input and output impedance? ie how should it be connected?

what is the gain?

- **some more detailed information...**

frequency response, linearity, noise level, ...

Operational amplifier approximation

- **very high gain voltage amplifier**

gain = A ->


infinite bandwidth

single output

dual, differential inputs, infinite impedance

amplifies difference in voltages between inputs

inputs are DC coupled

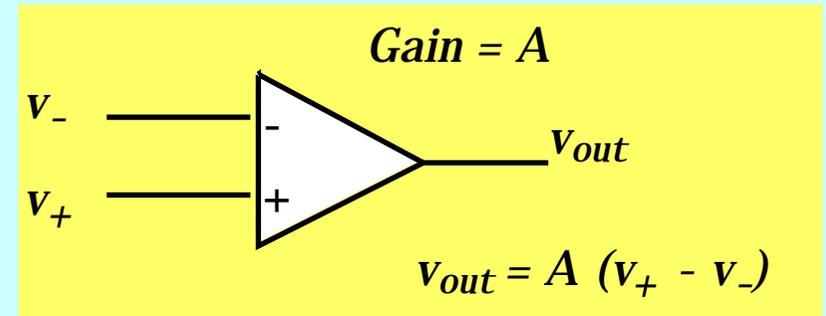

- **Real op-amps almost invariably used with (negative) feedback**

fraction of the output voltage fed back to the inverting input and subtracted from input signal.

open loop gain refers to amplifier gain without feedback

closed loop ... with feedback

- **Rules for calculation - (only hold with negative feedback)**




(i) inputs approach same voltage ($v_+ = v_-$)

(ii) inputs draw no current

only possibility for stability

A quick look inside...

•We may take another look later...

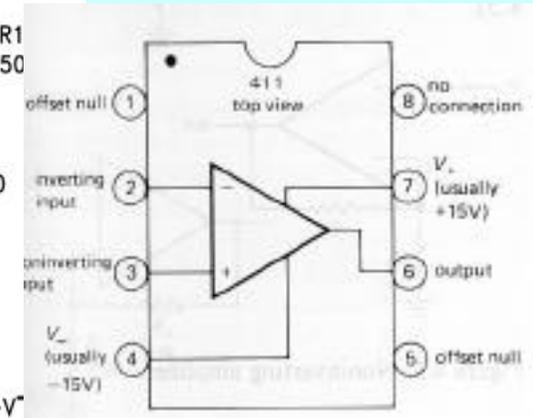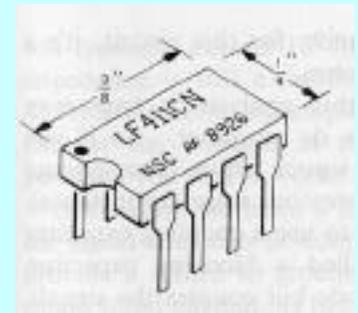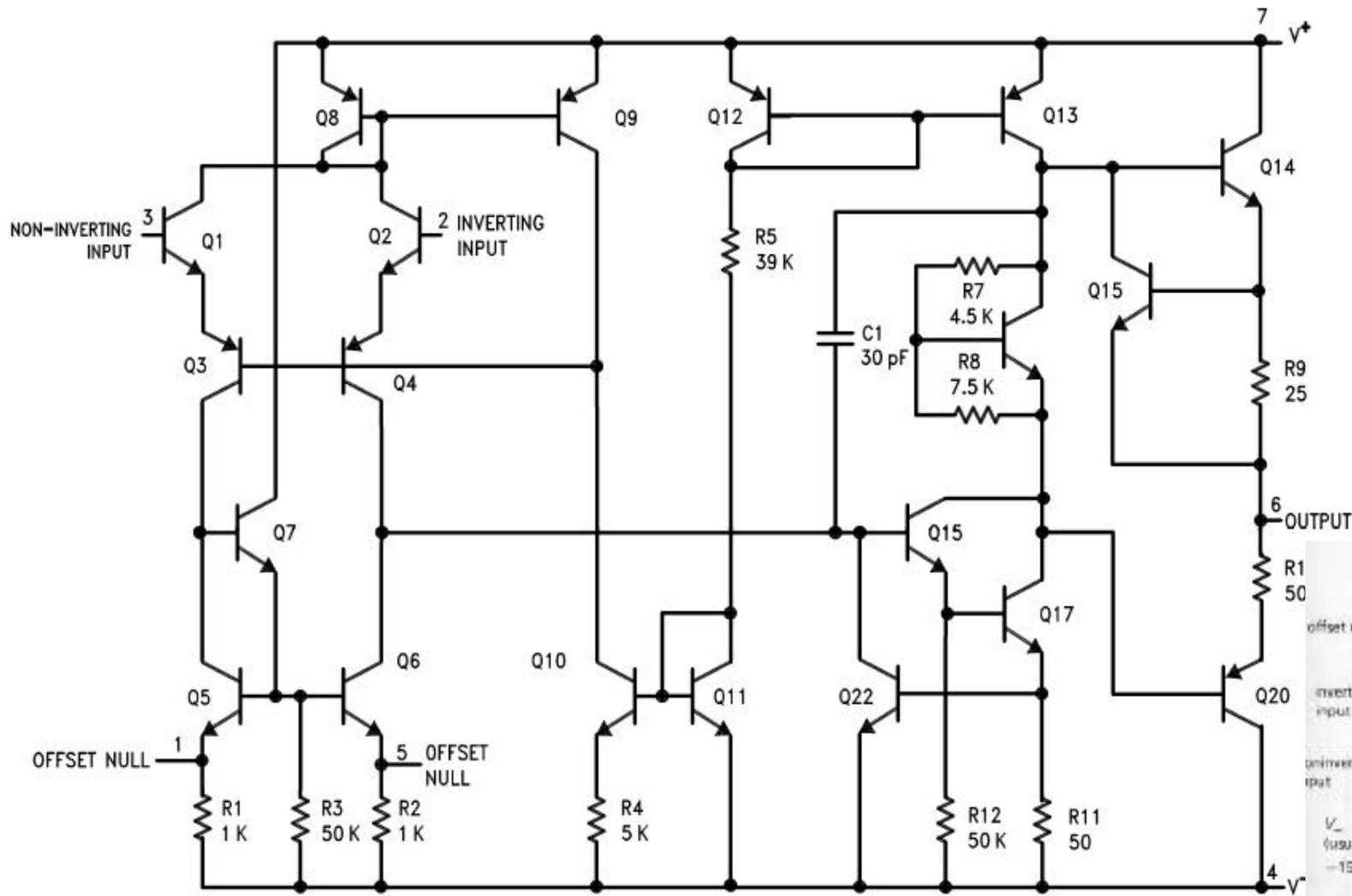

Inverting amplifier


- Apply these rules

$$v_- = v_+ = 0$$

- Consider current flow

$$(v_{in} - v_-)/(v_- - v_{out}) = Z_1/Z_2$$
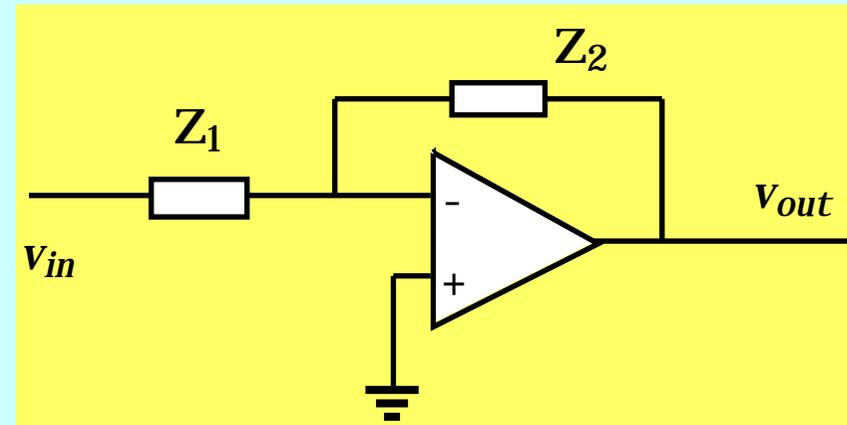
$$\text{Gain}_{\text{closed loop}} = v_{out}/v_{in} = -Z_2/Z_1$$



NB +/- connections

- Inverting input is virtual ground

held at 0V by rule (i)

- Input impedance

source at input sees only Z_1 to ground

so effective input impedance Z_1

usually low if aiming for - sometimes a disadvantage

Some conventions

- will often use upper case characters for DC values

I, V

- use lower case values for perturbations or AC values


$i = I$ or $i = I_0 e^{j t}$

etc

- Symbols

ask if you don't recognise a symbol

For ground:

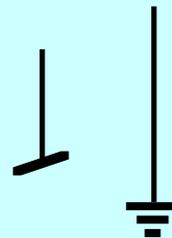

Non-inverting amplifier


- Apply rules

$$V_{in} = V_+ = V_-$$

- Voltage divider in feedback network

$$V_- = V_{out} Z_1 / (Z_1 + Z_2)$$
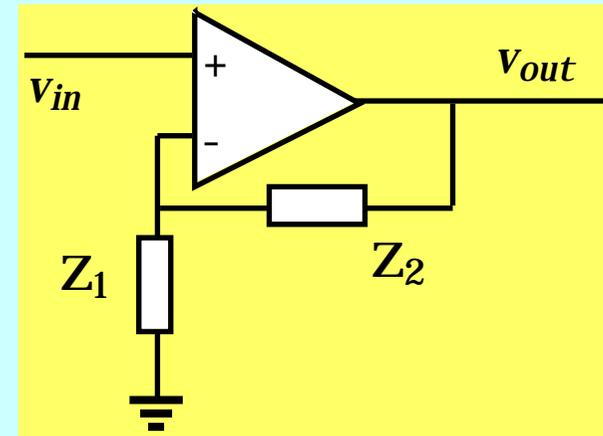
$$\text{Gain}_{\text{closed loop}} = V_{out} / V_{in} = 1 + Z_2 / Z_1$$




NB connections

- Input impedance

source at input sees only input impedance of op-amp input = very high ()
convenient for driving from any source


- Coupling signals in

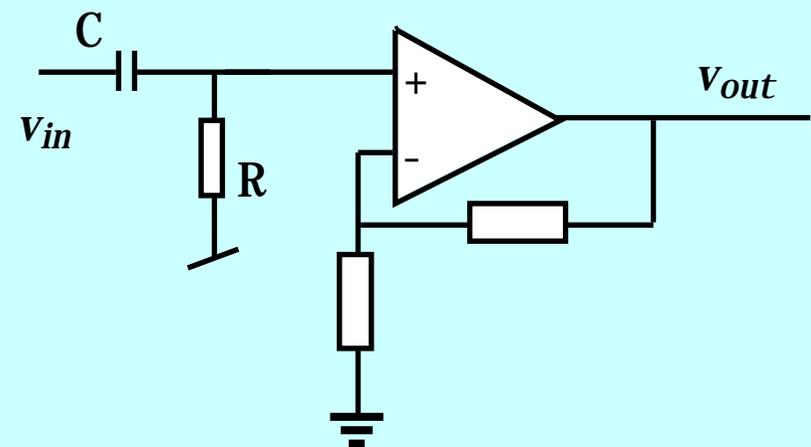real amplifiers do draw small currents
so if input is ac coupled, need a path for
current to flow to ground
make RC >> relevant time constant




Buffers and loading

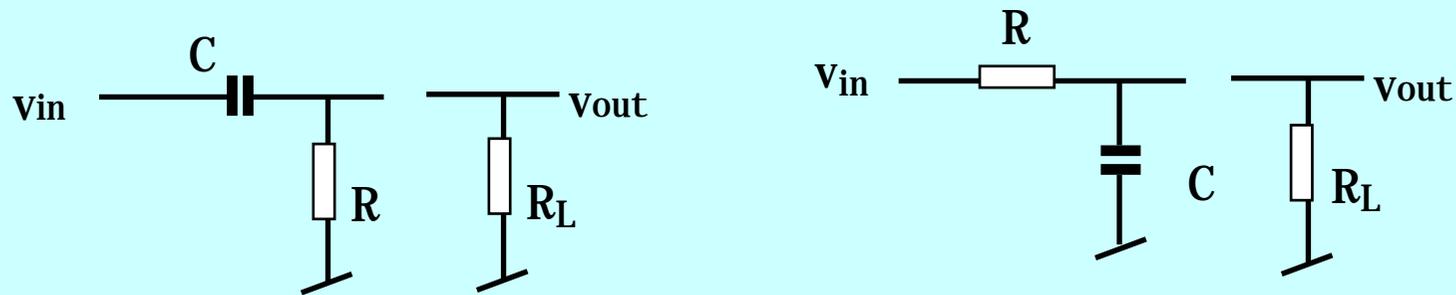- Play an important role in connecting circuit elements or blocks
eg a block may have a high output impedance where a low value is required
or a high input impedance where ... etc
- A load can change the characteristics of the circuit...



to overcome, insert a stage which matches impedances better
ie. isolates one stage from another

eg

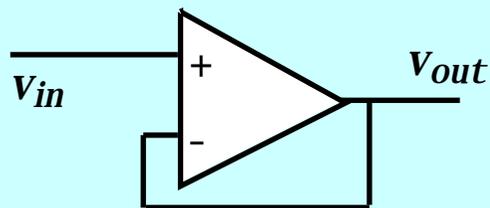

Integrator

- Variant of inverting amplifier where current is integrated on feedback capacitor

$$i_{in} = v_{in}/R$$

$$V_{out} = -(1/RC_f) \int v_{in} dt$$

useful for control circuits

- it will often be convenient to analyse this circuit for pulse processing, where often more convenient to work in frequency domain

$$V_{out} = -i_{in}/j \omega C_f$$



R is noise source and adds to input impedance

remove for charge integrator

$$V_{out} = -Q_{in} / C_f$$

- Must have a means of resetting the amplifier

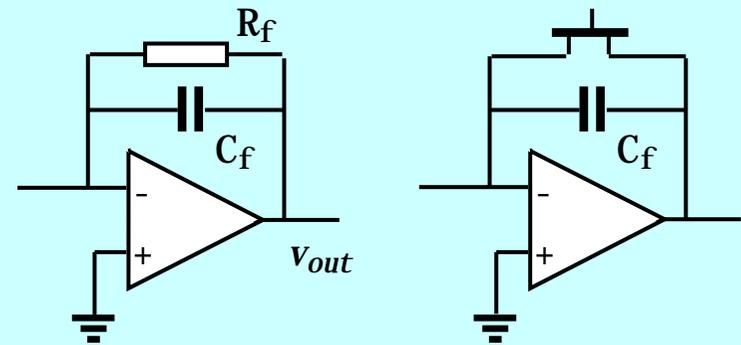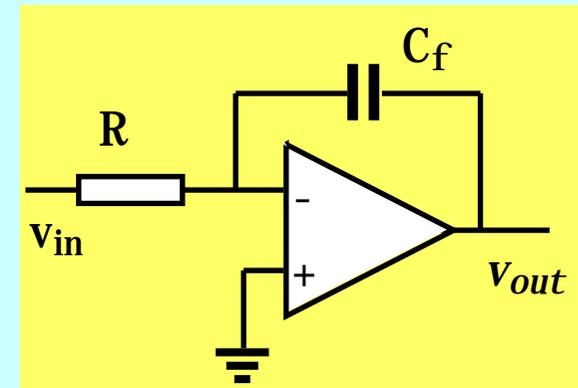provide a parallel resistor or a transistor switch



$R_f C_f \gg$ integration time

Other useful blocks


•Differentiator

$$i = CdV/dt$$

$$v_{out} = -RCdV/dt$$


or

$$v_{out}/v_{in} = -j RC$$

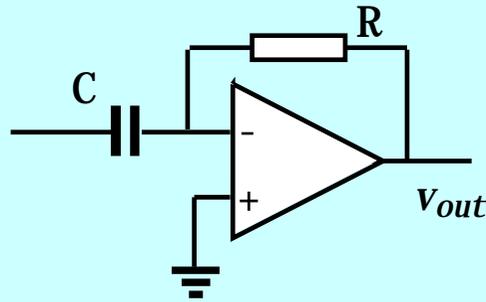

•Summing amplifier

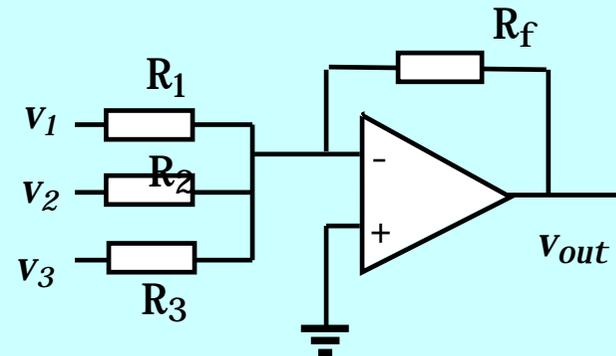weighted sum of inputs
(consider currents)




•Differential amplifier

$$v_{out} = (R_2/R_1)(v_2-v_1)$$

for matching need accurate component values

nice feature: removes common mode signal

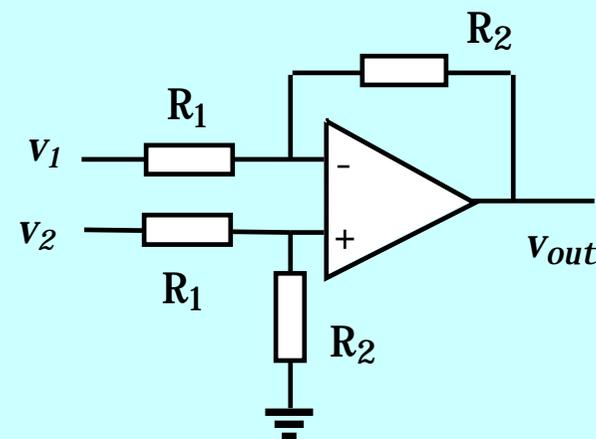

Common mode

- Suppose two signals at differential amplifier input are v_1 & v_2

in many cases they may have a common component

$$\text{ie } v_1 = u_1 + v_{\text{cm}} \quad v_2 = u_2 + v_{\text{cm}}$$

v_{cm} is called the common mode, remainder is normal mode

- The nice feature of a differential amplifier is

$$v_{\text{out}} = G(v_2 - v_1) = G(u_2 - u_1)$$

this is a very effective way of subtracting interference which affects both signals equally

eg power supply ripple

can't be used as universal remedy: lose dynamic range

- Common Mode Rejection Ratio - CMRR


CMRR = differential gain/common mode gain

~ 100-140dB for precision op-amps


Many other possibilities

- Not restricted to using resistors only in circuit

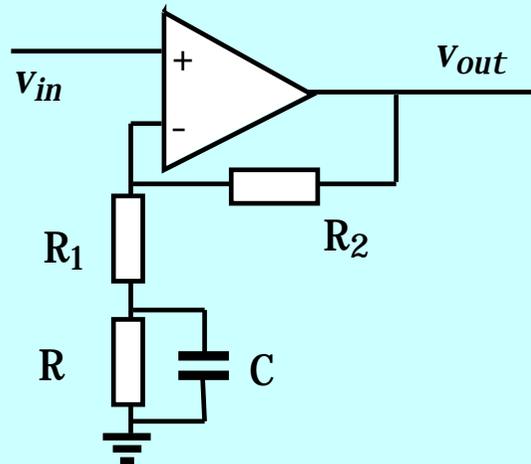eg gain at low f (or DC) with different value at high f



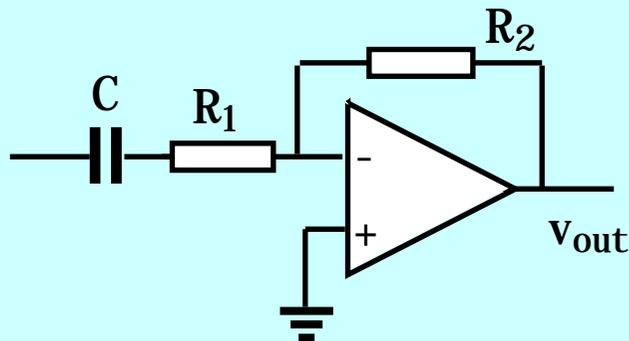differentiator/high pass filter with gain & inversion



Non-ideal op-amp behaviour

- **Just seen one example**

inputs do draw small currents - input impedances are finite
real amplifiers do not have infinite gain but very high values can be obtained
some examples of consequences later

- **Practical considerations**

easy to assume zero output for zero input - may be true for ac, but not dc
op-amps have nulling connections, and recommended compensation to adjust
often simple potentiometer (screwdriver adjustment)

output impedance - ideal op-amp has open-loop $R_{out} = 0$

slew rate - how fast can output voltage change?

applied voltages are limited - certainly can't expect to exceed supply voltages!

behaviour can change with temperature - powered circuits need cooling!

frequency response and bandwidth - discuss further

- **- most parameters are clearly specified so should use manufacturer's data to select best component for application**

many of these are important in precision applications

Specifications & typical values

• Along with obvious parameters; R_{in} , R_{out} , CMRR, V_S , bandwidth, power consumption, gain and phase shift, manufacturer's data sheets also give:

• Input bias current I_B

$$0.5 * (i_+ + i_-) \text{ with } v_+ = v_- = 0 \quad \sim \text{pA} - \text{nA}$$

• Input offset current I_B

$$i_+ - i_- \text{ with } v_+ = v_- = 0 \quad \sim \text{fraction of } I_B$$

• Input offset voltage V_{OS} & adjustment range

$$v_{out} \text{ with } v_+ = v_- = 0 \quad \sim 10\mu\text{V} - 5\text{mV}$$

• Input voltage range

$$\sim \pm |V_S| - 1\text{V}$$


• Slew rate (f dependent)

$$\text{maximum } dv_0/dt \quad \sim V/\mu\text{s}$$


• Power Supply Rejection Ratio (PSRR)

small changes in V_S can resemble signals
dB or $\mu\text{V}/\text{V}$

• Noise voltage & current (for later)





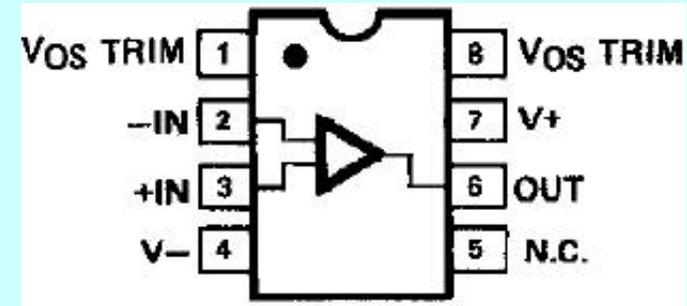


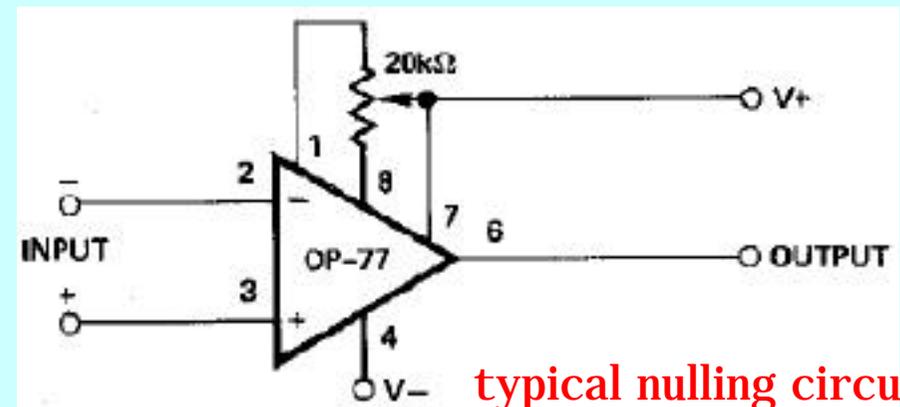NB some of these are T dependent
so take care in assumptions when adjusted



typical nulling circuit

Real op-amp data - OP77

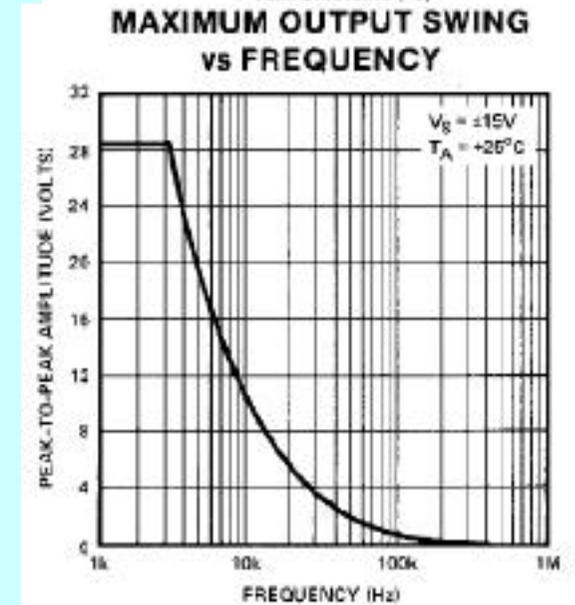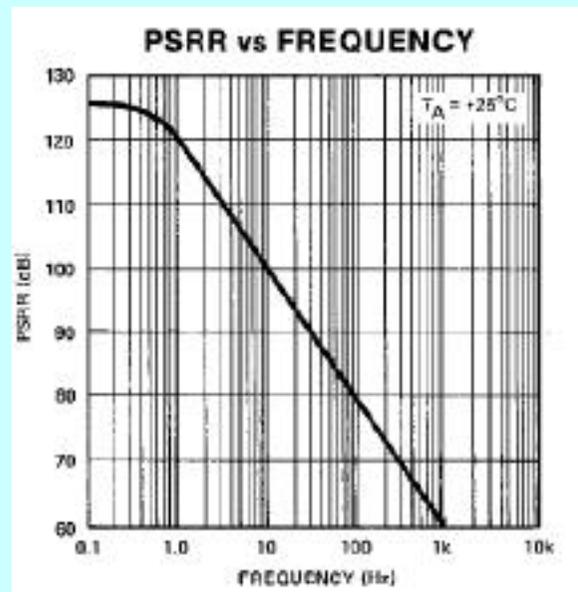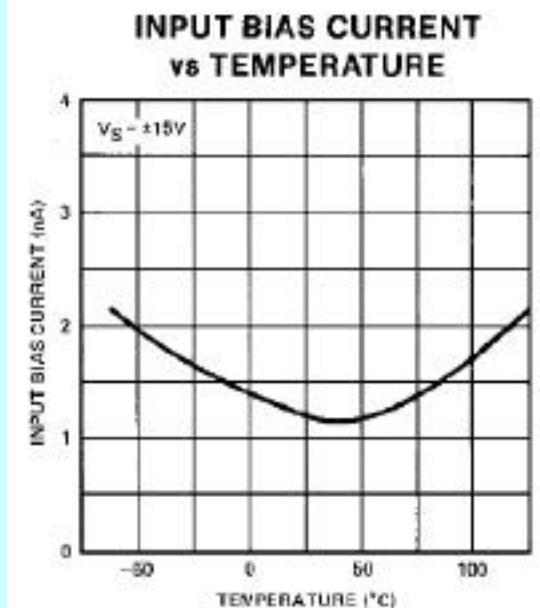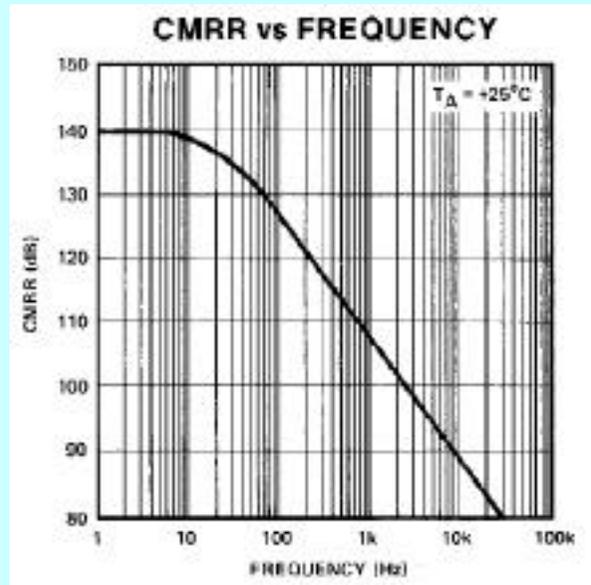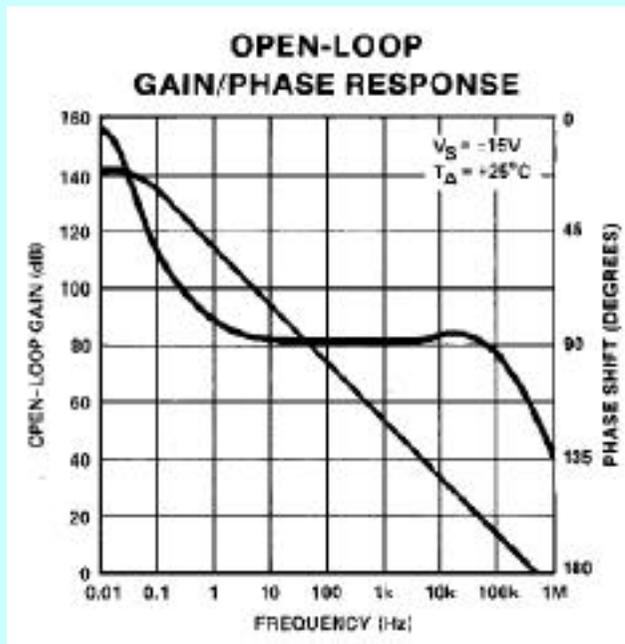

Advantages of feedback

•Why sacrifice gain?

even if amplifier gain is defined

component gain is not a reliable quantity

gain in feedback circuits fixed by components

can choose precision

negative feedback improves performance

stability, linearity, distortion

some components approaching ideal can be designed

eg current sources with very high output impedance

real gain depends on frequency


designing for lower closed loop gain extends f range where gain is uniform

- up to some limit

frequency dependent feedback can be used

simplifies some designs

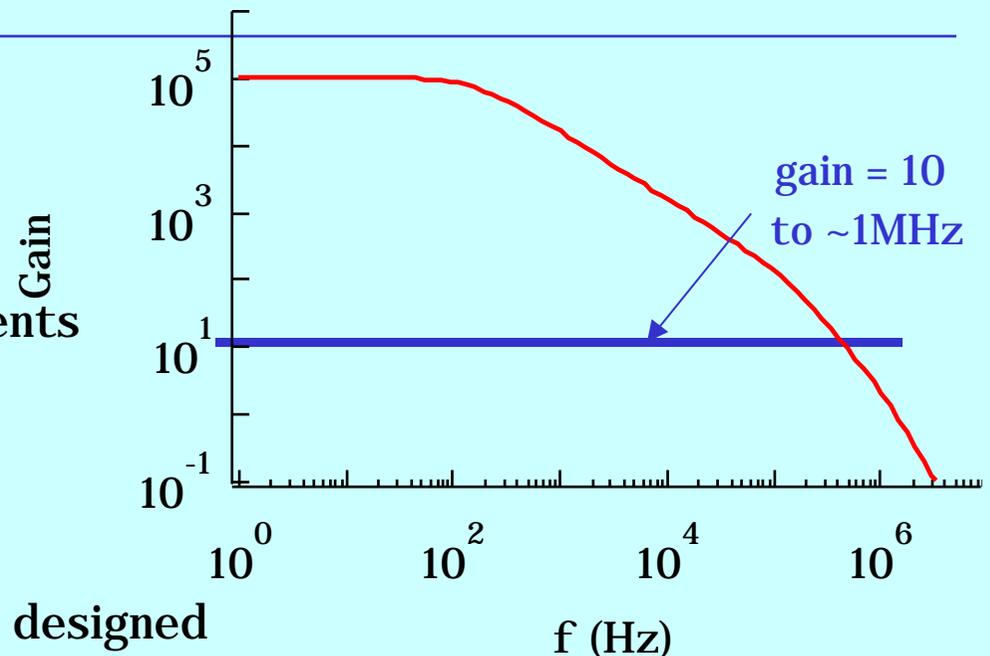positive feedback has uses - eg oscillators



Op-amp frequency response

- Reason for falling gain with frequency

low pass filters in different stages
formed by natural capacitances present
in circuit

- Poles

amplifier illustrated has poles at f_1 , f_2 , f_3

can give stability problems

if phase shift $> 180^\circ$ negative feedback
becomes positive

must ensure gain < 1 at frequency at which
phase shift $> 180^\circ$

some op-amps have this built in
if not, reduce gain

if feedback network introduces phase
changes, then this must be included in
discussion

Gain

(deg)

