

# Amplifiers

---

- This is a large and important part of this course

amplifiers are needed for many instruments

- inescapable in electronic instruments

even if not used to boost signals, amplifiers are the basis of most important functional blocks

- in many circumstances amplification, in the sense of “boosting” signals, is vital

signals to be measured or observed are often small

defined by source - or object being observed

and sensor - it is not usually easy to get large signals

data have to be transferred over long distances without errors

safest with “large” signals

# System block diagrams

- Introduction to...

- Points to note

summing node

output from node = sum of signals entering


note signs at entry

pick-off node

all outgoing signals = incoming signal

functional blocks & directions of signals

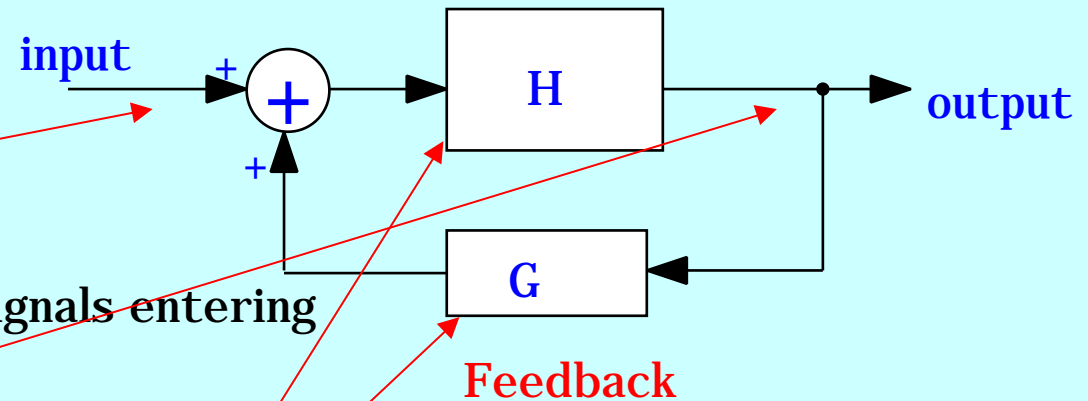usually label with transfer function of block



don't always distinguish summing nodes from others in diagrams - but only if it's very clear

- What kind of system?

electronic - but also mechanical, acoustic, optical,..

- How to manipulate?

label with signals, then follow rules

# Feedback


- After summing node

$$u(t) = x(t) + Gy(t)$$

- At output

$y(t)$ , but also  $Hu(t)$

$$\text{so } y(t) = H[x(t) + Gy(t)]$$

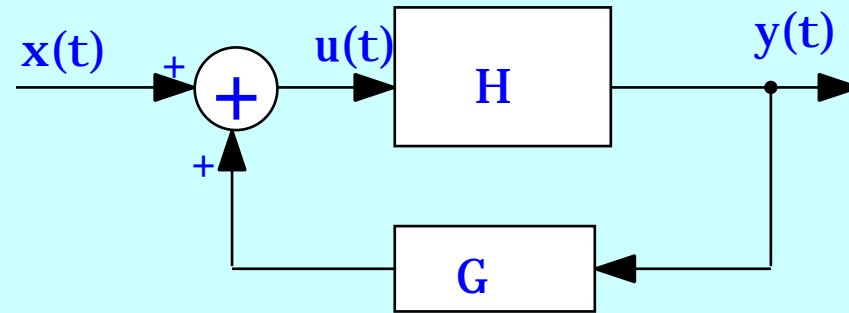

$$H_{\text{system}} = y(t)/x(t) = H/(1 - GH)$$

- Why is this useful?

suppose  $H \gg 1$  then  $H_{\text{system}} = -1/G$  ie. system transfer function independent of H

eg  $0 < G < 1$  system provides constant amplification

$G$  = feedback fraction

- Problems -

perhaps  $G \rightarrow 1/H$   $H_{\text{system}} \Rightarrow$  unstable - positive feedback

system will always be stable with negative feedback

- Applications...

# Operational amplifier

---

- **A good starting point for analogue electronics**

will later consider devices and components used to build real amplifiers but the op-amp is a convenient idealisation

- **building block**

much electronics consists in recognising building blocks which perform specific functions

*a large circuit can appear quite complex but can often be reduced to much simpler functional elements*

- **First questions to ask in analysing amplifying system**

what quantity is being amplified? - eg. current, charge or voltage

what type of signals? eg. fast pulses or slow waveforms?

what is the input and output impedance? ie how should it be connected?

what is the gain?

- **some more detailed information...**

frequency response, linearity, noise level, ...

# Operational amplifier approximation

- **very high gain voltage amplifier**

gain =  $A$  ->


infinite bandwidth

single output

dual, differential inputs, infinite impedance

**amplifies difference in voltages between inputs**

*inputs are DC coupled*

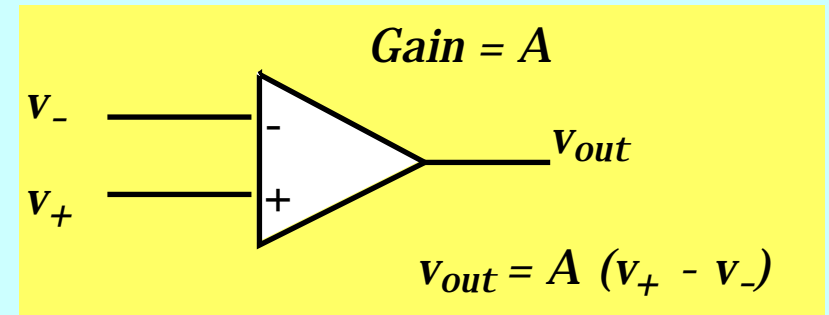

- **Real op-amps almost invariably used with (negative) feedback**

fraction of the output voltage fed back to the inverting input and subtracted from input signal.

*open loop gain refers to amplifier gain without feedback*

*closed loop ... with feedback*

- **Rules for calculation - (only hold with negative feedback)**




(i) inputs approach same voltage ( $v_+ = v_-$ )

(ii) inputs draw no current

only possibility for stability

# A quick look inside...

•We may take another look later...

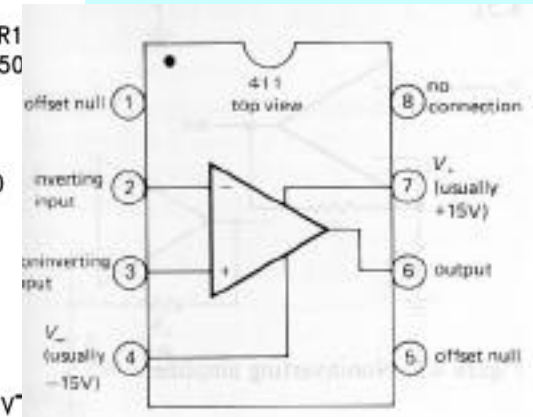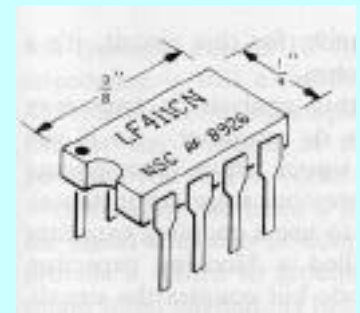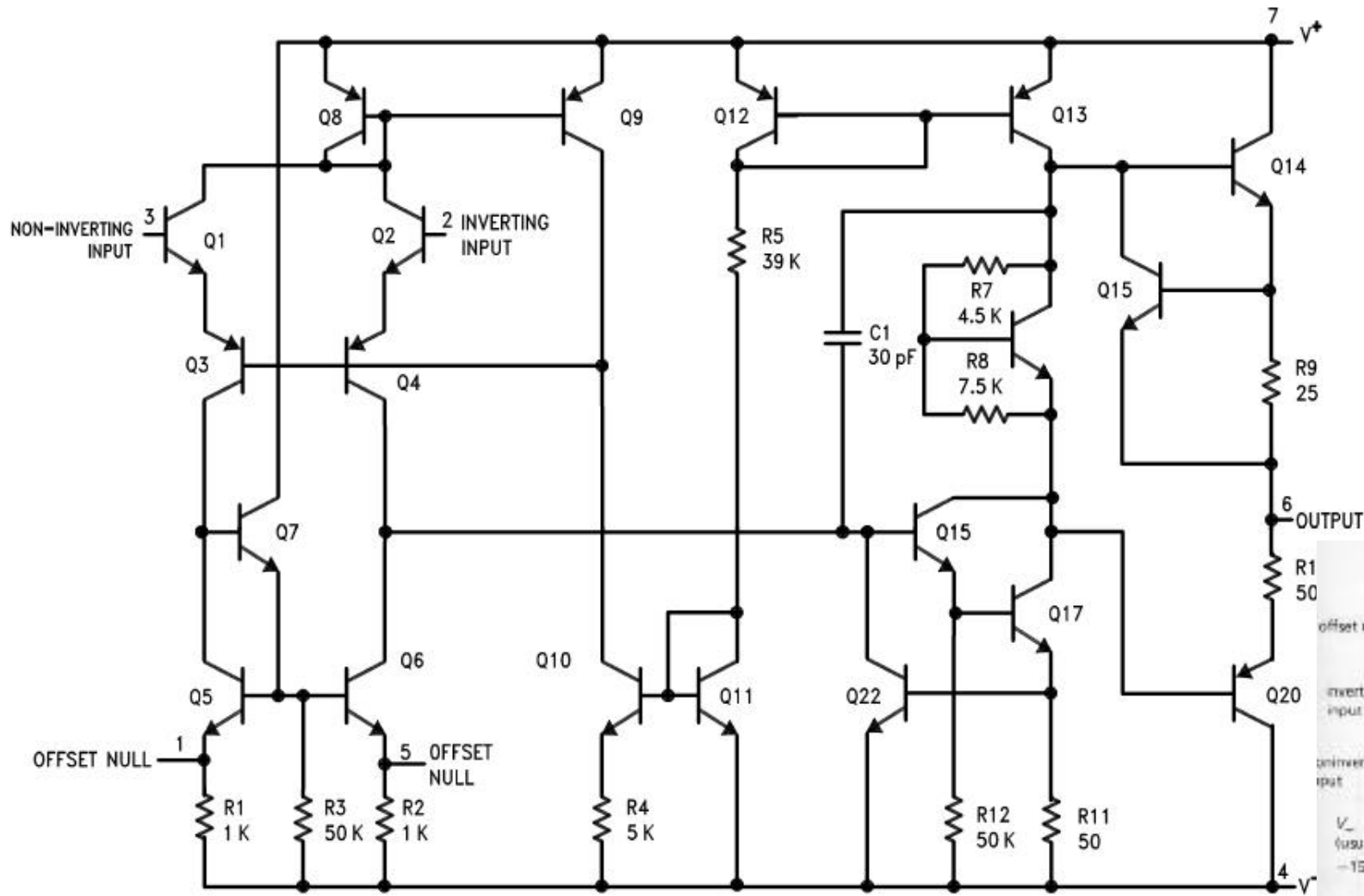

# Inverting amplifier


- Apply these rules

$$v_- = v_+ = 0$$

- Consider current flow

$$(v_{in} - v_-)/(v_- - v_{out}) = Z_1/Z_2$$
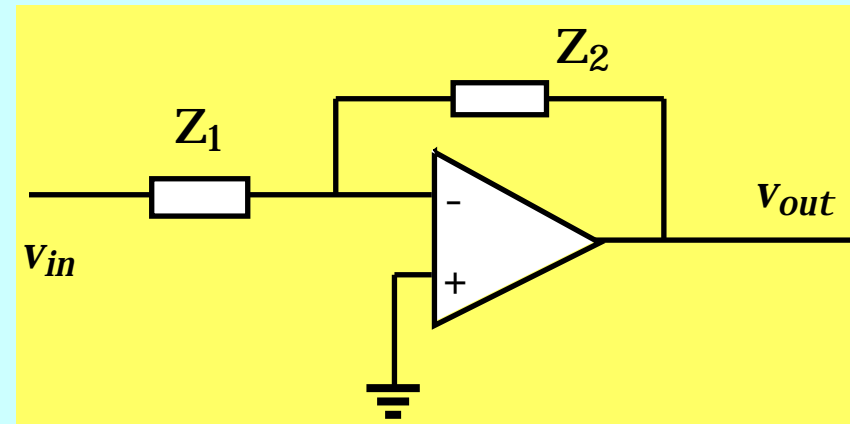
$$\text{Gain}_{\text{closed loop}} = v_{out}/v_{in} = -Z_2/Z_1$$



NB +/- connections

- Inverting input is virtual ground

held at 0V by rule (i)

- Input impedance

source at input sees only  $Z_1$  to ground

so effective input impedance  $Z_1$

usually low if aiming for - sometimes a disadvantage

# Some conventions

---

- will often use upper case characters for DC values

I, V

- use lower case values for perturbations or AC values


$i = I$  or  $i = I_0 e^{j t}$

etc

- Symbols

ask if you don't recognise a symbol

For ground:

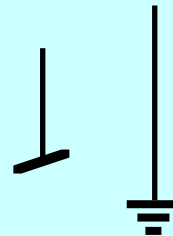



# Non-inverting amplifier


- Apply rules

$$V_{in} = V_+ = V_-$$

- Voltage divider in feedback network

$$V_- = V_{out} Z_1 / (Z_1 + Z_2)$$
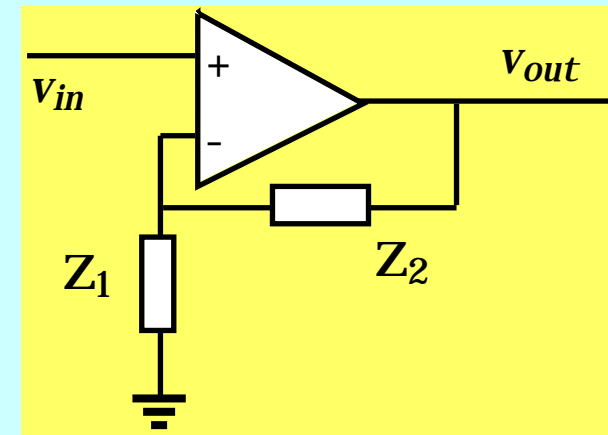
$$\text{Gain}_{\text{closed loop}} = V_{out} / V_{in} = 1 + Z_2 / Z_1$$




NB connections

- Input impedance

source at input sees only input impedance of op-amp input = very high ( )  
*convenient for driving from any source*


- Coupling signals in

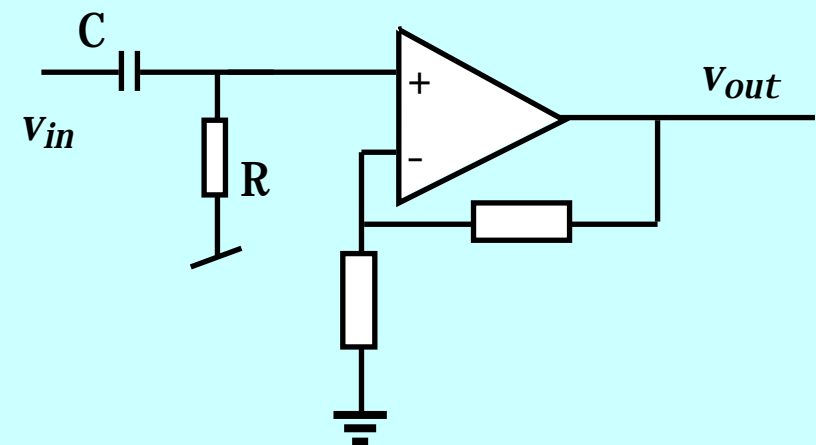real amplifiers do draw small currents  
so if input is ac coupled, need a path for  
current to flow to ground  
*make  $RC \gg$  relevant time constant*



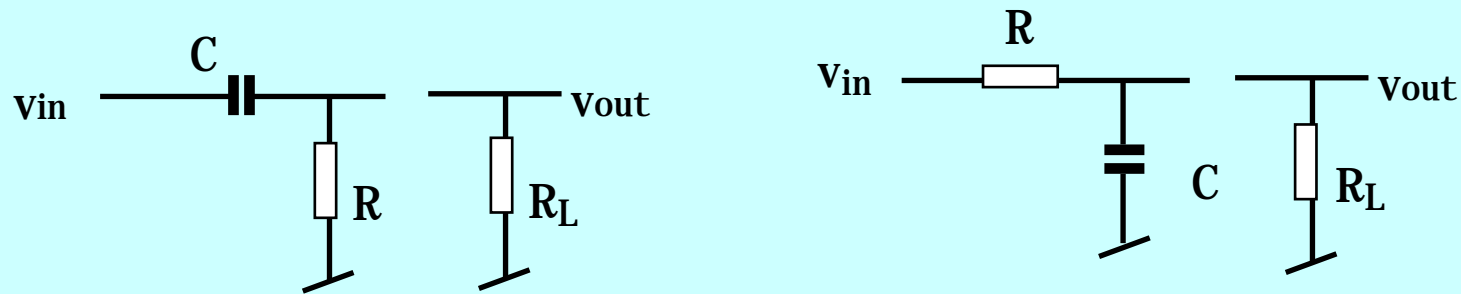
# Buffers and loading

- Play an important role in connecting circuit elements or blocks  
eg a block may have a high output impedance where a low value is required  
or a high input impedance where ... etc
- A load can change the characteristics of the circuit...



to overcome, insert a stage which matches impedances better  
ie. isolates one stage from another

eg

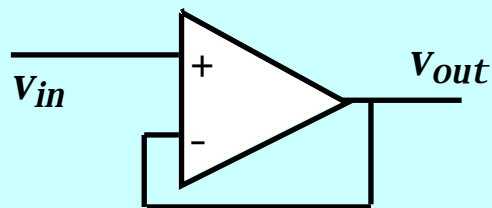

# Integrator

- Variant of inverting amplifier where current is integrated on feedback capacitor

$$i_{in} = v_{in}/R$$

$$V_{out} = -(1/RC_f) \int v_{in} dt$$

*useful for control circuits*

- it will often be convenient to analyse this circuit for pulse processing, where often more convenient to work in frequency domain

$$V_{out} = -i_{in}/j \omega C_f$$



R is noise source and adds to input impedance

*remove for charge integrator*

$$V_{out} = -Q_{in} / C_f$$

- Must have a means of resetting the amplifier

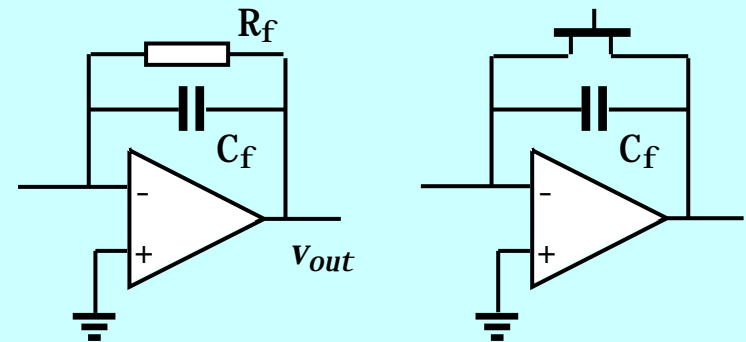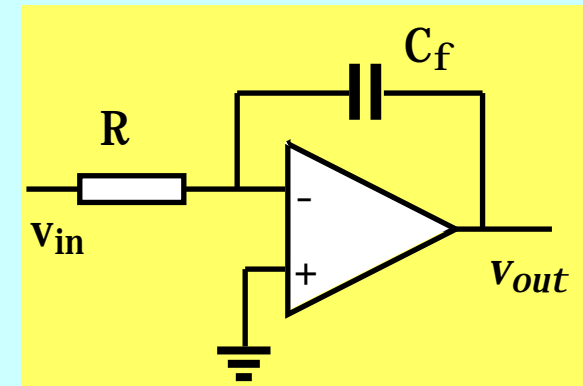provide a parallel resistor or a transistor switch



$R_f C_f \gg$  integration time

# Other useful blocks


## •Differentiator

$$i = CdV/dt$$

$$v_{out} = -RCdV/dt$$


or

$$v_{out}/v_{in} = -j RC$$

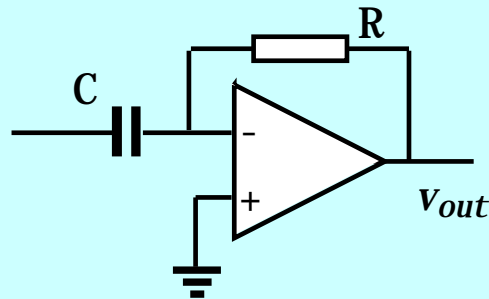
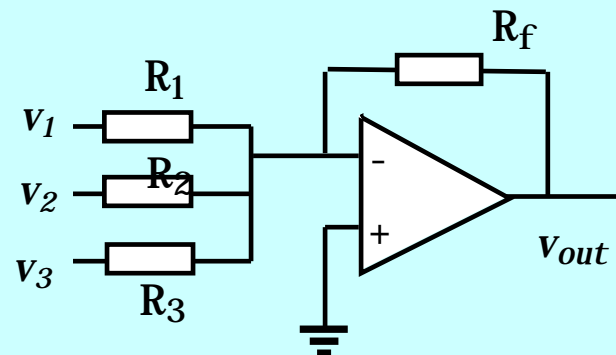
## •Summing amplifier

weighted sum of inputs  
(consider currents)



## •Differential amplifier

$$v_{out} = (R_2/R_1)(v_2 - v_1)$$

for matching need accurate component values

nice feature: removes common mode signal

