

Transistor electronic technologies

- **Bipolar Junction Transistor**

discrete or integrated circuit

discrete = individual component

- **MOS (Metal-Oxide-Silicon) Field Effect Transistor**

mainly used in integrated circuits

driven by digital applications but analogue


- **Junction Field Effect Transistor**

similar in many ways to MOS FET

discrete, not easily implemented in ICs

- **so - is this a course on circuits?**

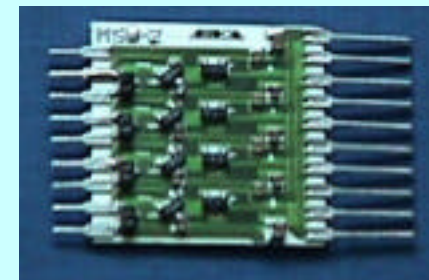No but it is necessary to understand some basics to be able to deal with more complex elements, including some features of op-amps



Bipolar transistor

- **pnp or npn**

semiconductor, usually Si, but also Ge
 heavily doped emitter, lightly doped base

- **Operation - npn**

base is biased more positive than emitter
so a forward biased diode

collector more positive than base = *reverse biased diode*

majority carriers from emitter diffuse across base to collector

small fraction combine with majority carriers in base

current reaching collector is

$$I_C = \beta I_B$$


$$I_B = (1 - \beta) I_E$$

$$I_C = \beta I_B = [\beta / (1 - \beta)] I_B$$


$$= \beta / (1 - \beta) = \text{d.c current gain} = h_{fe}$$

$$I_E \approx I_C$$

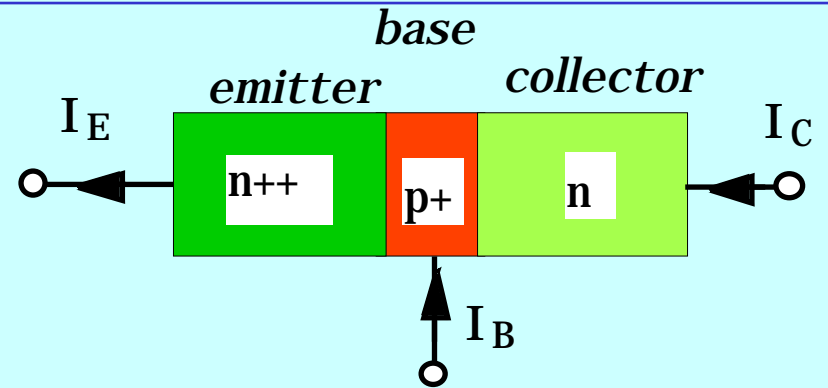eg $\beta = 0.99 \Rightarrow h_{fe} = 99$



arrows show direction of current flow

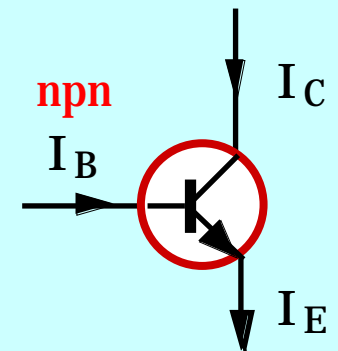

pnp transistor


- Works like npn transistor

bias arrangements different

but

if emitter is positioned at top

easy to remember both pnp and npn

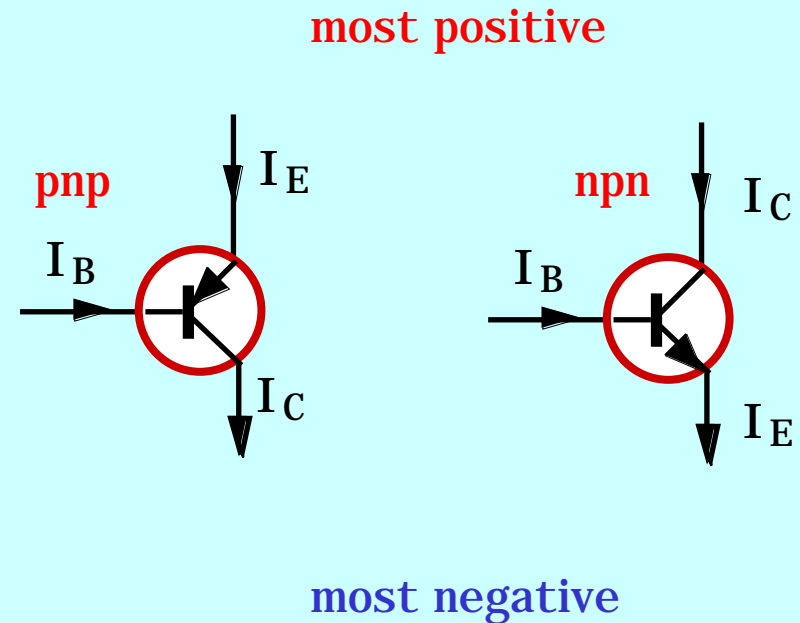

Slightly more precise picture

- to turn npn transistor on $V_B - V_E = V_{BE} > 0.6-0.7V$
(invert for pnp)

- so we can use it as a switch by controlling V_{BE}


$$V_{BE} = 0 \quad I_C = I_E = 0$$

- however, if transistor is ON $V_{BE} \approx 0.7V$


this is a consequence of the diode behaviour -
discuss in a moment

- in contrast, V_{BE} is not a reliable parameter for design

NB both
log scales

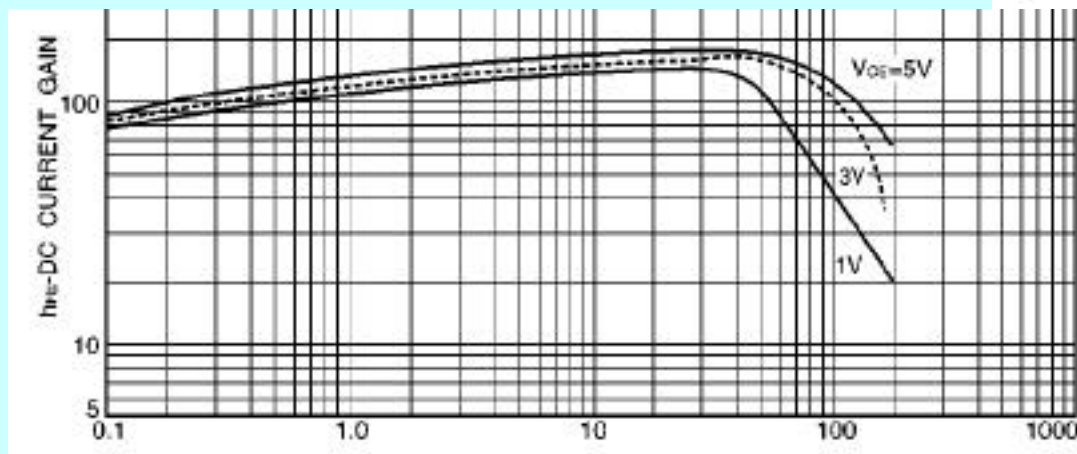

2n3906 npn transistor

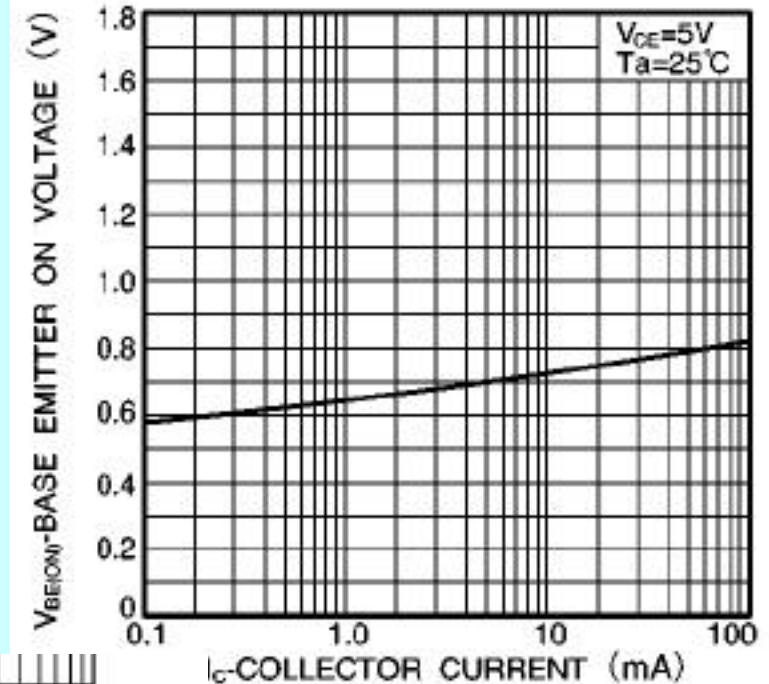

NB log scale for I_C

Ebers- Moll model

- Transistor can be modelled as two back-to-back diodes

I-V behaviour of diode $I = I_0[\exp(qV_{BE}/kT)-1]$

- Base-emitter diode is forward biased

$$I_E = I_{E0} \cdot [\exp(qV_{BE}/kT)-1] \approx I_{E0} \exp(qV_{BE}/kT) \quad \text{ie } V_{BE} = (kT/q) \log_e I_E$$

this explains why V_{BE} varies so little with I
also basis of band-gap T reference

- Base-collector diode is reverse biased

$$I_{BC} = I_{C0} [\exp(qV_{BC}/kT)-1] \approx I_{C0} \quad \text{which is small}$$

so current arriving at collector is dominated by current from emitter, which has diffused across base

- How does current vary with small change in V_{BE} ?

$$dI_E/dV_{BE} = i_e/v_{be} = (q/kT)I_{E0} \exp(qV_{BE}/kT) = (q/kT)I_E$$

$$i_e r_e = v_{be} \quad \text{with } r_e = kT/qI = 25 / I_E (\text{mA})$$

NB we don't usually need to distinguish between I_C and I_E - consider them equal

ie to ac current signals transistor looks like dynamic resistance

Emitter-follower

- **DC conditions** $\pm 6V$ are example values, but results don't depend on them at all

apply our rule that $V_{BE} = 0.7V$

$$I_E = [V_E - (-6V)]/R_E = (V_B + 5.3V)/R_E$$

- **Now ac behaviour**

$$v_{in} = v_b = V_B = (V_E + 0.7V) = v_e = v_{out}$$

amplifier with gain = 1 - not very interesting!!??

- **Input impedance**

$$R_{in} = v_{in}/i_{in}$$


$$i_{in} = i_b = i_c/$$

$$i_c = i_e = v_e/R_E$$

$$R_{in} = R_E \text{ high, eg } \sim 100, R_E \sim 1k$$

(more careful treatment $\Rightarrow R_{in} = (R_E + r_e)$)

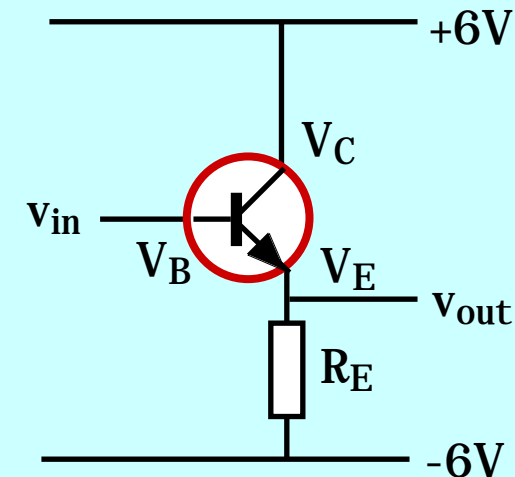this is promising for a voltage buffer - what is the output impedance?



Emitter-follower output impedance

- How to find it? Consider the black box...

vary v_{out} and see what happens to i_{out}

keep other conditions fixed

- Use Ebers-Moll result $V_{BE} = (kT/q)\log_e I_E$

$$dV_{BE}/dI_E = v_{be}/i_e = (kT/qI_E)$$



- If V_B is constant

$$V_{out} = V_e$$

$$i_{out} = i_e$$

$$Z_{out} = (kT/qI_E) = r_e = 25 / I_E(\text{mA})$$

small, as required for buffer

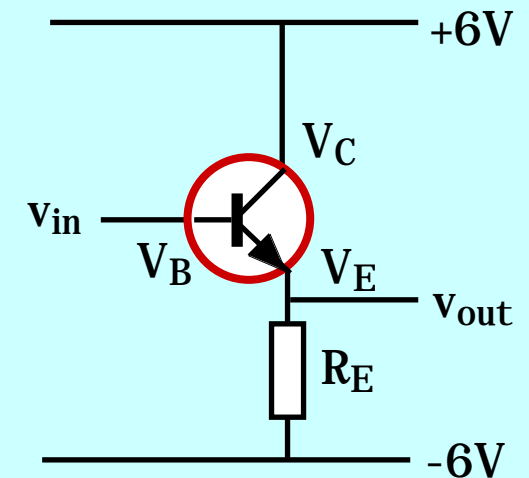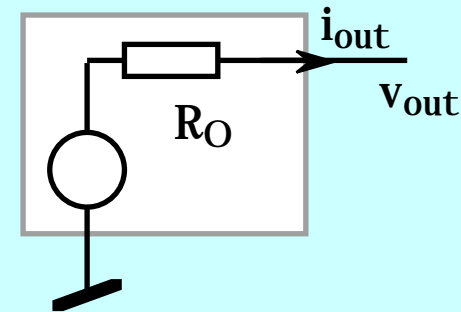

Short footnotes

- In analysing circuits for small signal (AC) behaviour

all fixed DC levels are equivalent to ground

ie ac current does not need to distinguish voltage at other end of path

- This is often useful in looking at circuits to tell if routes are in parallel

- Calculations

keep simple

try to make approximations - 1% answers are almost never required

if so better tools exist

eg parallel resistances

transistor - assume 100 - unless better value known or is critical

47 51 50

Common-emitter amplifier

- **DC conditions** $\pm 6V$ are example values again

$$V_C = 6V - I_C R_C$$

$$V_E = -6V + I_E R_E$$

Since $V_E = V_B - 0.7V$, I_E & I_C defined by bias network

- **small signal, AC behaviour**

$$v_e = v_b = v_{in} = i_e R_E$$


$$v_{out} = -i_c R_C$$

$$\text{so } v_{out}/v_{in} = -R_C/R_E$$

amplifier with gain

- **Input impedance: signal sees bias network in parallel with transistor**

$$\text{so } R_{in} = R_1 || R_2 || (R_E + r_e) \quad - \text{ typically a high value}$$

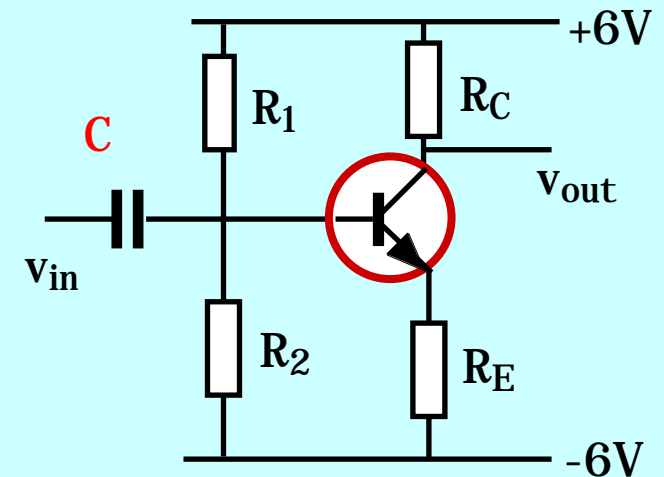

what's the purpose of C?

Common-emitter output impedance

- Play same trick as emitter-follower

but this time, from output terminal, the two paths for i_{out} are


collector-base junction

reverse biased diode = high impedance

R_C

usually much lower than r_{cb}

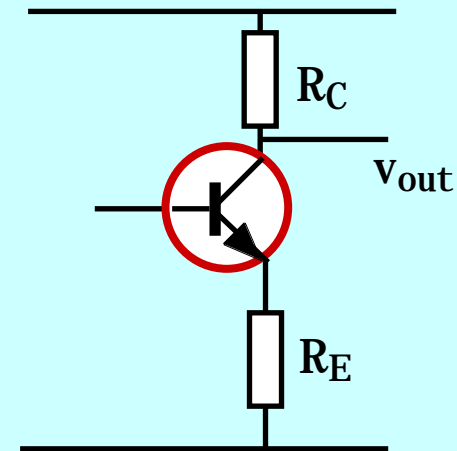no need to worry about any source impedance driving amplifier



so $Z_{out} \approx R_C$

usually relatively high

Reading circuits

- look for the building blocks

usually blocks are "vertical columns"

- look for feedback paths

horizontal paths, which are not DC bias, or output-input

