

Instrumentation Problem Sheet 1

- (1) (i) Find the Thevenin equivalent circuit for a voltage divider made of two resistors R_1 and R_2 driven by a voltage V , with the output voltage taken across R_1 .
 (ii) Find the Norton equivalent of the same circuit.
- (2) (i) Verify that when a load impedance R_{load} is connected to a voltage source with impedance R_{source} , the power in the load is maximised when $R_{source} = R_{load}$.
 (ii) Show that the matching condition that $R_{source} = R_{load}$ holds also for a current source when maximum power is to be transferred to the load.
- (3) What is the Thevenin equivalent of (i) a high pass filter and, (ii) a low pass filter?
- (4) What is the 3dB frequency of (i) a high pass filter with $RC = \tau$, (ii) a low pass filter with the same time constant? What are the numerical values for $\tau = 1\mu s$, $\tau = 20ms$?
- (5) A student decides to construct a band-pass filter by connecting the output of a low pass filter to the input of a high pass filter. Why would this not work as intended?
- (6) A step pulse of amplitude 1V is passed through a low pass filter with a time constant of 50ns. Sketch the pulse shape for a step pulse duration is 100ns, 200ns, 500ns.
- (7) What is the 10-90% rise time of a step pulse passed through a low pass filter with time constant τ ?
- (8) An optical fibre telephone cable has an attenuation of 2.5dB/km at $\lambda = 850nm$ and 0.8dB/km at $\lambda = 1300nm$. Signals of both wavelengths with equal initial power are launched into the fibre. What is the relative power of the two signals in dB after 100km?
- (9) The precision of an energy measurement is often quoted in terms of ΔE , where ΔE is the Full Width at Half Maximum (FWHM) of the resolution function, which is usually assumed, or measured, to be a gaussian distribution. Show that in this case ΔE is related to the standard deviation by $\Delta E = 2.35 \sigma$.

As a reminder: the gaussian probability distribution whose mean is E_0 and variance is σ^2 is given by

$$p(E) = (1/2\pi\sigma^2)^{1/2} \cdot \exp[-(E-E_0)^2/2\sigma^2]$$

- (10) The splitter in the figure is designed to connect a radio aerial to two cables connected to radios. All the cables and loads are transmission lines with $R = 75 \Omega$. What value should be chosen for r so that no matter what direction the system is viewed from, a load of 75Ω is seen?

