

Instrumentation Problem Sheet 6

(1) A delay element for digital pulses can be constructed using RC circuit and comparator. Devise a way to do this. A clock waveform (ie square digital pulses with equal ON and OFF times) has a period $4T$. Using a delay element which produces a delay T , show that the XOR'ed output of the clock and delayed clock produces another clock waveform. What is its period?

(2) Satisfy yourself that the following logic identities are true:

[notation is $A' = \text{Not}A$, $+$ = OR, x = AND, $AxB = AB$]

$$A(B+C) = AB + AC$$

$$A + AB = A$$

$$A + BC = (A+B)(A+C)$$


$$AA' = 0$$

and DeMorgan's theorems:

$$(A+B)' = A'.B' \quad \text{and} \quad (AB)' = A' + B'$$

(remember these are logic levels, or binary numbers).

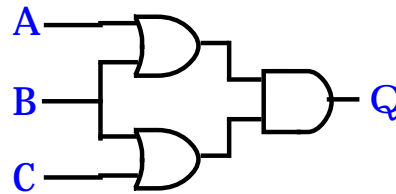(3) Find the truth table for the logic diagram illustrated.



(4) Design a 3-bit Gray-to-binary decoder using 2 XOR gates. (Hint: start with the two high order bits. The lowest bit needs the result of the higher binary digit.) Show that this is easily extended to 4-bits (and beyond) by duplicating the lowest order bit logic.

(5) Use the Laplace transform to find a solution to the differential equation


$$x'' - a^2x = f(t)$$

(6) Two identical amplifiers with impulse response $f(t) = te^{-t}$ in the time domain are connected in series.

- a) What is the transfer function of a single amplifier in isolation ?
- b) What is the transfer function of the two amplifiers in series ?
- c) Using partial fractions find the time domain output of the two amplifiers in series for a step function input $x(t) = u(t)$ at a time $t=0$.

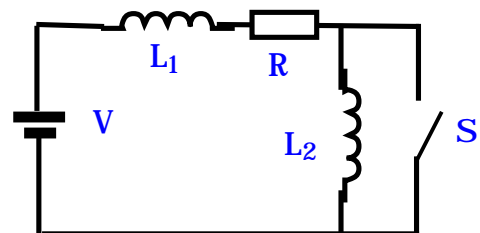(7) A circuit containing a resistor and two inductors is constructed as shown.

Initially the switch S is closed (shorting out inductor L_2). The switch is opened at a time $t=0$, increasing the effective inductance of the circuit from L_1 to $(L_1 + L_2)$.




- a) Write down a simple expression for the steady state current that flows through the circuit at a time $t < 0$ before the opening of the switch.
- b) Write down a simple expression for the steady state current in the limit t after the opening of the switch.
- c) Write down a differential equation relating the current and voltage in the circuit for times $t > 0$. Use the Laplace transform to solve this equation and derive an expression for the time domain behaviour for all times $t > 0$.

(8) The inductance L_2 of the previous problem is replaced with a capacitor C . Show that the current flowing for $t > 0$ can be written as

$$i(t) = (V/L)[Ae^{at} + Be^{bt}] + C$$


$L = L_1$. What are the values of A , B , C , a and b ? Is the system stable?

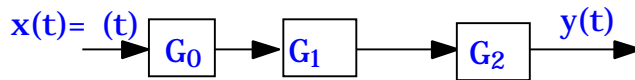(9) Use the Laplace transform and partial fractions to find the system impulse response of the system in the figure.



G_0 is a unity gain integrator, G_1 is a high pass filter with $\omega_1 = 1/2$, and G_2 is a low pass filter with $\omega_2 = 1/3$.

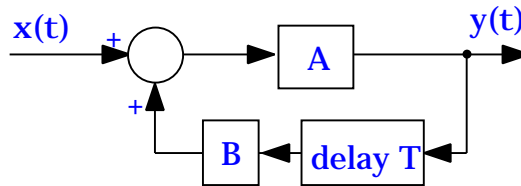(10) The system in the figure represents an audio system where $x(t)$ is the input at the microphone and $y(t)$ is the output at the loudspeakers. A represents amplification following the microphone.



The feedback path represents a signal returned to the input as a consequence of the microphone sensing the sound from the speakers. B is an attenuation factor and there is also a delay. Write down an equation to represent the system response in the time domain. Derive the corresponding equation in the s -domain using the time shift property of the Laplace transform. Hence show under what conditions stability can be guaranteed.

(11) Find the z -transform of the filter which has an impulse response $(t/n) \exp(-t/n)$. Hence find the inverting filter which is needed to recover an impulse, and the weights which should be applied to consecutive samples. (There should be just 3).