

# Noise and electronics for semiconductor detectors

---

A big subject but restrict to very essential information only

Some slides will be skipped and are there only to provide supplementary details for those wishing to seek further information.


Key point: Semiconductors need amplifiers since they usually do not have any built-in amplification

hence some understanding of amplifiers is required when considering how to build detector systems

if you are prepared to accept the noise is what it is, then it may be enough for working with data from such systems just to be aware that noise is present and it probably cannot be improved, although it might be worsened!
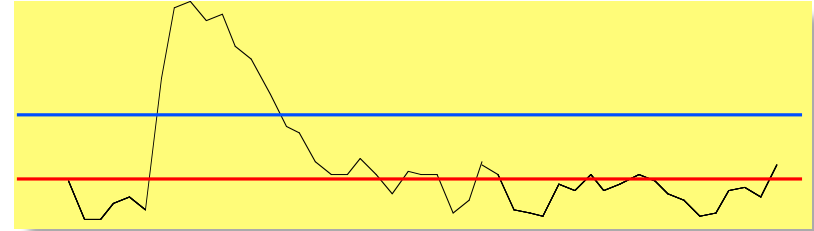
# Noise

- What is NOISE? A definition:  
Any unwanted signal obscuring signal to be observed  
two main origins




- EXTRINSIC NOISE                    examples...  
pickup from external sources    unwanted feedback  
RF interference from system or elsewhere, power supply fluctuations  
ground currents  
small voltage differences => currents    can couple into system


may be hard to distinguish from genuine signals                    *but* AVOIDABLE  
Assembly & connections, especially to ground, are important

- INTRINSIC NOISE  
Fundamental property of detector or amplifying electronics  
Can't be eliminated but can be MINIMISED

# Noise in amplifier systems

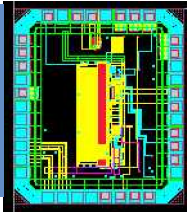

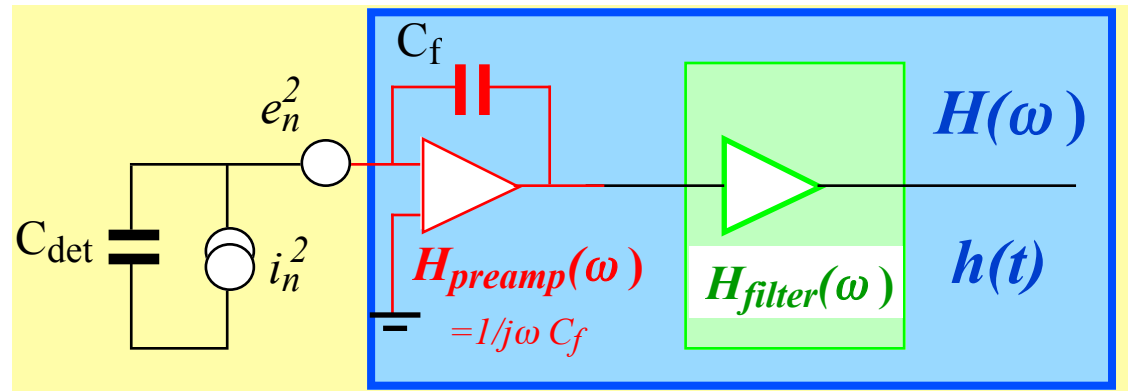- VFE systems comprise
  - preamplifier - with noise sources
  - shaping amplifier or other filter



- Preamplifier usually designed with noise as an important consideration
  - preamplifier pulse shape is long duration with short, sharp peak
  - so modify it with shaper to
    - optimise signal to noise
    - generate a more practical pulse shape, avoiding pile-up
  - **the first (pre-) amplifier is the most important part of the system for noise**
- The system noise can be calculated once sources are understood
  - relies on Campbell's theorem and summation over bandwidth


# Preamplifier types

Omit most – just be aware that different amplifier types have different noise properties and are not interchangeable

- Current sensitive - common for photodiode signals

$$V_{out} \approx -i_{in} R_f$$

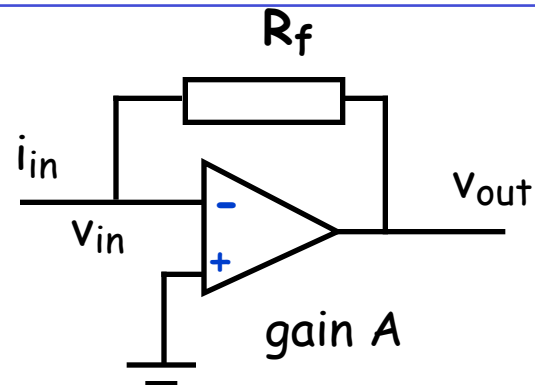- signals follow input current, ie fast response but not lowest noise



- Charge sensitive amplifier



Ideally, simple integrator with  $C_f$   
but need means to discharge capacitor  
- large  $R_f$

- Simple integrator


$$V_{out} \approx -Q/C_f$$

- with feedback resistor  $R_f$

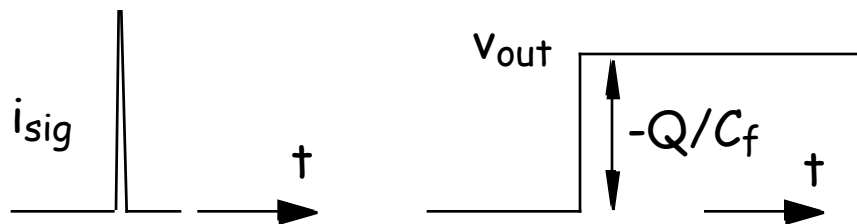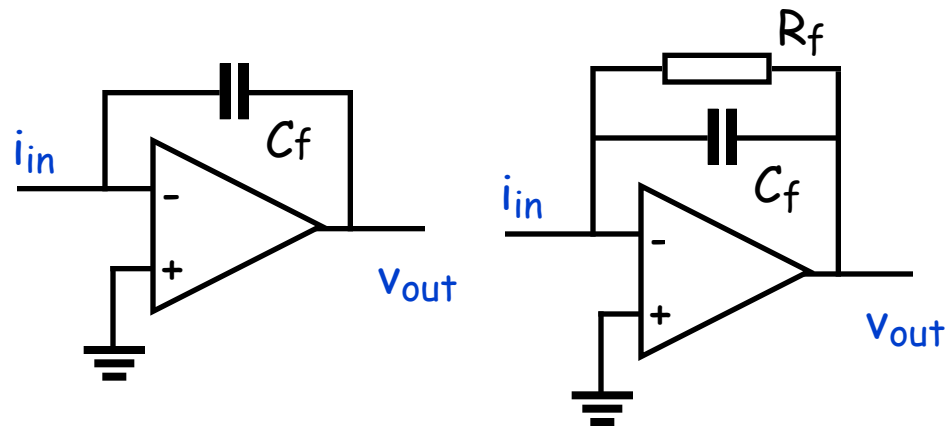
$$v_{out}(t) \approx -(Q/C_f)\exp(-t/\tau) \quad \tau = R_f C_f$$




# Signal processing

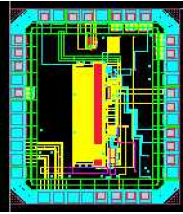

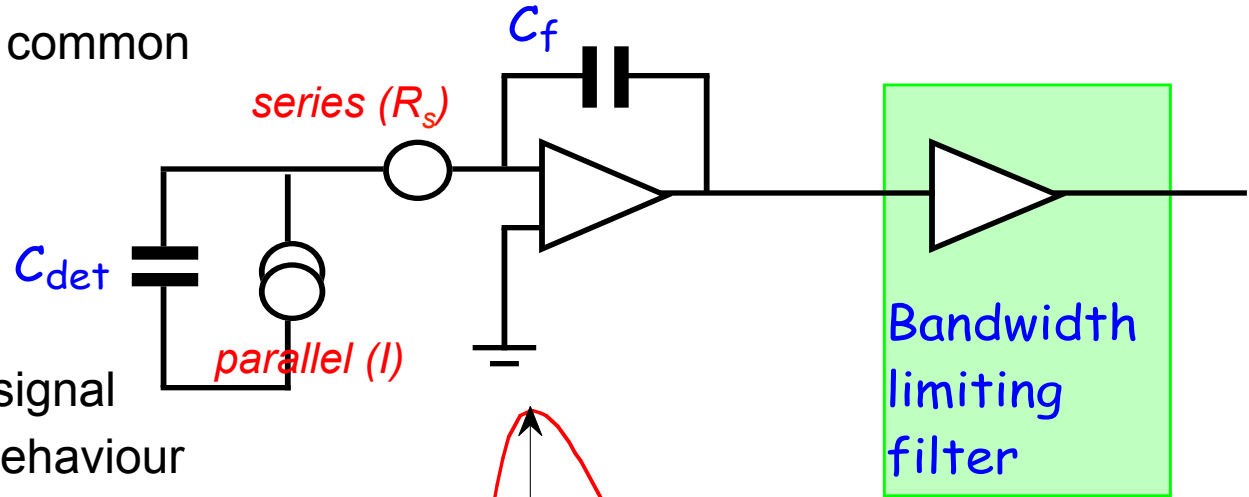
- If noise sources are defined, their impact can be calculated
  - **pulse shaping** is most common



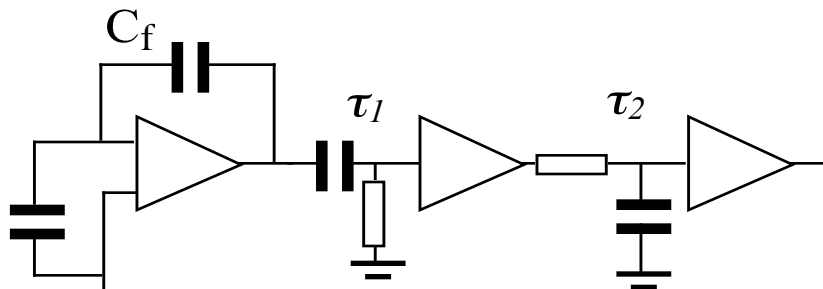- **sampling** an amplifier signal can produce equivalent behaviour



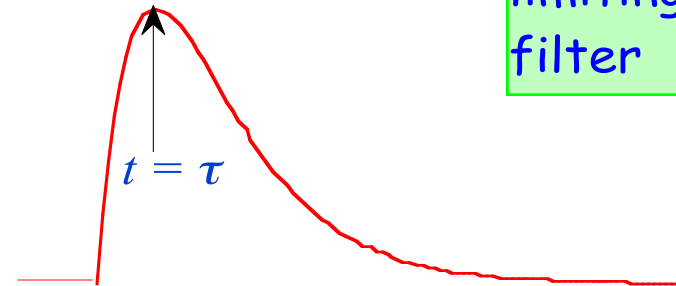- Useful point of comparison: CR-RC filter



*numerical result for many cases*

$$ENC^2 = \frac{e^2}{8} \left( \frac{4kTR_s C_{tot}^2}{\tau} + 2eI\tau \right)$$

# Some numerical values

---

- An approximate numerical value

$$ENC^2 [e^2] \approx \left( \frac{24^2 R_s [k\Omega] C_{tot}^2 [pF]}{\tau [\mu s]} + 100^2 I \tau [\mu s] \right)$$

- using CR-RC filter, ignoring 1/f noise

ie



$$I = 1\text{nA}$$

$$\tau = 1\mu\text{s}$$


$$ENC_p \approx 100e$$

$$R_s = 10\Omega \quad C = 10\text{pF} \quad \tau = 1\mu\text{s} \quad ENC_s \approx 24e$$

# Noise vs technology

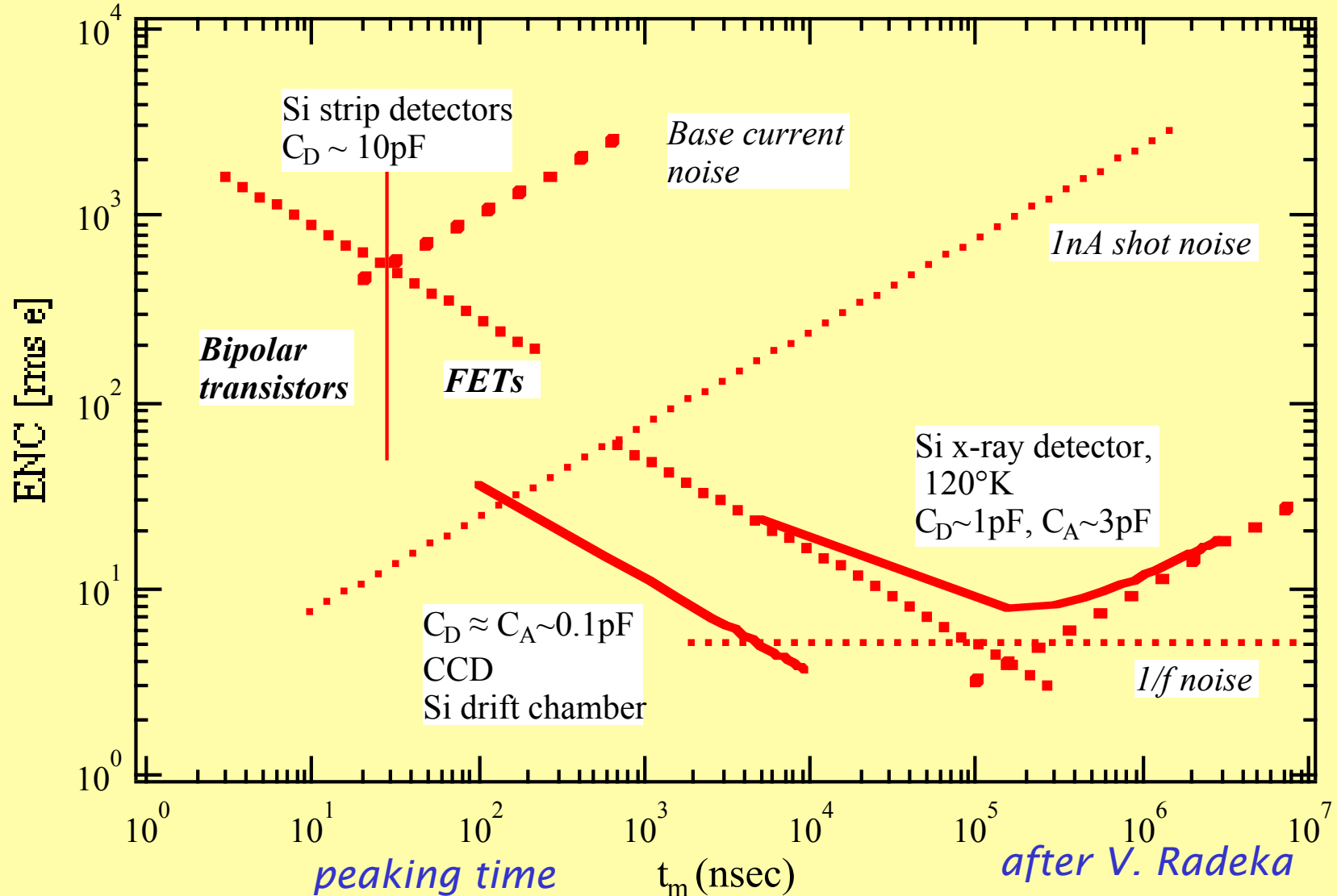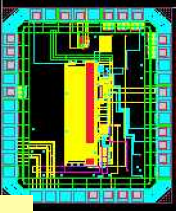

# Noise calculations

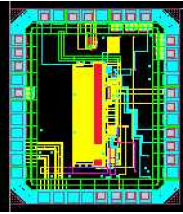


## ■ Summary of principles


- integrate signal spectrum over bandwidth
- integrate noise in quadrature over bandwidth
- computation can be done in time or frequency domain but simplifications are often possible
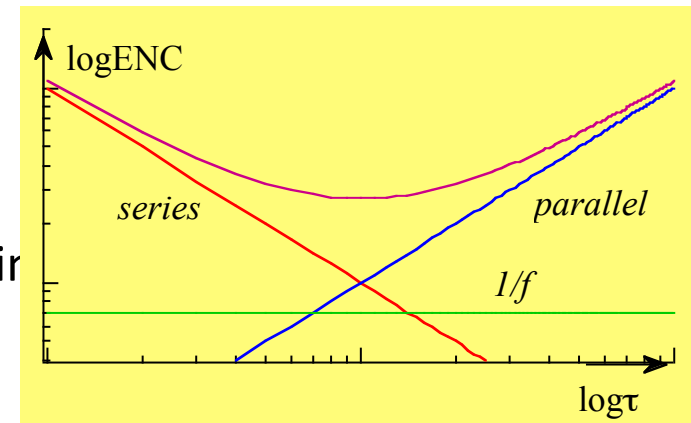
## ■ System noise can be computed with knowledge of impulse response and noise sources

- $\sigma^2 \sim e_n^2 C^2 \int [h'(t)]^2 dt + i_n^2 \int [h(t)]^2 dt$
- provided noise sources  $e_n$  &  $i_n$  are white
- *properly normalise to signal of unit amplitude*



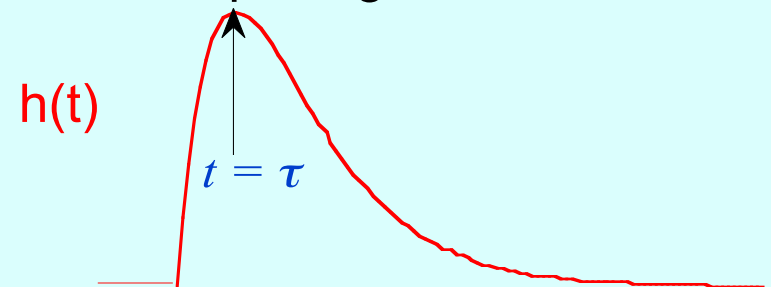Impulse response =  
output of system following fast  
 $\delta$ -like input signal





# Campbell's theorem

Omit

- Most amplifying systems designed to be linear

$$S(t) = S_1(t) + S_2(t) + S_3(t) + \dots$$


- Impulse response

$$h(t) = \text{response to } \delta$$

- Transfer function

$$H(\omega) = v_{\text{out}}(\omega)/v_{\text{in}}(\omega) = \int_{-\infty}^{\infty} h(t) \cdot e^{-j\omega t} dt$$

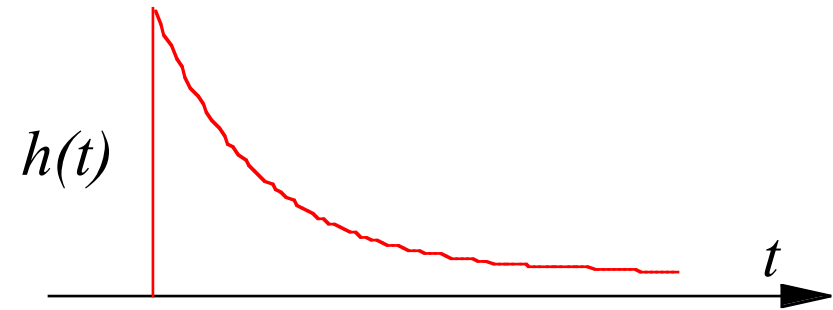ie impulse response  $h(t)$  and transfer function  $H(\omega)$  are Fourier pair




- In a linear system, if random impulses occur at rate  $n$

$$\text{average response } \langle v \rangle = n \int_{-\infty}^{t_{\text{obs}}} h(t) dt$$

$$\text{variance } \sigma^2 = n \int_{-\infty}^{t_{\text{obs}}} [h^2(t)] dt$$

$$\text{so } \sigma^2 = n \int_{-\infty}^{\infty} h^2(t) dt = n \int_{-\infty}^{\infty} |H(\omega)|^2 df$$

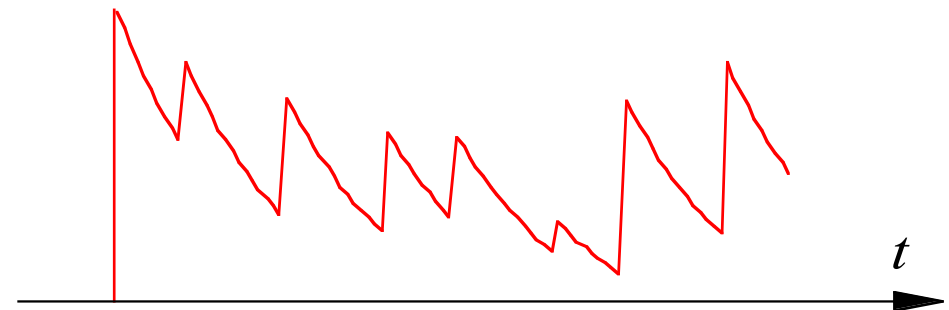i.e. sum all pulses preceding time,  $t_{\text{obs}}$ , of observation



# "Rules" of low noise amplifier systems

---

- Combine uncorrelated noise sources in quadrature

$$e_{\text{tot}}^2 = e_1^2 + e_2^2 + e_3^2 + \dots + i_n^2 R^2 + \dots$$

follows from Campbell's theorem

consider as combinations of gaussian distributions


- First stage of amplifier dominates

noise originates at input

*input transistor is most important - defines noise in most cases*

- Noise is independent of amplifier gain or input impedance  
so noise can be referred to input
- In real systems both are approximations - but normally good ones  
so often sufficient to focus on input device

# Equivalent Noise Charge

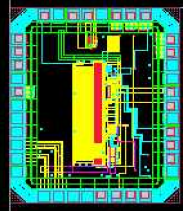


- Systems need to be calibrated:
- ENC is the signal magnitude which produces an output amplitude equal to the r.m.s. noise
  - *ideally measure in some absolute units - e, coul, keV(Si),... rather than ADC channels*


- to calibrate
  - inject charge and look at result
    - eg x-ray signal of known size
    - or electronic test pulse
      - *preferably in-situ*

- measure  $V_{out}$  for known  $Q_{in}$

$$Q_{test} = C_{test} V_{test} = Ne$$

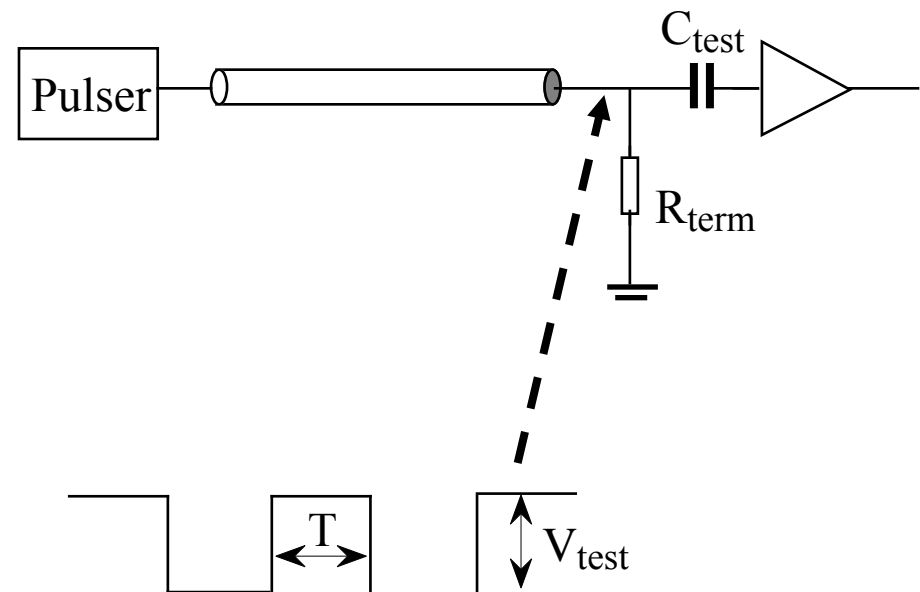


# Noise sources

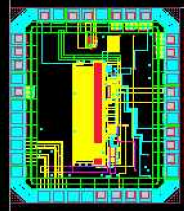

- Thermal noise
  - Quantum-statistical phenomenon; carriers in constant thermal motion
    - macroscopic fluctuations in electrical state of system
  - Typically associated with input transistor or resistive components
- Shot noise
  - Random fluctuations in DC current flow
  - Typically associated with sensor
- $1/f$  noise
  - commonly associated with interface states in MOS electronics
  - Luckily, less important for high speed electronics
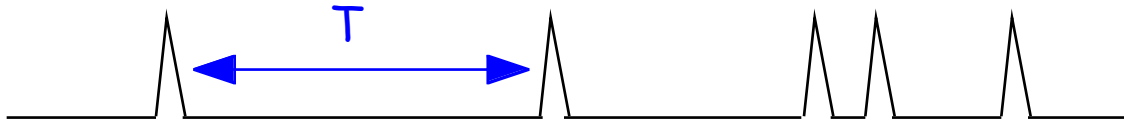
# Shot noise

- Poisson fluctuations of charge carrier number  
eg arrival of charges at electrode in system - induce charges on electrode



quantised in amplitude and time

- Examples  
electrons/holes crossing potential barrier in diode or transistor  
electron flow in vacuum tube

$$\langle i_n^2 \rangle = 2qI \Delta f$$

WHITE

(NB notation  $e = q$ )

$I$  = DC current

**gaussian distribution  
of fluctuations in  $i$**

# Thermal noise

Just note that this is needed to do calculations

- Einstein (1906), Johnson, Nyquist (1928)

Mean voltage  $\langle v \rangle = 0$

Variance  $\langle v^2 \rangle = 4kT.R.\Delta f$   $\Delta f =$  observing bandwidth

$\sigma(v) = \sqrt{\langle v^2 \rangle} = 1.3 \cdot 10^{-10} (R.\Delta f)^{1/2}$  volts at 300K



e.g.  $R = 1M\Omega$   $\Delta f = 1\text{Hz}$   $\sigma(v) = 0.13\mu\text{V}$

Noise power =  $4kT.\Delta f$

independent of R & q independent of f - WHITE

- Circuit representations

Noise generator + noiseless resistance R

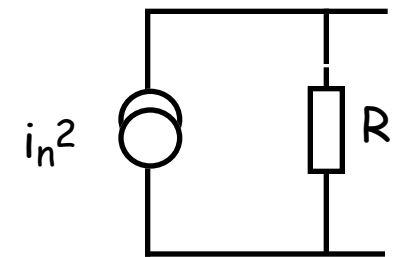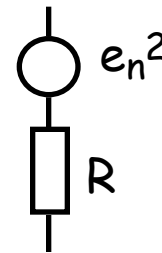

**gaussian distribution  
of fluctuations in v**


- Spectral densities

mean square noise voltage or current per unit frequency interval


$$w_v(f) = 4kTR \quad (\text{voltage})$$

$$w_i(f) = 4kT/R \quad (\text{current})$$


# CMOS transistor

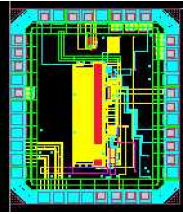

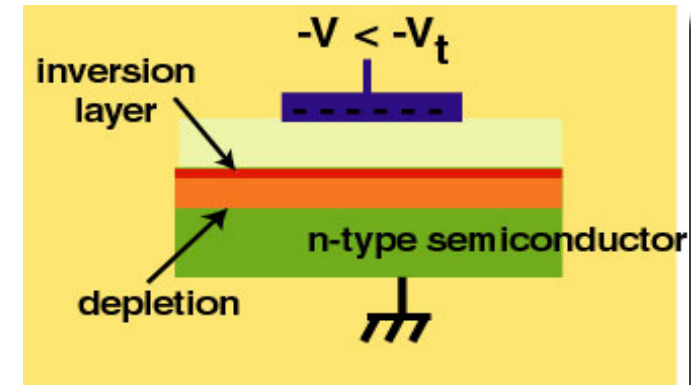- Reminder of basic FET physics
  - bias “metal” gate to deplete substrate
  - beyond a certain threshold voltage, substrate does not deplete deeper
  - instead “inversion layer” created




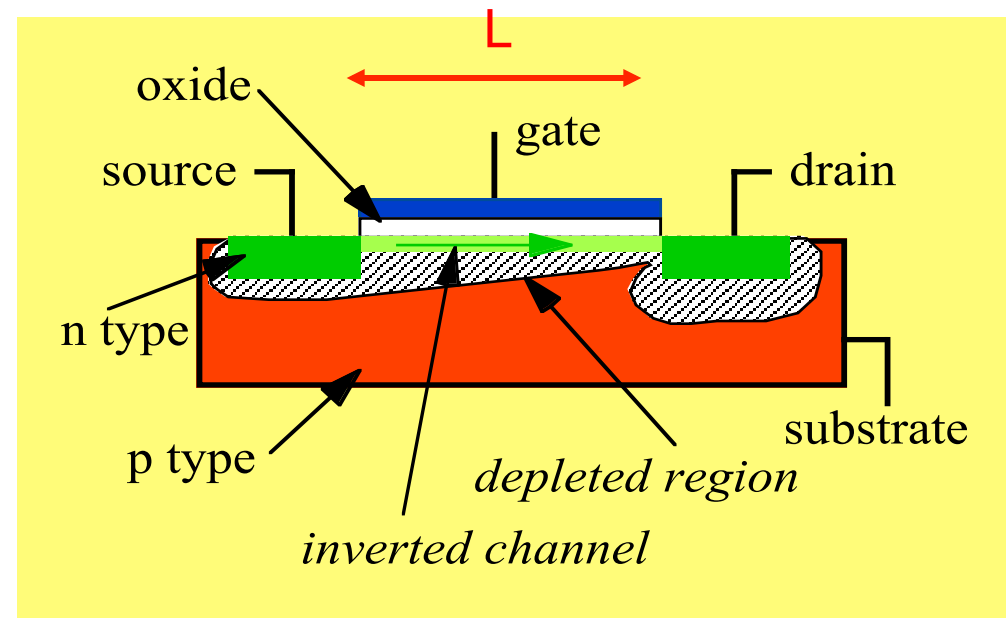- Inversion layer
  - extremely shallow, at oxide-silicon interface
  - carriers mobile in applied field
- Transistor operation
  - Modulation of source-drain current via  $V_{gate}$



# Noise in MOS circuits

Omit

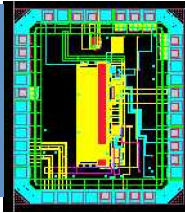

- Gate shot noise is negligible *insulating gate and no current*
- Thermal noise voltage from channel

$$e_n^2 = 4kT\gamma\left(\frac{2}{3g_m}\right)\Delta f$$

$\gamma = \text{excess noise factor} \sim 1$

- Transconductance

- $C_{ox} = \epsilon_{ox}/t_{ox}$


- $W/L = \text{transistor width/length}$

$$g_m = \sqrt{2\mu C_{ox} I_{DS} \left(\frac{W}{L}\right)}$$

- $1/f$  noise usually unimportant (for LHC)

- Implications

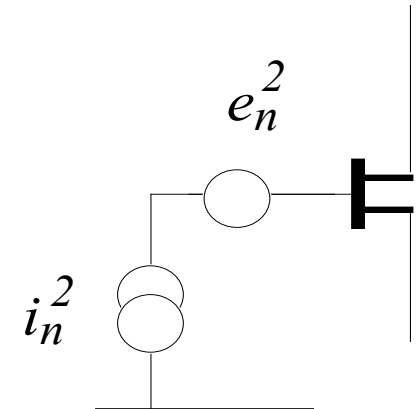
- To achieve low noise, aim for large  $W/L$  and large (tolerable)  $I_{DS}$
- but  $C_{amp} = C_{ox}WL$  and require capacitance matching:  $C_{amp} \approx C_{det}/3$
- Mobility is also T dependent, influencing noise and speed  $\mu(T) \sim T^{-3/2}$



C = capacitance  
 T = temperature  
 $\Delta f$  = bandwidth  
 $\mu$  = mobility (v/E)



# Noise spectra

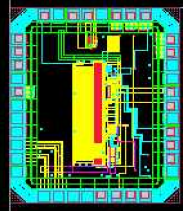

- pMOS preferred for lower 1/f noise

- 3dB bandwidth


- eg LHC


$\Delta f_{3\text{db}} = 2.6 - 15.4\text{MHz}$

- CR-RC pulse shaping

- $\tau = 25\text{ns}$



- or 1/f noise might be an issue

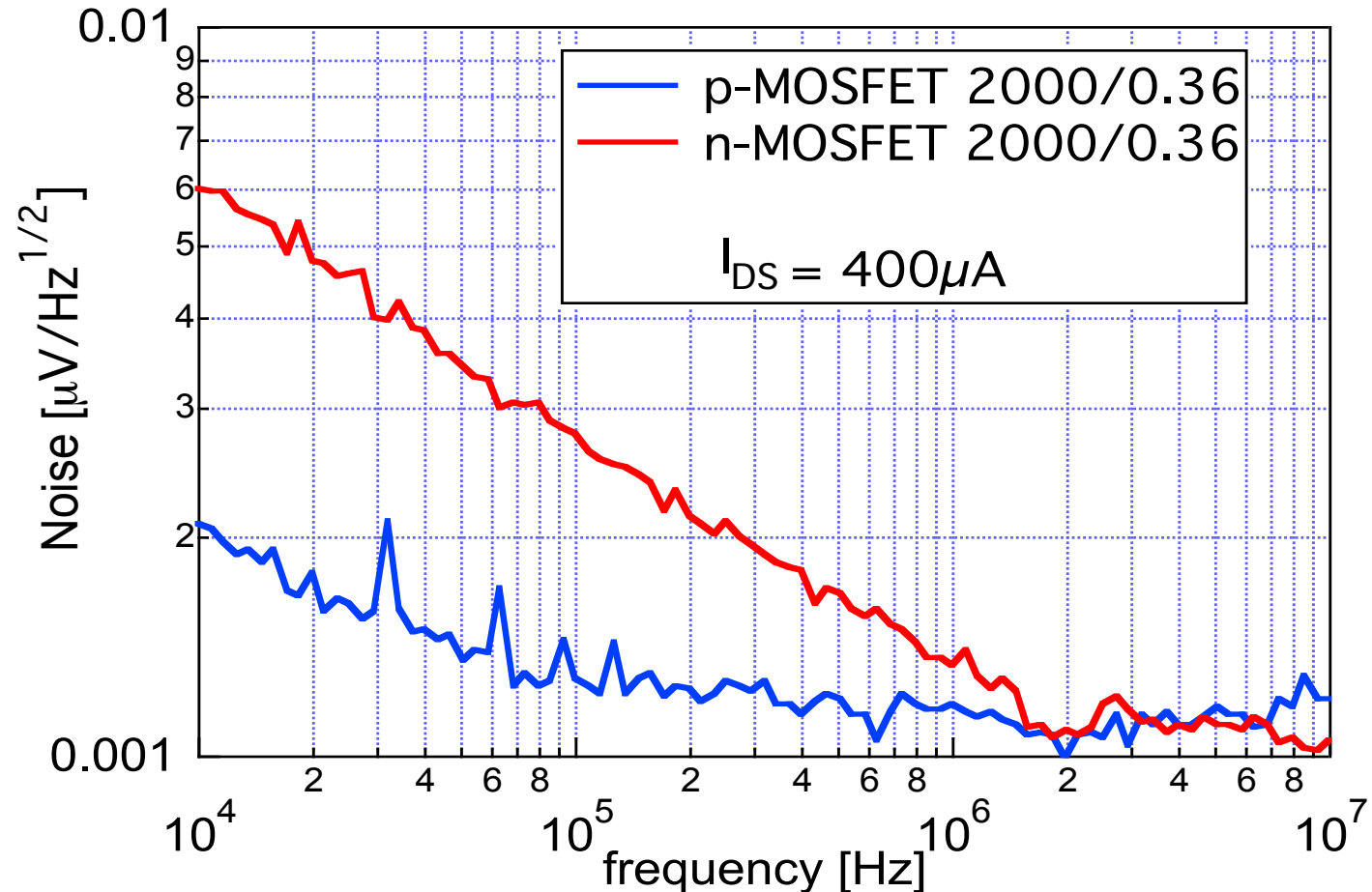

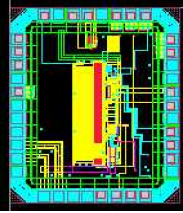

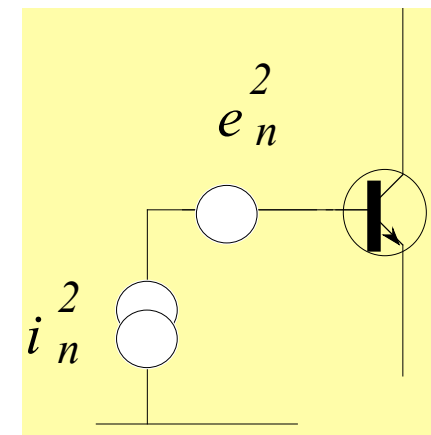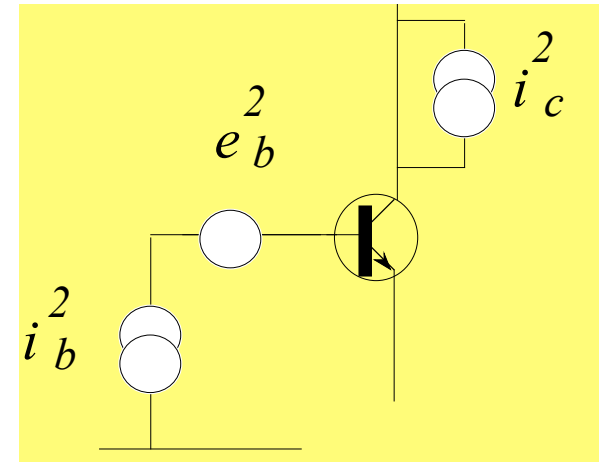
# Bipolar transistor noise



- Basic sources are
  - Shot noise in  $I_C$   $i_c^2 = 2eI_C\Delta f$
  - Shot noise in  $I_B$   $i_b^2 = 2eI_B\Delta f$
  - Thermal noise in base & contacts
    - $e_b^2 = 4kT \cdot r_{bb'} \cdot \Delta f$
- Reconfigure so that noise sources are external which then shows that
  - $i_n^2$  and  $e_n^2$  are **correlated**,  
ie can't reduce both simultaneously
  - so achievable range of noise is limited and happens to provide best performance for high speed applications
  - however bipolar noise determined mainly by currents
    - so easy to estimate



# Time variant filters - sampling

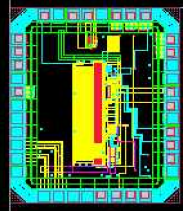


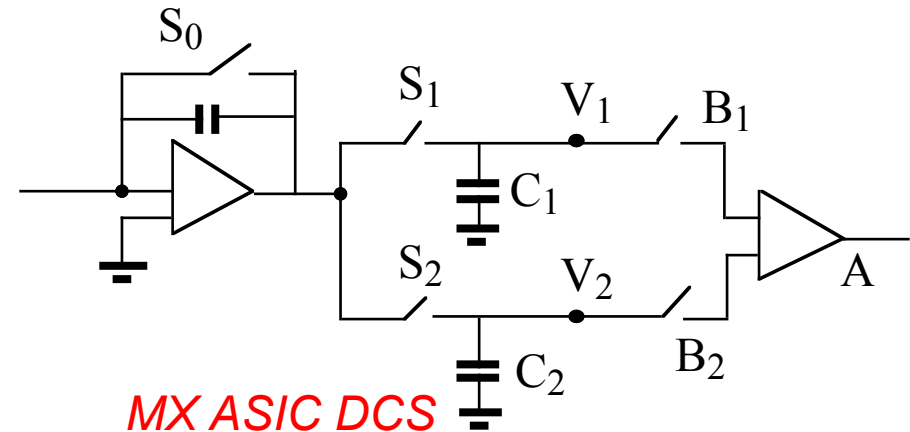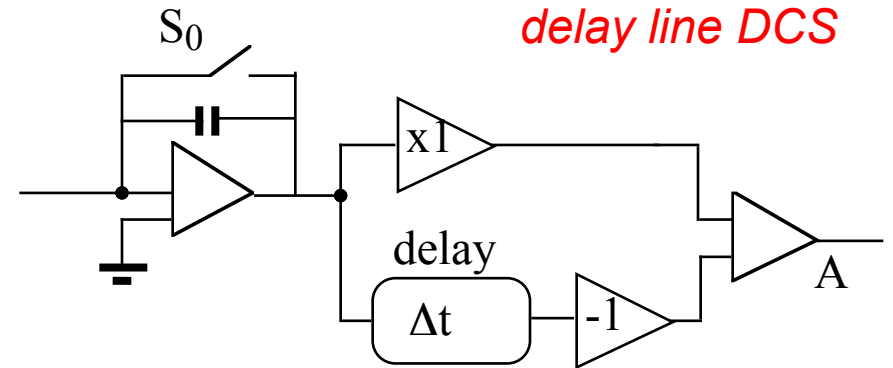- Alternative to pulse shaping
  - filters based on summation
  - easy to implement in several technologies
  - eg. typically switched capacitor filters
  - but also delay-line or digital possible
    - beware of extra noise issues
- based on sample & hold
  - e.g. double correlated sampling
- Switched capacitor design convenient for CMOS
  - accurate capacitances (ratios)
  - MOSFET switches




# Weighting function

Omit

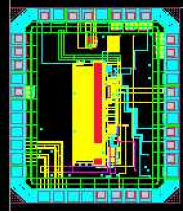

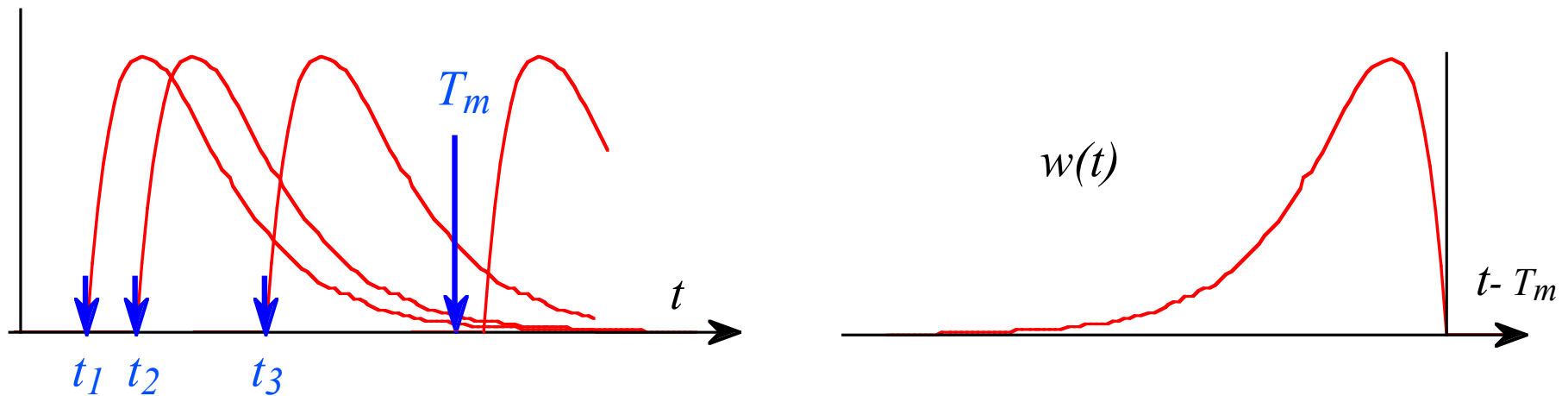
- How to calculate noise of time variant systems?
  - What output is produced at  $T_m$  by impulse at time  $t$ ?
  - consider all  $t$  - defines weighting function



- Time invariant filter      $w(t)$  is mirror image of  $h(t)$
- Noise calculation      $ENC^2 = e_n^2 C^2 \int [w'(t)]^2 dt + i_n^2 \int [w(t)]^2 dt$
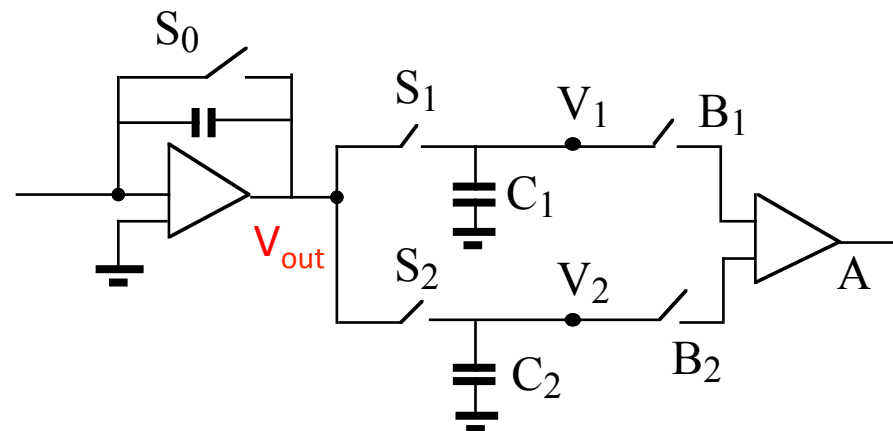
# Double correlated sampling

- Sample & hold method  
initially switches  $S_0$   $B_1$   $B_2$  open,  $S_1$   $S_2$  closed  
switch  $S_0$  is Reset



$V_{out}$  = output from charge sensitive preamplifier


open  $S_1$  : preserves  $V_{out}$  on  $C_1$

after time  $\Delta t$  open  $S_2$  : preserves  $V_{out}$  on  $C_2$

then, close  $B_1$  and  $B_2$ :


output  $A = V_1 - V_2$

reset preamp later


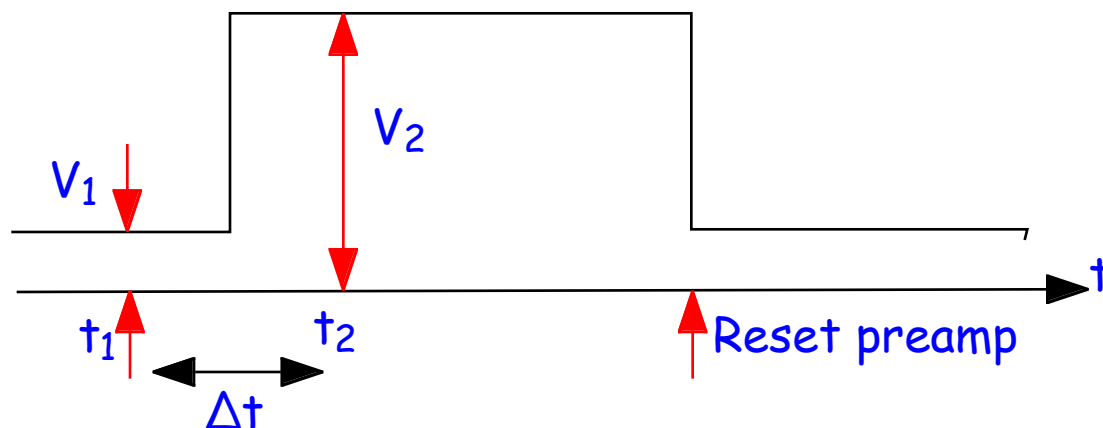


- need to know when signal will arrive!


# CR-RC pulse + integrating ADC

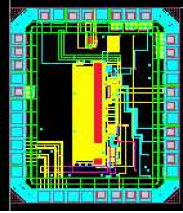

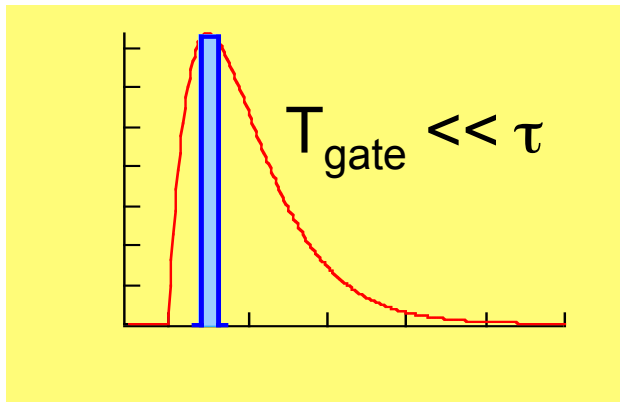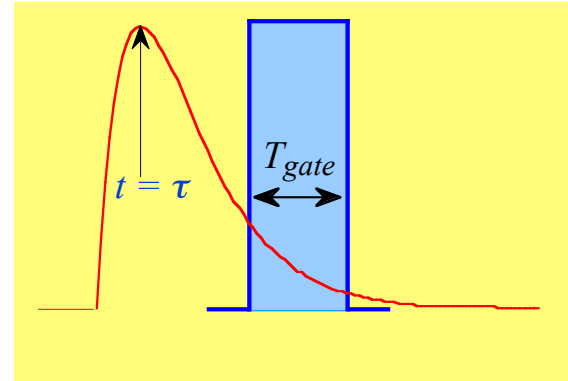- Example of time-variant filter..
- Convolution of pulse shape with gate
  - $w(t) = h(t) * g_{gate}(t)$
  - (ignoring  $t$  reflection)
  - examples



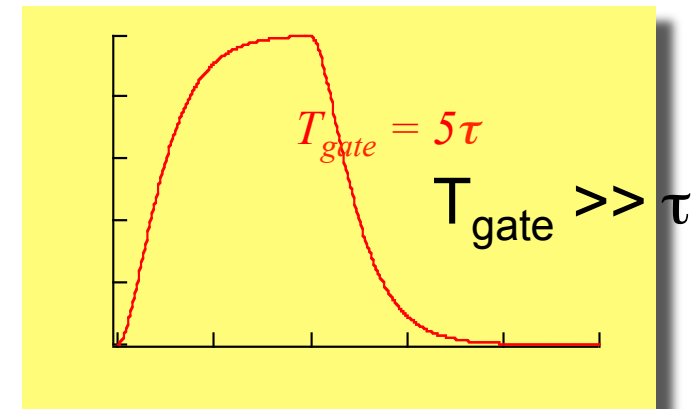similar to peak sensing ADC  
*gated at peak!*



new, wider weighting function  
*recompute noise integrals*

ADC may change filtering and **increase** or **decrease** noise

# Digitisation noise

- Eventually need to convert signal to a number  
quantisation (rounding) of number = noise source  
the more precise the digitisation, the smaller the noise

- After digitisation all that is known is that  
signal was between  $-\Delta/2$  and  $\Delta/2$

$$\langle x \rangle = \int x \cdot p(x) \cdot dx / \int p(x) \cdot dx$$


$$\sigma^2 = \langle x^2 \rangle = \int x^2 \cdot p(x) \cdot dx / \int p(x) \cdot dx$$

$$\int p(x) \cdot dx = \int_{-\Delta/2}^{\Delta/2} dx = [x]_{-\Delta/2}^{\Delta/2} = \Delta$$

$$\int x^2 \cdot p(x) \cdot dx = \int_{-\Delta/2}^{\Delta/2} x^2 \cdot dx = [x^3/3]_{-\Delta/2}^{\Delta/2} = 2\Delta^3/24$$

so  $\sigma^2 = \Delta^2/12$

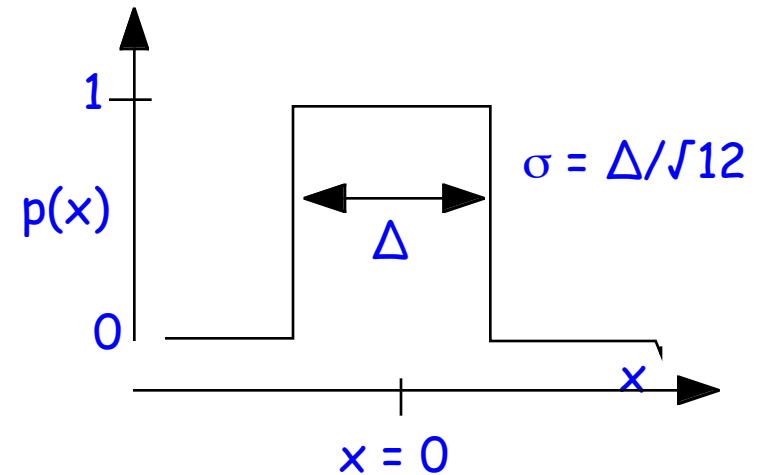- ie statistical noise which is proportional to digitisation unit




# Time measurements and noise

- When did signal cross threshold ?  
noise causes “jitter”

$$\Delta t = \sigma_{\text{noise}} / (dV/dt)$$

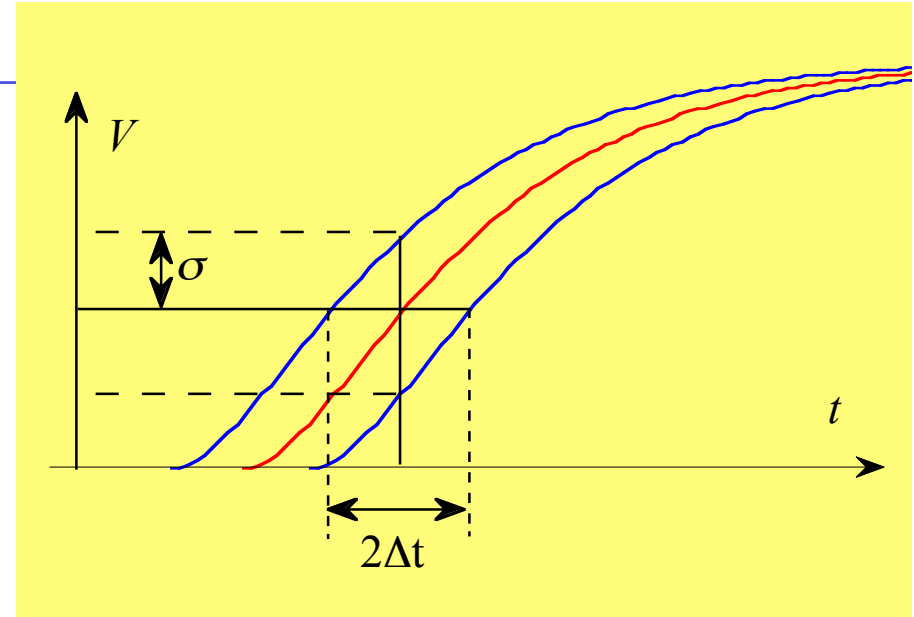- compromise between  
bandwidth (increased  $dV/dt$ )  
noise (decreased bandwidth)



- limits systems where preamplifier pulse used to generate trigger  
eg x-ray detection

- typical preamp response  
 $V = V_{\text{max}}(1 - e^{-t/\tau_{\text{rise}}})$

$$\text{so } \Delta t \approx \sigma_{\text{noise}} \tau_{\text{rise}} / V_{\text{max}} \quad t \ll \tau$$

