 


CBC3 Architecture & Plans

STFC RAL: [Mark Prydderch](#), D. Braga, L. Jones, M. Key-Charrier

Imperial College: G. Hall, M. Raymond, M. Pesaresi





Imperial College
London




Science & Technology
Facilities Council

Outline

  


- **CBC2 Architecture: Reminder**
- **CBC3 Architecture: What's new**
- **Plans**


CBC2 Architecture

 

CBC3 Architecture

 

CBC3 Front End

 

Pre-Amplifier:

- Single polarity
- Return to baseline within 50 ns
- 1V operation
- Larger Detector Capacitance

Gain Amplifier:


- Single polarity
- 1V operation

Comparator:


- Balance current load
- 1V operation

Hit Detect


CBC2

 

CBC3

 

Stub Logic

 

CBC3 Stub Gathering Logic

Outputs from correlation logic
(Correlation bit + 5 bit bend)


Example:

2 positive correlations at cluster locations $n+1/2$ & $n+1 1/2$

Left multiplexer chain activated for cluster $n+1/2$


Middle multiplexer chain activated for cluster $n+1 1/2$

 Note: CWD logic will never pass immediately adjacent clusters (i.e. active clusters on n and $n+1/2$ are not possible)




Output
3x(8 bit Address + 5 bit bend)

CBC3 Bend Look-Up Table

 

CBC3 Data Readout

 

S = Cluster address ($\frac{1}{2}$ strip resolution)

B = Bend data

SoF = Stub Overflow (>3 Stubs)


? = Spare/To be defined

Sync = For synchronisation with CC

R = Triggered readout data
(remains unparsified)




Six differential (SLVS) outputs running at 320 Mbps

CBC3 Triggered Data Format

 

NOTE: Existing buffer length of 32 is sufficient for very low inefficiency at 1 MHz rate

CBC3 SRAM

   

Layout of 8 SRAM cells

Miscellaneous

Fast Command Interface: Fast Reset, Trigger, Test Pulse Trigger, L1 Counter Reset

Biases: VCTH to be monotonic & 1 mV resolution (10 bit); Modify IREF so that I_{bias} is related to GND rather than VDDA.

I2C register SEU immunity: Modify registers to improve immunity


Clock domains: DLL with programmable tap off for all of 40 MHz domain

Powering: 1.2V VDDD +/- 10%; no switched cap DC-DC; LDO modified to cope with minimum VDD

40MHz Test Mode: To allow testing at 40MHz on Wafer Prober

Pad Pitch: As for CBC2

CBC3 schedule

 

- Manufacture on MOSIS MPW
- Aim to have CBC3 in hand ~1st half 2016
- CBC4 is an 'insurance iteration' in case something needs fixing

END