

CMS Binary Chip status

Outline

- introduction

- front end design & simulated performance

- current layout status

- system aspects

 - architecture, powering, module concepts


- summary

CBC context

CBC targeted at phase II outer tracker region
 $r > \sim 50$ cm

assumed instrumented by short strips
 $\sim 2.5 / 5$ cm

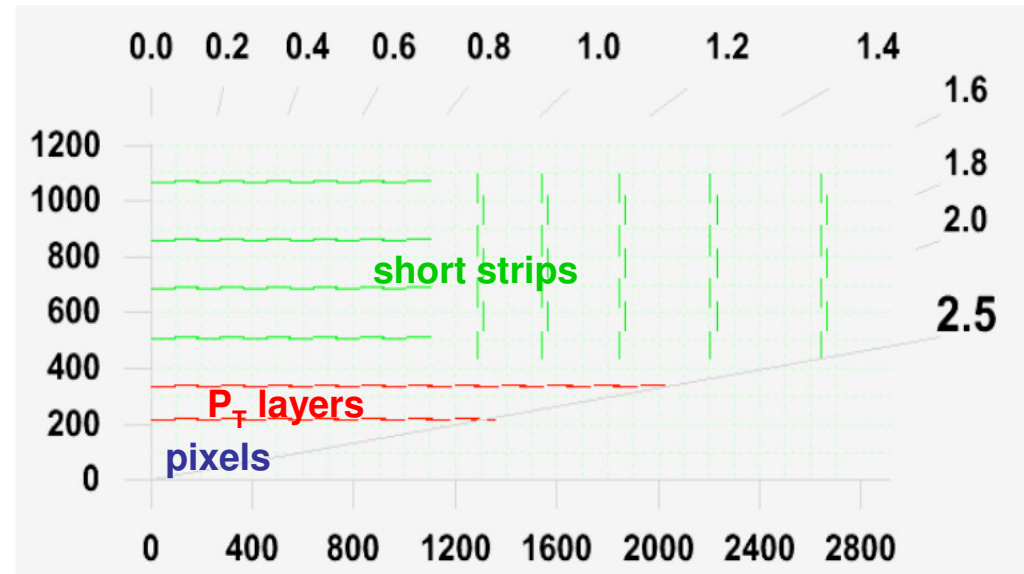sLHC CMS tracker will operate at low T
 $\sim -30 \rightarrow -40$ degrees



=> important to meet specs at low temperatures for all simulation process corners
(but will still want to test and run chips and modules at room temperatures)

DC-DC power supply system assumed

run frontend at $V_{DD}=1.1$ V to provide headroom for LDO in supply rail to improve PSR

CBC under design since March 2009 in 130nm IBM CMOS
Lawrence Jones (RAL engineer)
planned submission May 2010

architecture choice

binary un-sparsified architecture

simplicity/robustness, lowest power


main functional blocks

- fast front end amplifier – 20 nsec peaking
- comparator with programmable threshold trim
- 256 deep pipeline (6.4 μ s)
- 32 deep buffer for triggered events
- output mux and driver (SLVS)
- fast (SLVS) and slow (I2C) control interfaces

some target specs (see * for full list)


- both signal polarities
- DC coupled to sensor – up to 1 μ A leakage
- noise: $< 1000e$ for $C_{\text{SENSOR}} \sim 5$ pF
- power consumption
 < 0.5 mW/channel for $C_{\text{SENSOR}} \sim 5$ pF

CBC

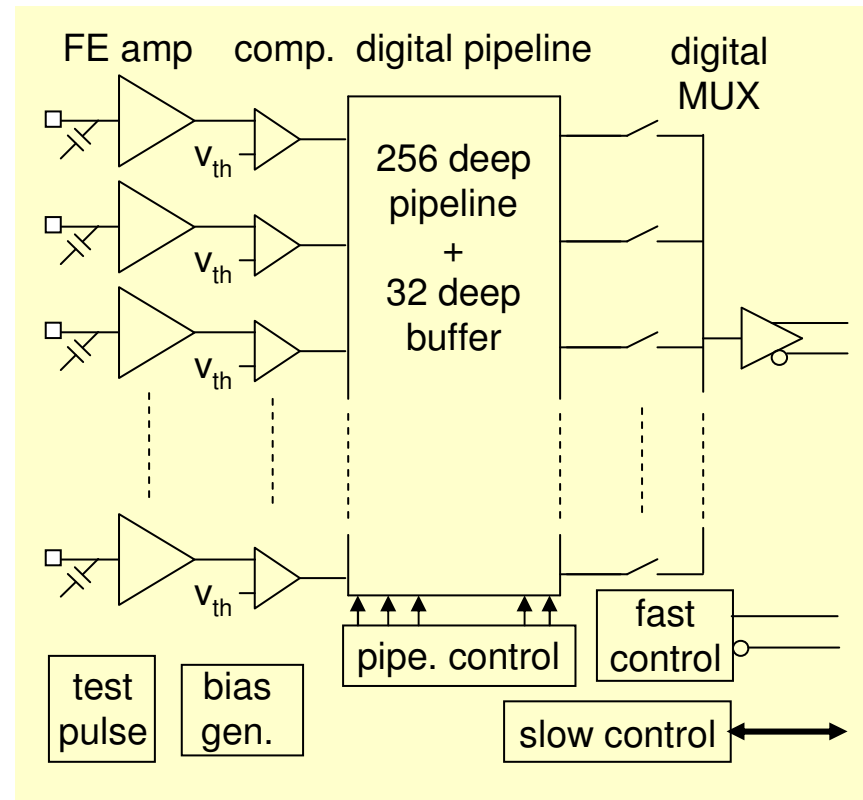

* http://icva.hep.ph.ic.ac.uk/~dmray/CBC_documentation/CBC_specifications.pdf

CBC front end

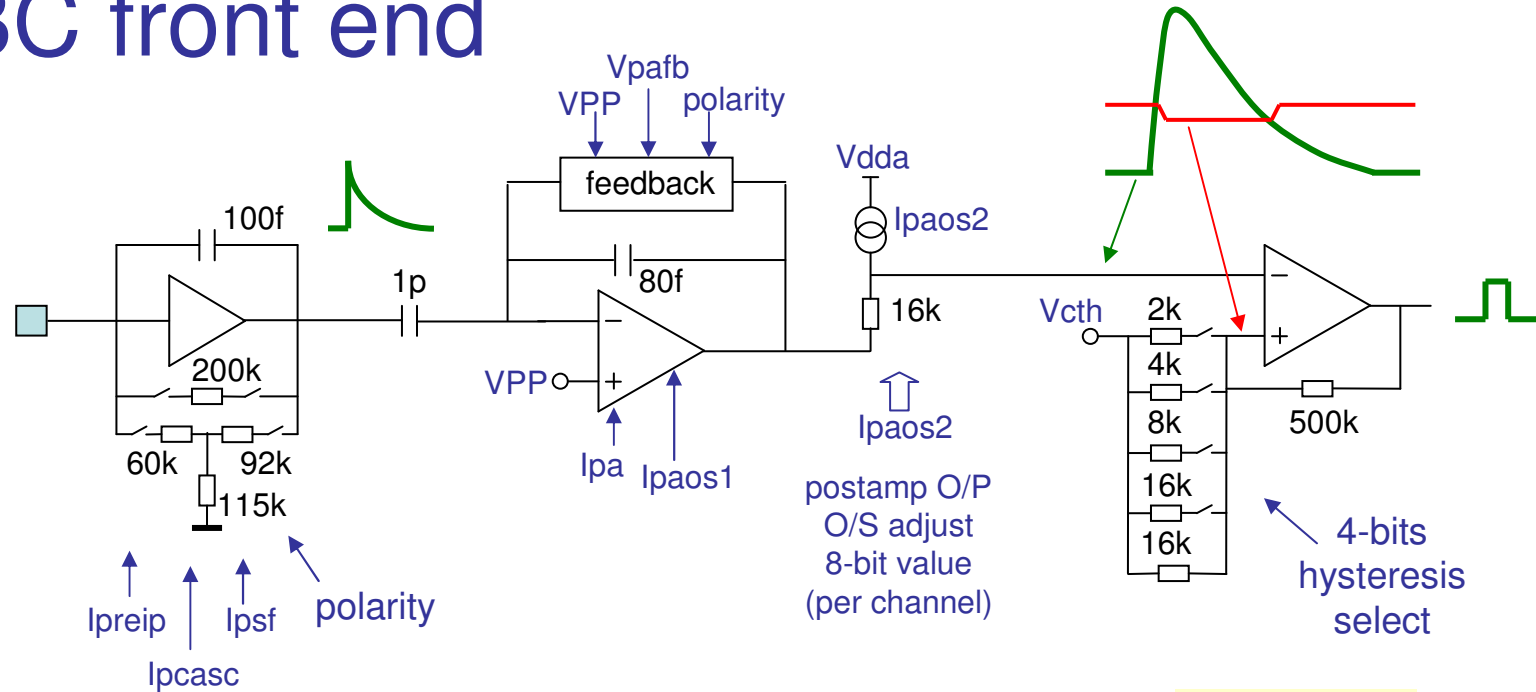

preamp

resistive feedback absorbs I_{leak}
 T network for holes
 $R_f.C_f$ implements short
 diff. time constant
 (good for no pile-up)

postamp

provides gain and int. time constant
 $\sim 50 \text{ mV} / \text{fC}$
 AC coupled removes I_{leak} DC shift
 individually programmable O/P DC level
 implements channel threshold tuning
 8-bits, $0.8 \text{ mV} / \text{bit}$, 200 mV range

comparator



global threshold
 (indiv. tuning at postamp O/P)
 programmable hysteresis

short summary of simulated front end performance follows
 for much more detail see design review talk:


http://icva.hep.ph.ic.ac.uk/~dmray/CBC_documentation/frontend_design_review_Oct_09.pdf

postamp output pulse shape

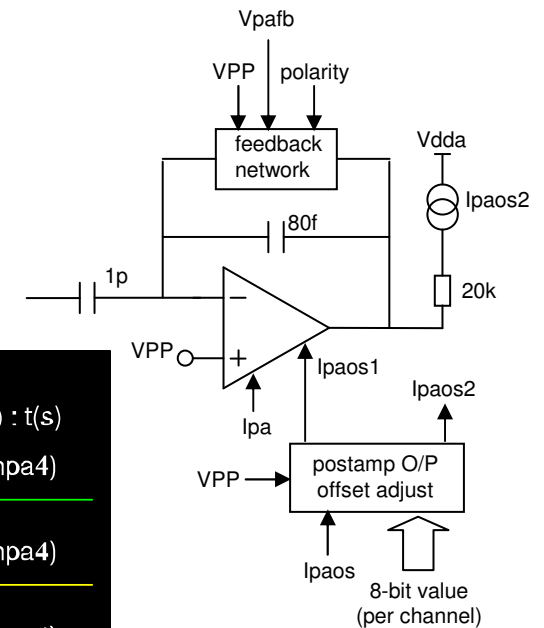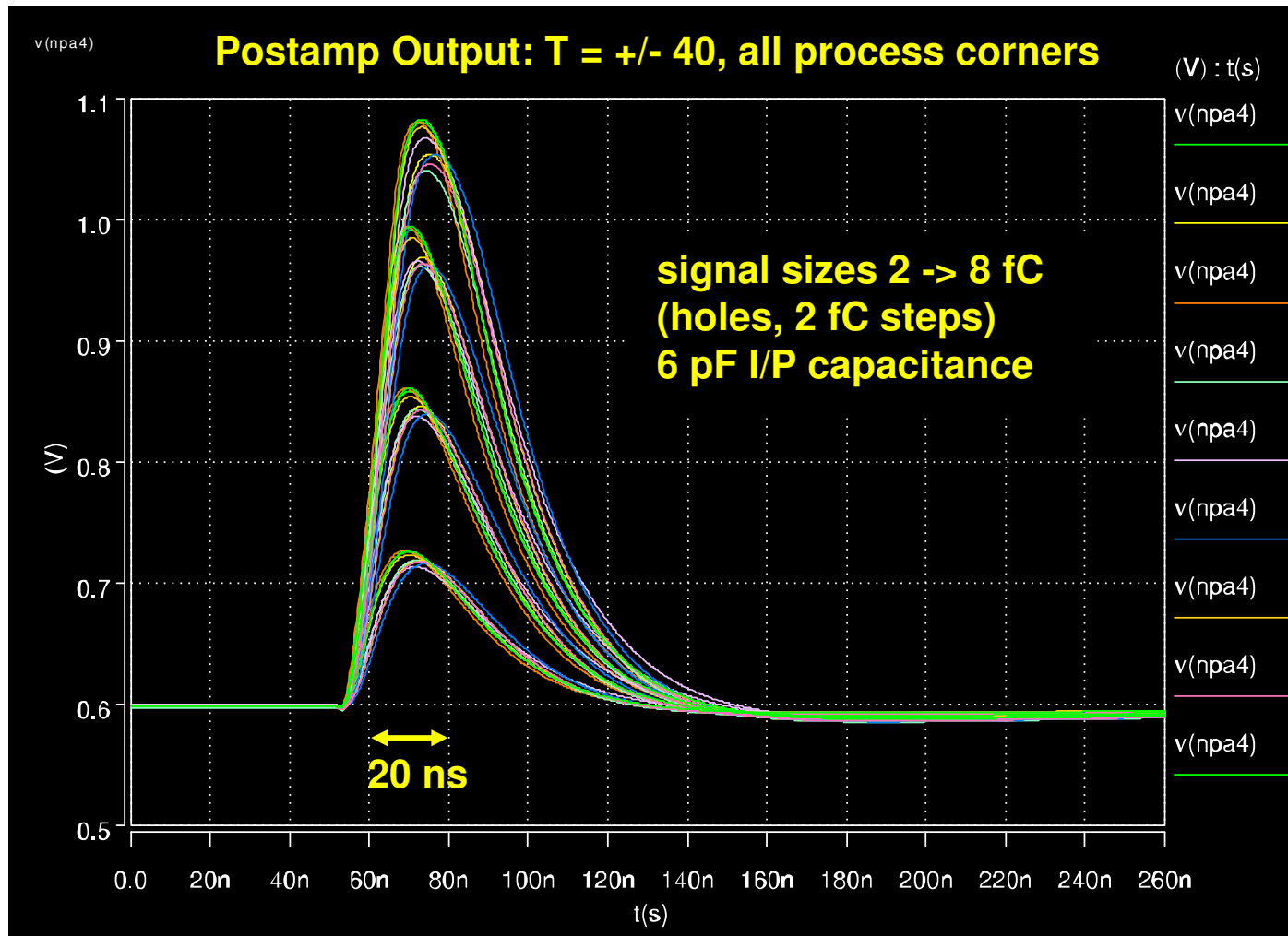~ 20 nsec peaking, ~ 50 mV / fC
robust to temperature (-40 -> +40) and process variations





noise at postamp output

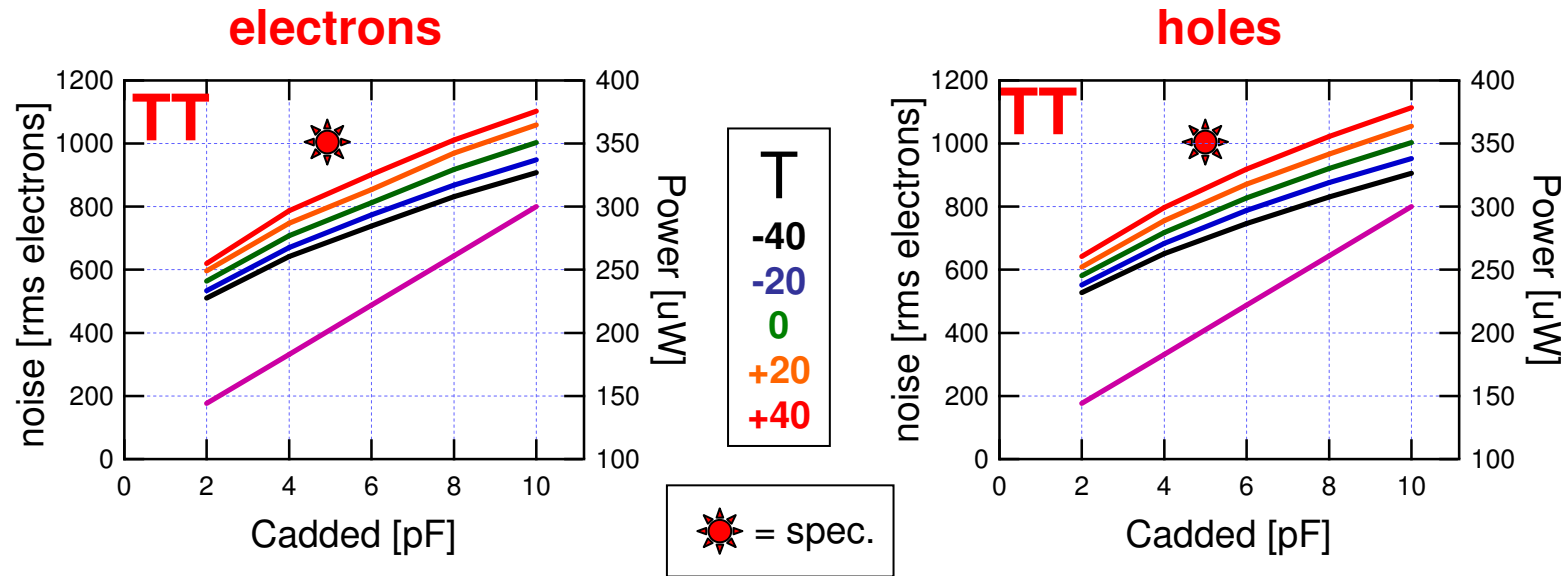



preamp input device power varied with C_{added} to maintain pulse shape
note: power in figures above includes preamp and postamp

noise within spec. (doesn't vary much ($< \sim 10\%$) with process variation)

overload recovery at postamp output

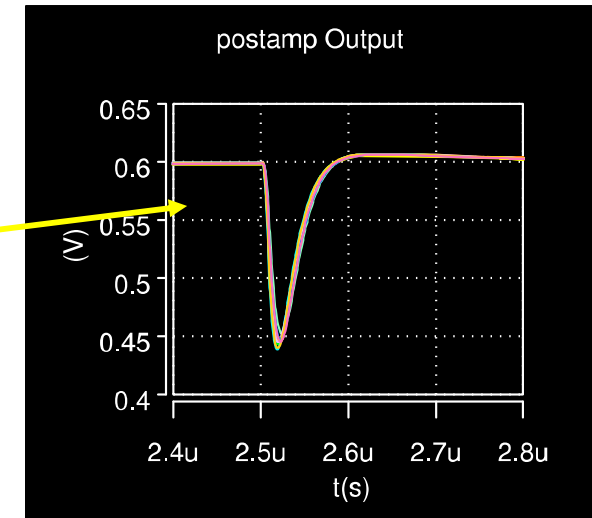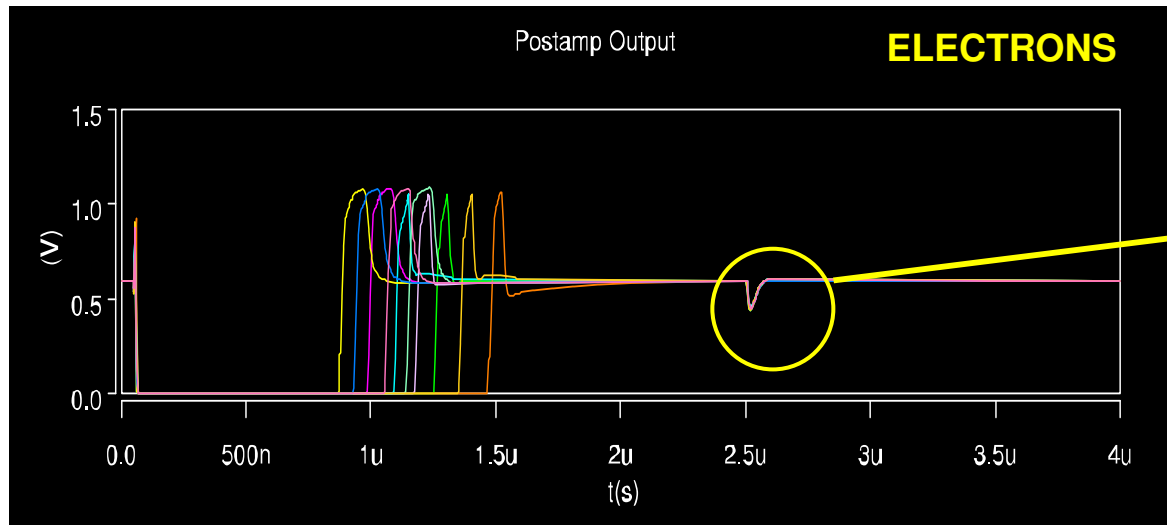

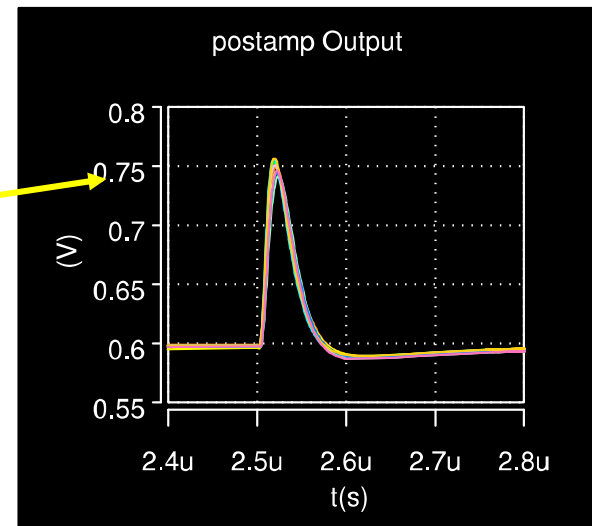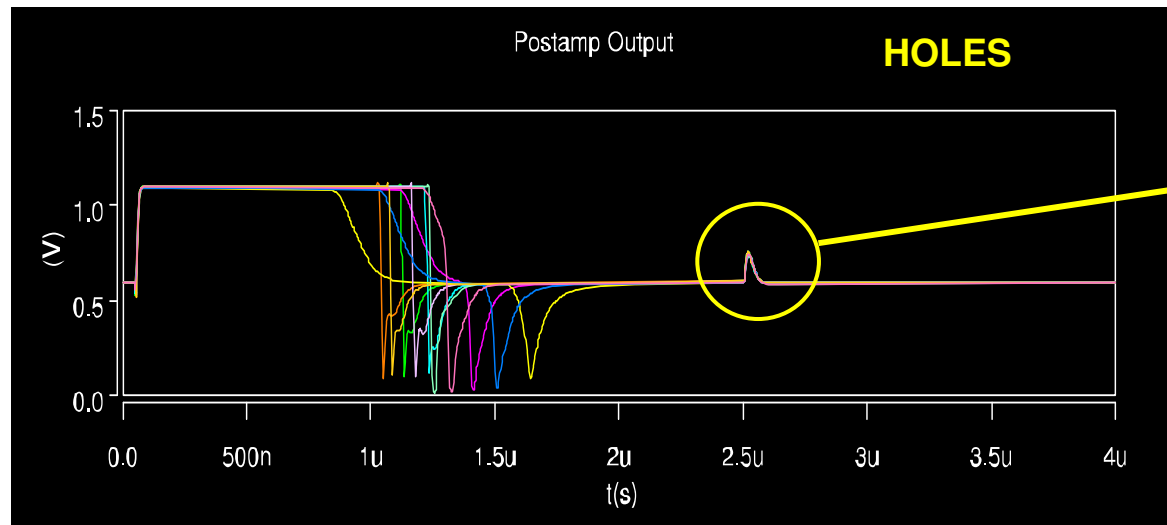T = - 40 & +40, I_{leak} = 0.5 μA, preamp C_{in} = 6 pF, all process corners
4 pC injected at t = 50 ns, 2.5 fC injected at t = 2.5 μs
recovery spec. comfortably met (< 2.5 μsec)






time-walk at comparator O/P

dependence of comparator fire time on signal size
must be less than 1 BX

Atlas specification

≤ 16 ns time difference between comparator output edges for input signals of 1.25 fC and 10 fC, for a threshold setting of 1 fC

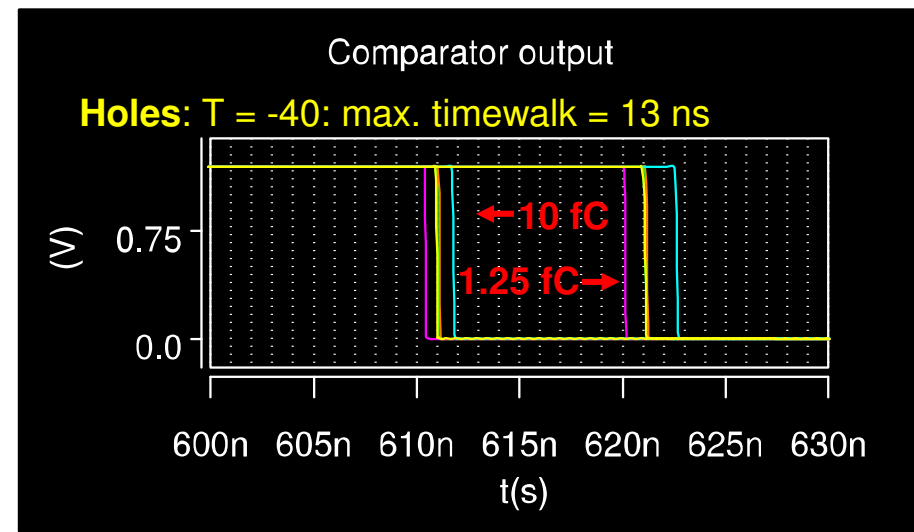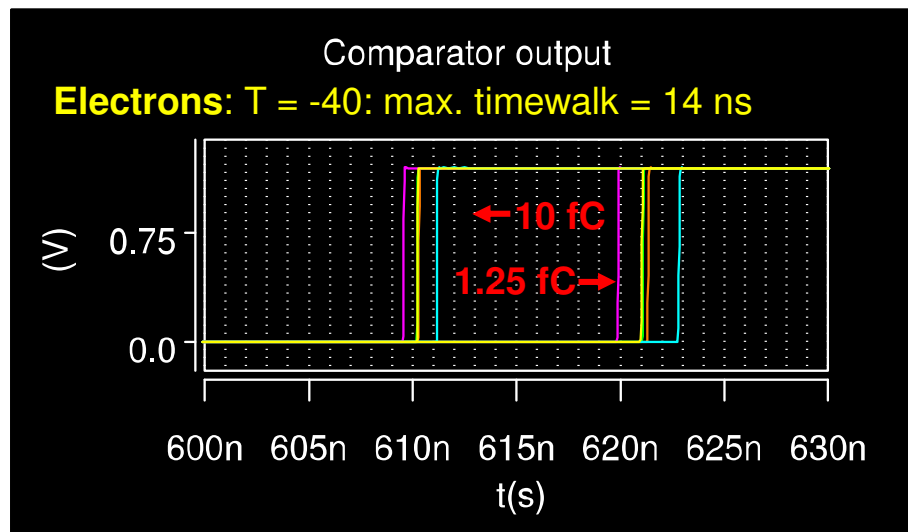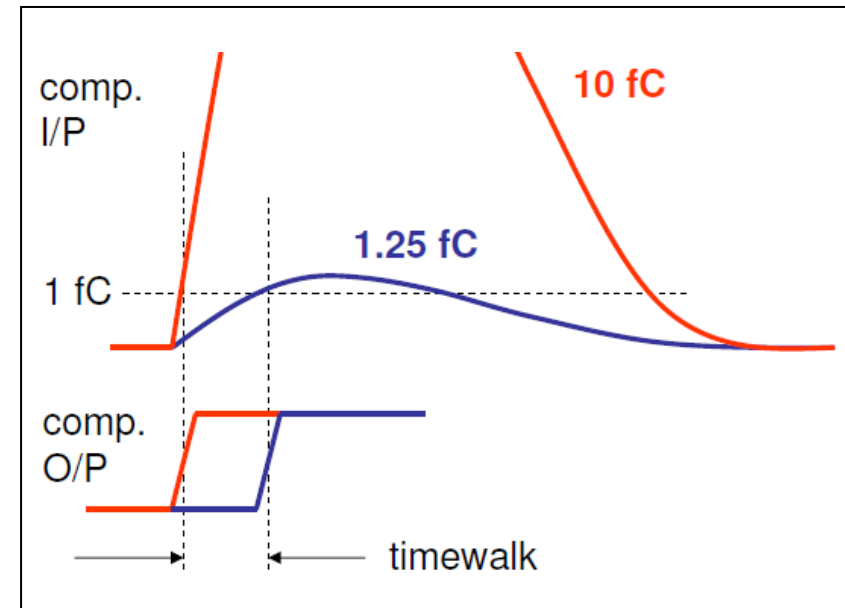(spec. defined for 300 μ m sensors – but still maintained for 200 μ m, scaling all quantities by 2/3)



overall layout – so far

what's really there

- complete front end chain

 - preamp

 - postamp + output offset adjust

 - comparator + adjust register

- 256 cell pipeline

- 32 cell L1 triggered data buffer

- pipeline control logic

- I²C

- bias generator

items in yellow not there yet

(and not necessarily in final position)

- multiplexer

- output pads

- powering circuitry (DC-DC & BandGap from CERN)

- fast control interface

- test pulse


 - no time for DLL based version

 - will provide pads to feed test caps

...


DC-DC -> bandgap/LDO separation issues

7 mm

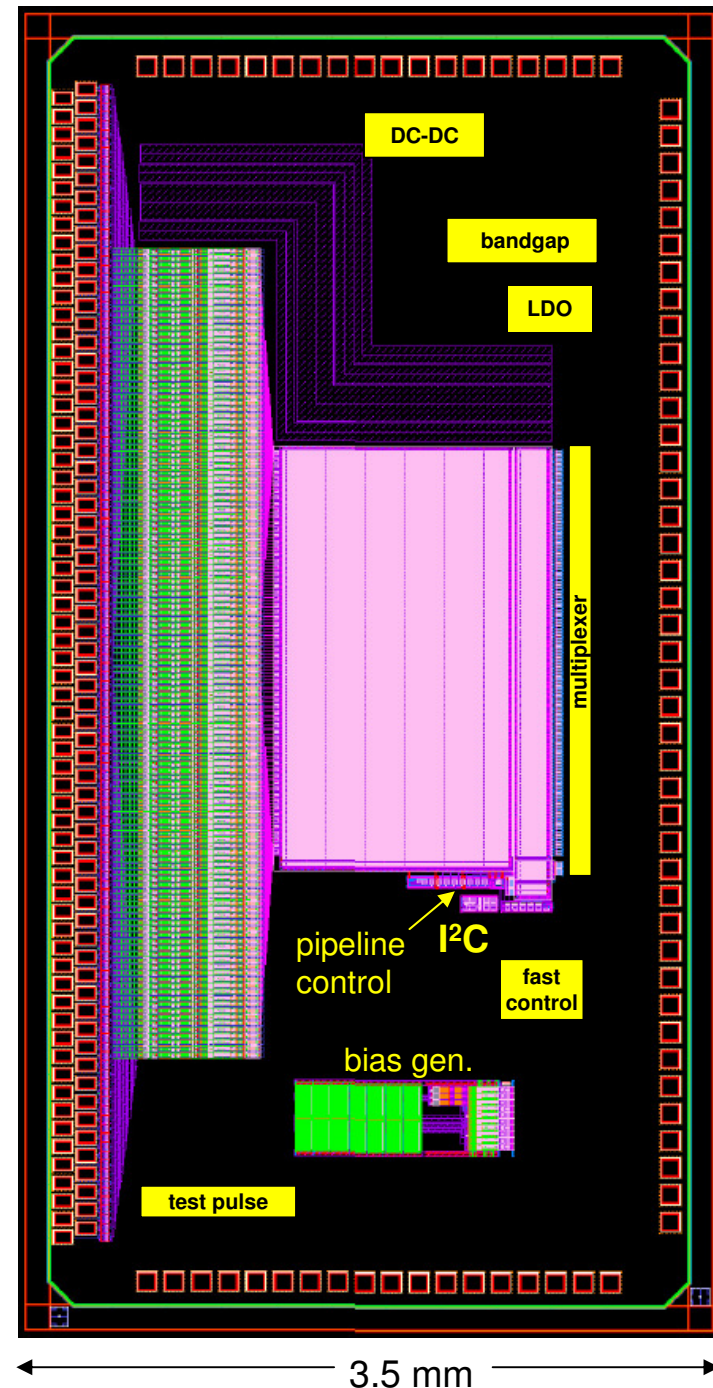

3.5 mm

sLHC strips readout system

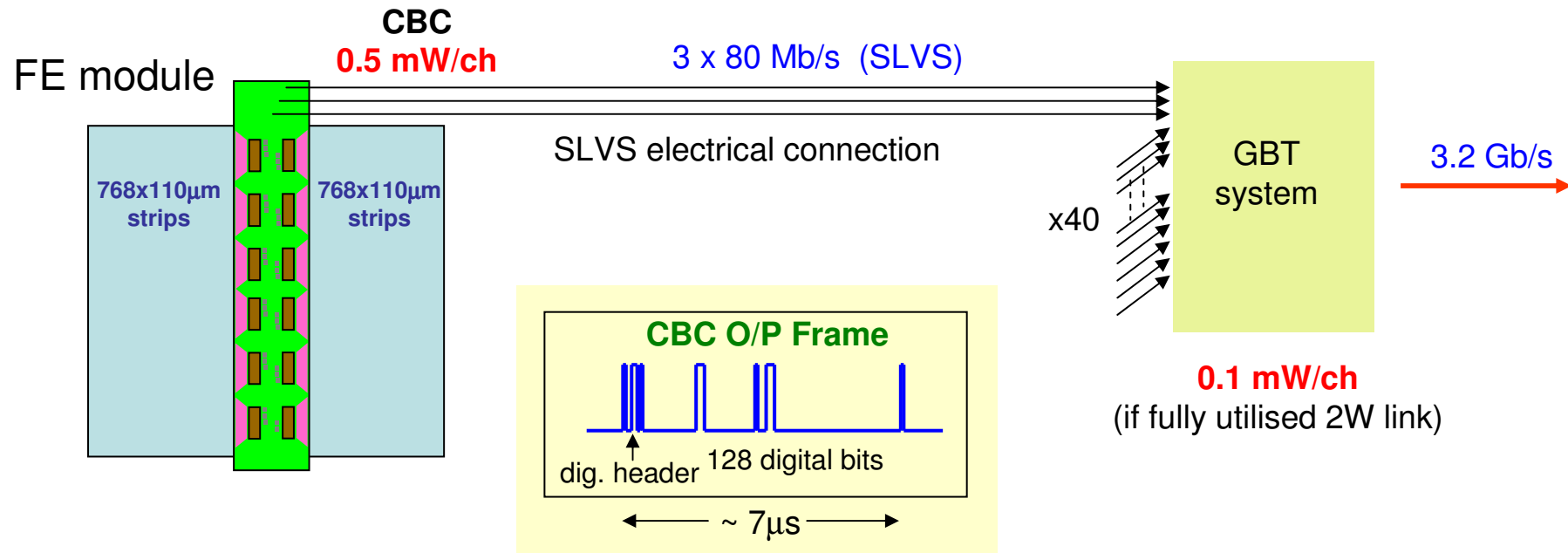

binary unparsified output frame format similar to APV (just hits, not analog values)

keep data frame $\sim 7 \mu\text{s}$ (must be less than average L1 separation)

=> 128 channel CBC provides output data at **20 Mbps**

=> 4 CBCs data combined onto one **80 Mbps** link to GBT input

plan to use GBT e-link (e-port IP block in chip)

takes care of data transfer synchronization

but not on this CBC version

modularity issues

40 x 80 Mbps lanes / GBT

integer number of GBTs preferred / module group (e.g. TOB rod)

=> no. of e-links needs to be close to $n \times 40$ for efficient GBT usage (\leq , not just over)

TOB rod example

rod length 120 cm, module dimensions $\sim 10 \times 8.5 \text{ cm}^2$


=> **12** modules / rod

for 5 cm strips, $\sim 110 \text{ um}$ pitch => **3** e-links / module

=> **36** e-links total => **1** GBT / rod

for 2.5 cm strips (2 hybrids / sensor)

=> **72** e-links => **2** GBT's / rod

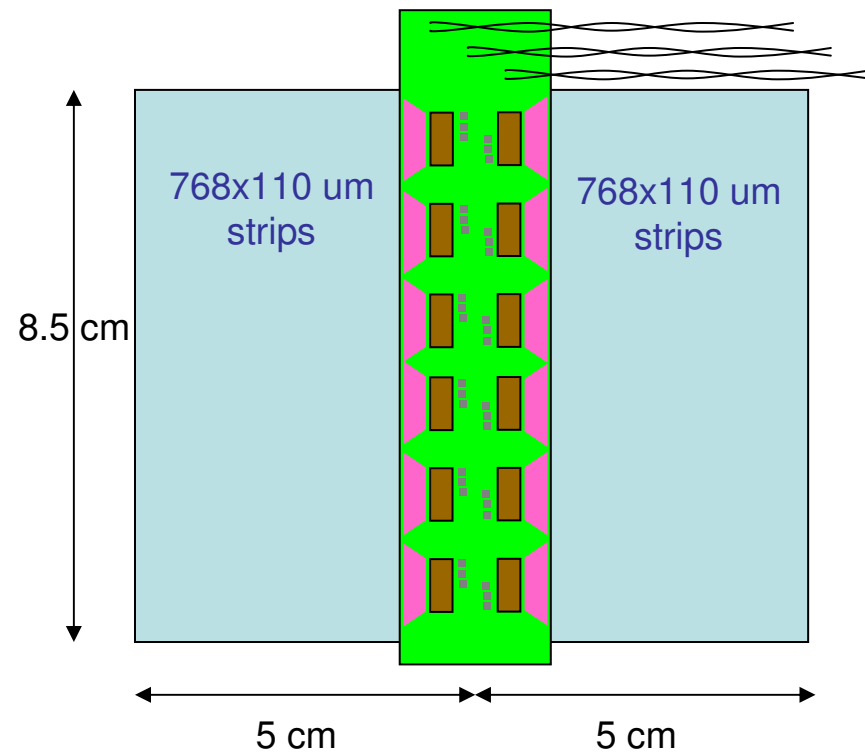

powering

would like to explore some options

switched capacitor DC-DC (CERN) ¹

converts 2.5 -> 1.25

might be needed if tracker I/P voltage (~12V)

cannot be converted to ~1.25 V in one stage

could use 1.25 to provide CBC digital rail

LDO (low drop-out) linear regulator

converts 1.25 -> 1.1

provides regulated rail to analog front end

provides some supply noise rejection ²

needs bandgap reference input (CERN)

can incorporate without risk - ensure can be over-ridden


e.g. don't use DC-DC

power digital separately (1.25 or less)

power LDO from separate 1.25

or don't use DC-DC or LDO

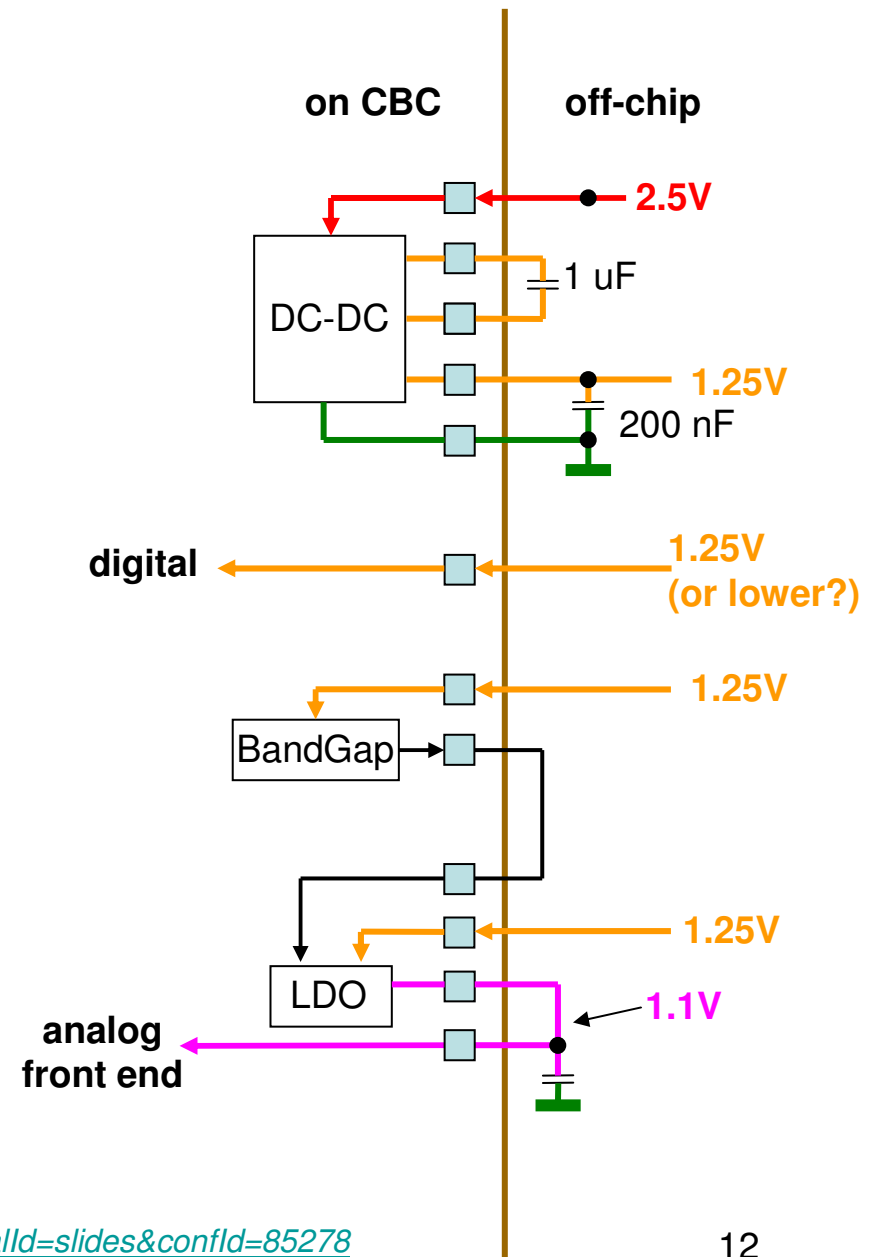power digital and analog independently
(or together)



¹ <http://indico.cern.ch/getFile.py/access?contribId=3&resId=0&materialId=slides&confId=85278>

² http://icva.hep.ph.ic.ac.uk/~dmray/CBC_documentation/LDO_PWG_Sep09.pdf

module concepts

hybrid, bonding, PA issues

CBC prototype will be “conventional” layout

128 channels, effective pitch 50 μm , wire-bondable
no special test setup preparations & generally easier to test

but 50 μm not well matched to sensor pitch $\sim 100 \mu\text{m}$

=> pitch adaption somewhere - where?

(would like to avoid separate PA's in future system)

hybrid? - possible but uses space for fanout

would help if CBC input pad pitch better matched to sensor $\sim 100 \mu\text{m}$ pitch




other issues

would module design benefit from 256 (2 x 128 channels back-to-back)?

(not impossible - but detailed study may yet reveal difficulties)

should we be looking at bump-bonding for chip/hybrid/sensor connection?

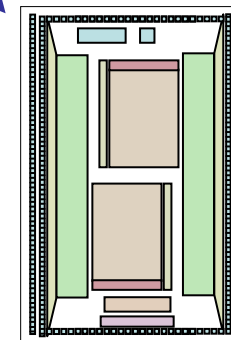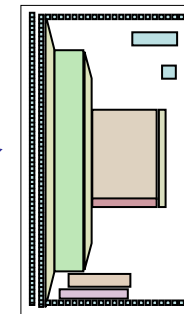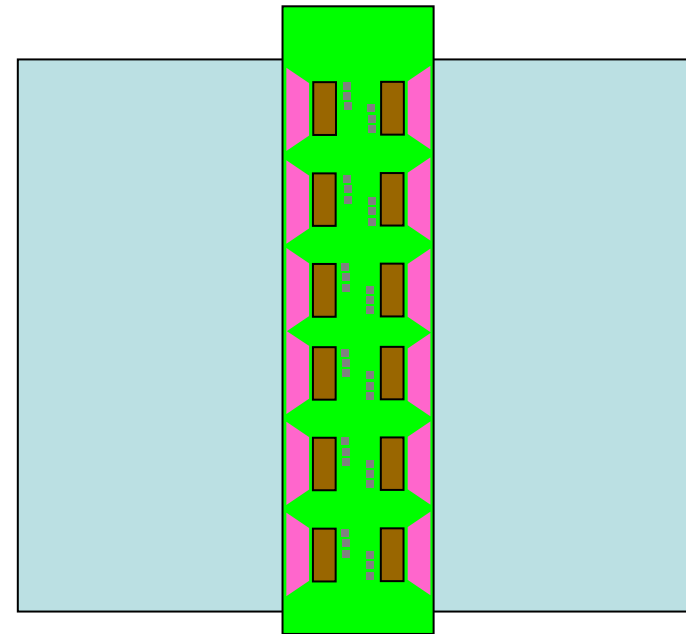=> a number of issues to re-examine for a subsequent iteration



summary

CBC development at advanced stage

- most of chip design complete

- front end meets all specs for simulated performance

 - 40 -> +40, all process corners, VDD = 1.1V

May submission – CERN 130nm MPW => plenty of chips

- expect back ~ September

system issues

- compatible with DC-DC powering schemes

 - some options to study (with/without switched cap. DC-DC and/or LDO)

- route to compatibility with GBT system seems clear

 - can incorporate e-link in future

will learn a lot from this prototype

- gain valuable experience with 130 nm

- lots of functionality and performance issues to study

 - noise, power, powering, radiation (SEE),....

- useful information for future chip and system developments

extra

test structures

lots of space available

test structures to include will be:

one complete dummy channel with buffered signals along chain (top edge of chip)

e.g. preamp, postamp and comp. O/P's


pads on bias generator outputs

allows to directly measure and/or over-ride

other test structures

e.g. individual components and arrays

....

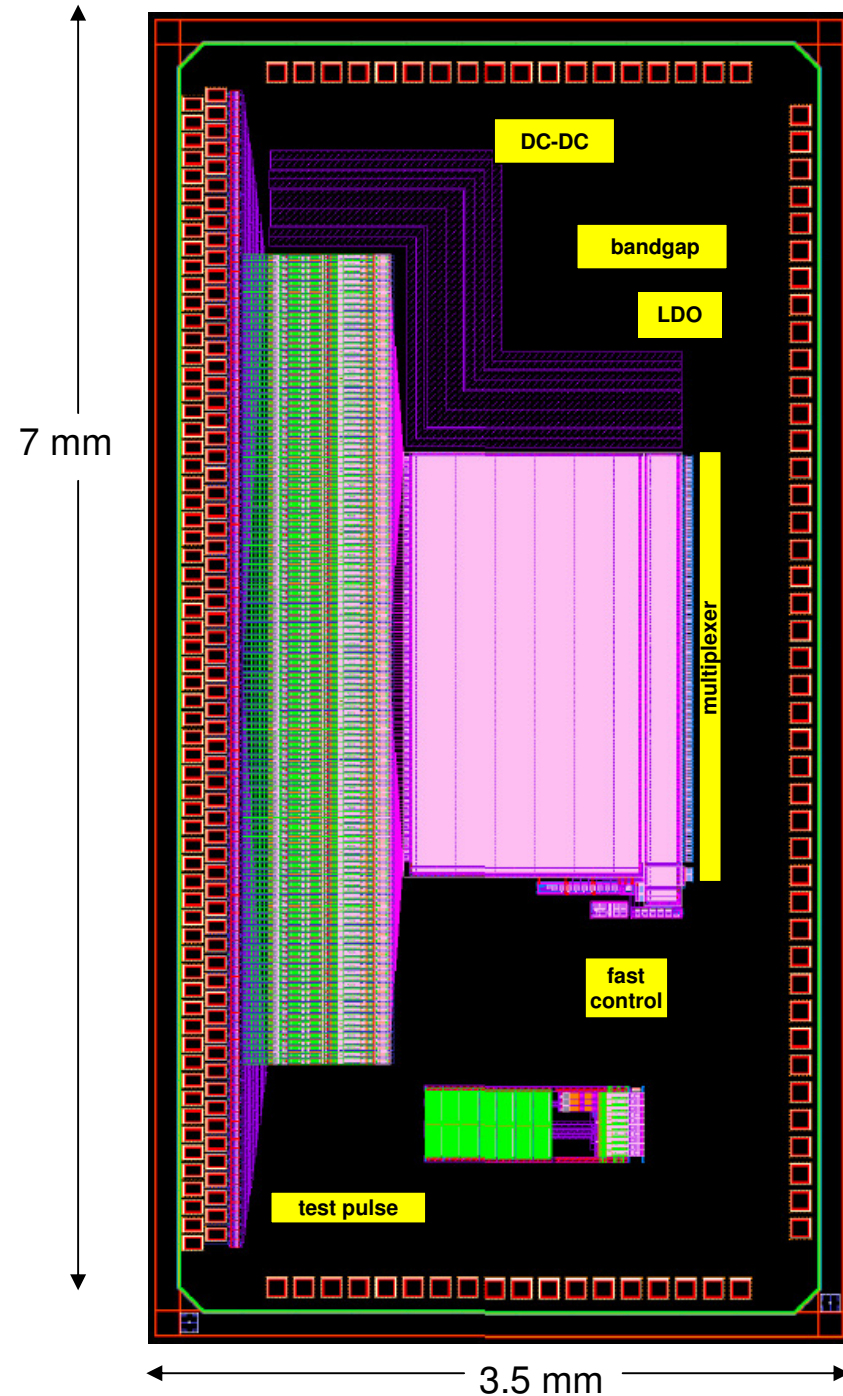

128 -> 256 back-to-back?

can share some functionality
e.g. power, control
but not much else

reduced area, cheaper

less pads available on 256 version

less flexible

overall power consumption
probably not much different

conclusions




256 back-to-back probably
not impossible

but detailed study may yet reveal difficulties


bump-bond option will increase height by factor ~ 2 , plus many other implications

-> significant changes to layout

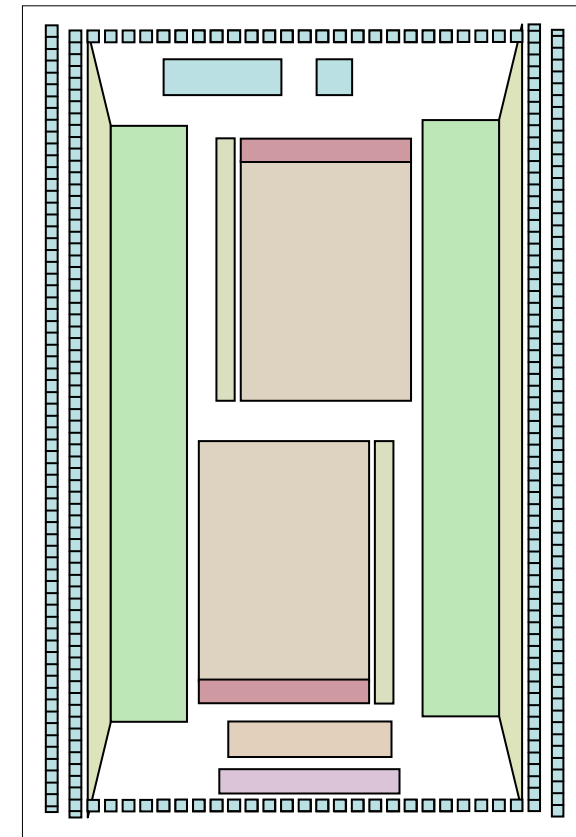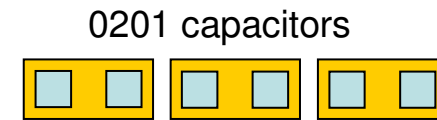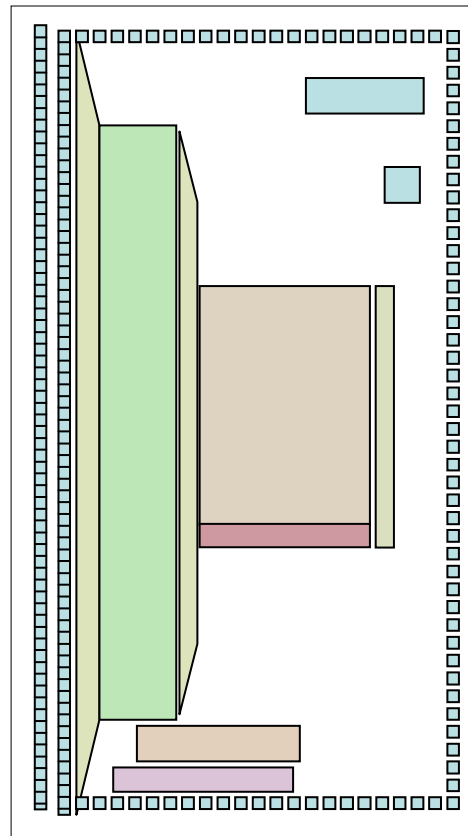128 is still the best prototype unit for now



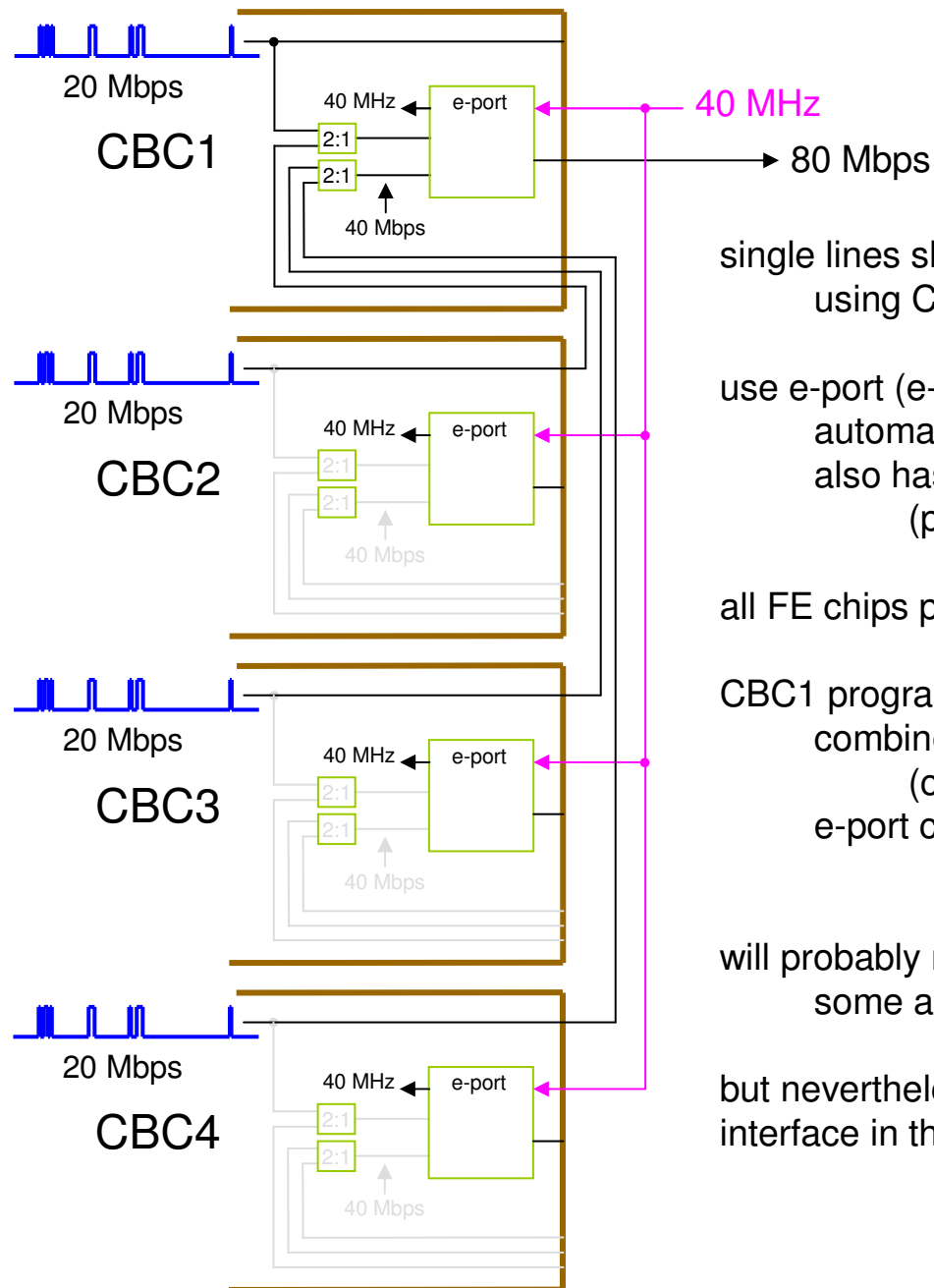combining chips output data using CERN e-port IP core



single lines shown outside chips but assume all differential SLVS using CERN SLVS interface driver/receiver

use e-port (e-link) to communicate with GBT (CERN IP core)
automatically takes care of synchronization
also has receive data path but we will probably not use
(plan to use I²C bus for slow control)

all FE chips produce 20 Mbps output data frame

CBC1 programmed to be master
combines pairs of CBC data streams into 2 x 40 Mbps
(compatible with e-port requirements)
e-port combines 40 Mbps streams to produce 80 Mbps

will probably not implement e-port in CBC May '10 submission
some aspects still under development

but nevertheless a clear route to provide the CBC->GBT system interface in the future


alternative scheme

put e-port in separate GBT interface chip

incorporates circuitry to combine CBC data streams

another chip on hybrid but could offer some future flexibility

an option to consider in the future

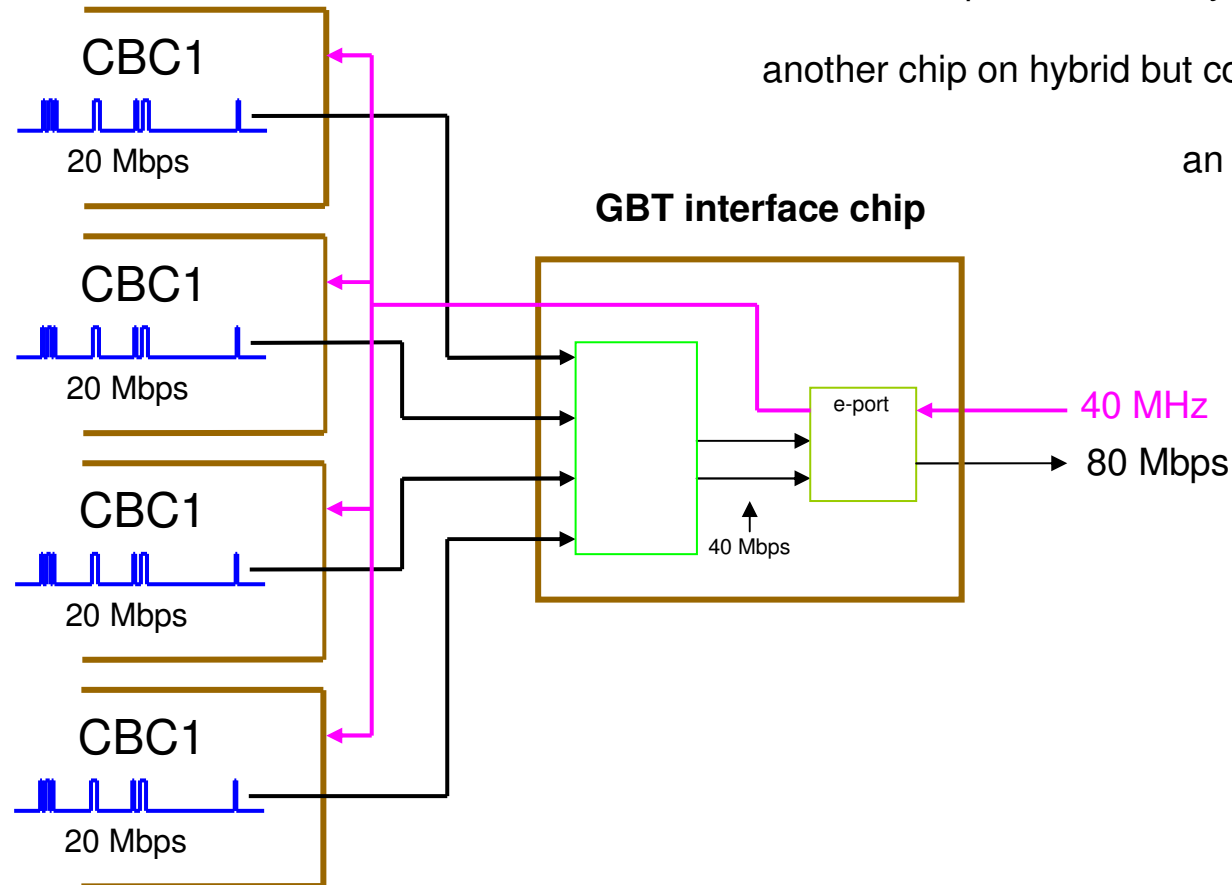

CBC power

preamp/postamp

20 nsec peaking time, short strips $C_{\text{SENSOR}} \sim 5\text{pF}$
($\sim 100 + (20 \times C_{\text{SENSOR}})$)

comparator

digital

take 0.25 μm APV25 (digital 400 μW)
/10 for technology, x3 for SEU
(pessimistic? CBC logic should be simpler)

output

LV differential \sim few mW / 128 chans.

contingency

just guess nominal figure to bring overall power to 0.5 mW

power/FE chan.

200 μW

14 μW

$\sim 200 \mu\text{W}$
analogue

120 μW

30 μW

$\sim 300 \mu\text{W}$
digital

150 μW

0.5 mW / channel seems like an achievable target (c.f. 2.7 mW for APV25)

digital is biggest uncertainty, and maybe largest contributor

hope to improve estimate as design progresses


can consider running at lower voltage (dig. power $\sim V^2$) \Rightarrow extra contingency

e.g. 1.2 \rightarrow 0.85 power consumption halved

will keep power rails separate on chip to keep option open

using numbers above: 128 chan. chip needs ~ 20 mA analogue, ~ 30 mA digital

front end PSR **without** LDO supply

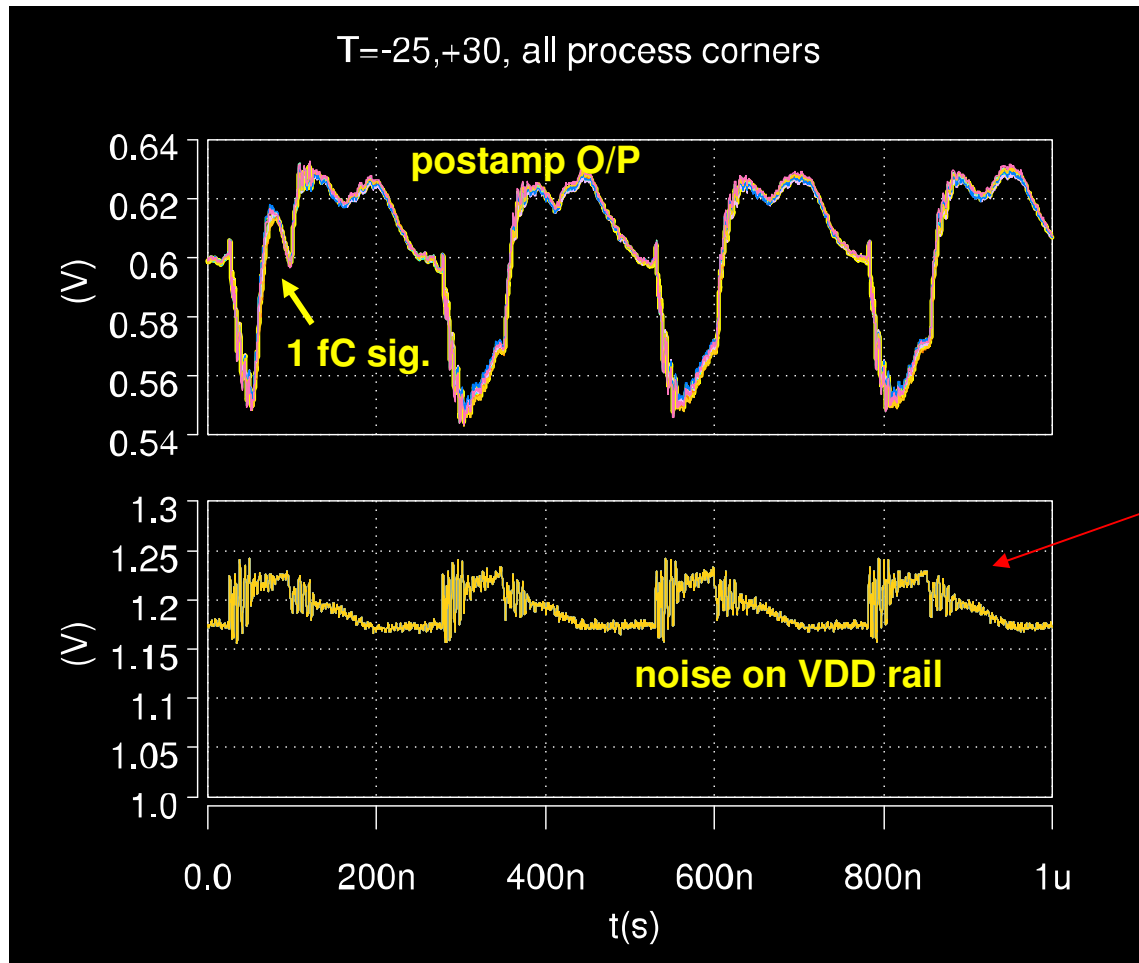

time domain picture

measured noise waveform added to VDD rail supplying FE circuit

sampled scope data for Enpirion "quiet" converter provided by Aachen


but x10 to (artificially) make it noisier

~ 80 mV pk-pk

1 fC normal signal completely swamped by noise

Ref: <http://indico.cern.ch/getFile.py/access?contribId=24&sessionId=0&resId=0&materialId=slides&confId=47293>

front end PSR **with** LDO supply

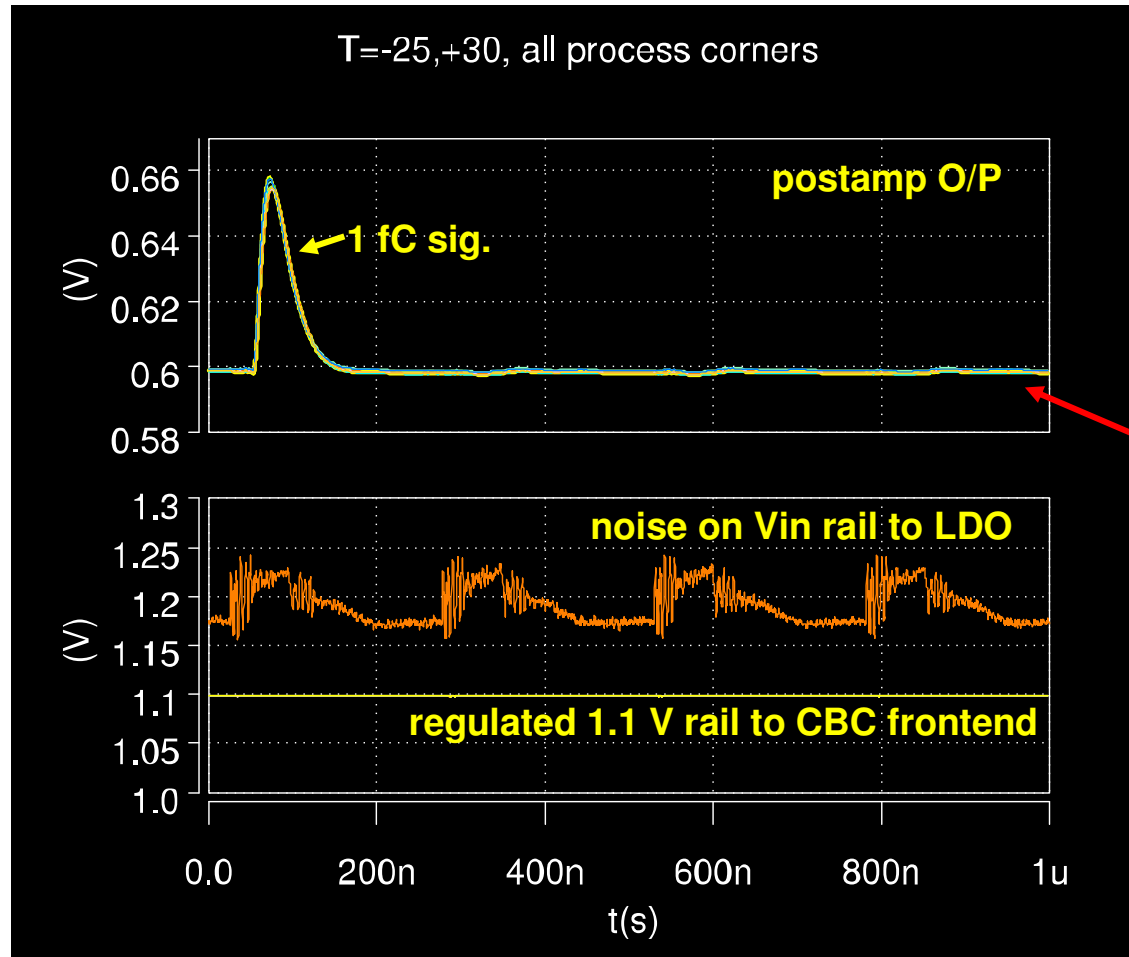

measured **x10** (80 mV pk-pk) noise waveform now added to LDO V_{in}

LDO loaded by single CBC frontend + 25 mA extra dummy load

1 fC signal at postamp O/P now appears

postamp O/P noise just visible

~ 125e pk-pk

matching CBC modules to GBT links

Duccio's FNAL workshop
talk – October '09

Tag	OB_L1	OB_L2	OB_L3	OB_L4	EC_R1	EC_R2	EC_R3	EC_R4	EC_R5	EC_R6	EC_R7
Type	rphi	rphi	rphi	rphi	rphi	rphi	rphi	rphi	rphi	rphi	rphi
Area (mm ²)	8475.8	8475.8	8475.8	8475.8	8475.8	8475.8	8475.8	8475.8	8475.8	8475.8	8475.8
Occup (max/av)	2.7/2.6	3.2/3.0	1.9/1.8	0.8/0.8	3.9/3.5	2.8/2.5	2.2/2.0	3.3/3.0	2.6/2.4	2.0/1.8	1.7/1.5
Pitch (min/max)	110	110	110	110	110	110	110	110	110	110	110
Segments x Chips	4x6	2x6	2x6	2x6	4x6	4x6	4x6	2x6	2x6	2x6	2x6
Strip length	24.9	49.8	49.8	49.8	24.9	24.9	24.9	49.8	49.8	49.8	49.8
Chan/Sensor	3072	1536	1536	1536	3072	3072	3072	1536	1536	1536	1536
N. mod	960	1248	1536	2016	400	480	560	600	680	760	800
Channels (M)	2.95	1.92	2.36	3.1	1.23	1.47	1.72	0.92	1.04	1.17	1.23
Power (kW)	1.5	1	1.2	1.5	0.6	0.7	0.9	0.5	0.5	0.6	0.6
N of GBTs	160	104	128	168	80	80	120	60	60	80	80
GBT power (kW)	0.3	0.2	0.3	0.3	0.2	0.2	0.2	0.1	0.1	0.2	0.2

~ radius [cm]	50	65	85	110
circumference [cm]	314	408	534	692
rods per ½ barrel	40	52	64	84
128 channel chips/module	24	12	12	12
chips / rod	288	144	144	144
80 Mbps lanes / rod	72	36	36	36
(40 lane)GBTs / rod	2	1	1	1

module dimensions 10 x 8.5 cm² (z x rphi)

½ barrel 120 cm long

=> 12 modules / ½ barrel rod

GBT lanes not fully utilised, but integer no. of GBT's per rod is presumably optimal

unsparsified binary advantages

data volume known - no trigger-to-trigger variations – occupancy independent

=> simpler readout system on-detector

FE chips -> GBT -> link

no extra data buffering and concentrating chips in the system

=> simpler system off-detector too I think

known and unchanging origin and volume of data – must simplify processing

synchronous system - all FE chips doing same thing at same time – easy to emulate externally

no need to timestamp on front end

easy to spot upset chips (pipe address wrong)

likely to be lowest power FE chip architecture

analog FE + comparator followed by simple digital pipeline and off-chip mux

no ADC, no analog pipeline readout

easier to scale designs to even finer feature processes

(analog pipelines using gate capacitance probably only just possible in 0.13)

easy to keep dynamic power variations small or negligible

simpler FE module design (less chips)

unsparsified binary disadvantages

no pulse height information

binary worse for position resolution

common mode immunity – (short strips will help – less pickup)

larger data volume => more off-detector links

data volumes

unsparsified data volume / 128 channel chip = 128 bits + header (say 12) = 140 bits

sparsified data volume / hit

- 8 bit chip address

- 7 bit channel address (x no. of channels above threshold)

- 8 bit timestamp

occupancy 0.8%, 1 hit, data volume = 23 bits

occupancy 4%, 5 hits, data volume = 51 bits

so factor ~ 3 – 6 (depending on occupancy) inefficient assuming 100% link bandwidth utilised

factor ~ 1.5 – 3 inefficient assuming 50% link bandwidth utilised


(do we need to provide for heavy ion running in CMS at SLHC?)

layout pictures

Preamp

35 μm


110 μm

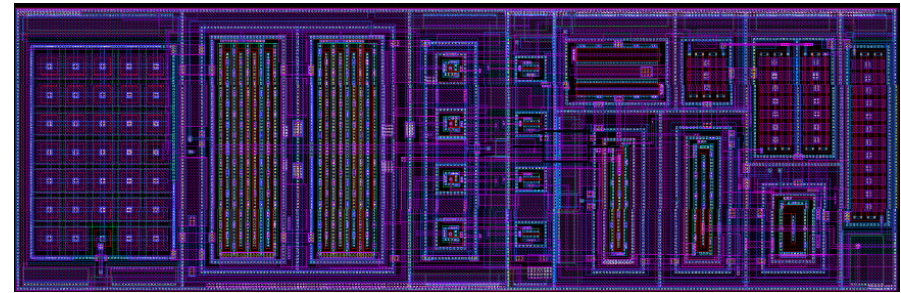

Postamp

230 μm


35 μm

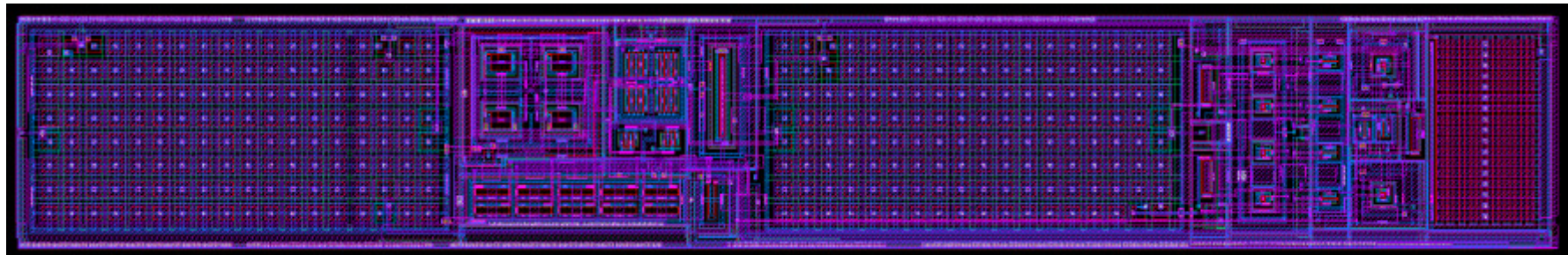

160 μm

**Postamp
output offset
adjust**


35 μm

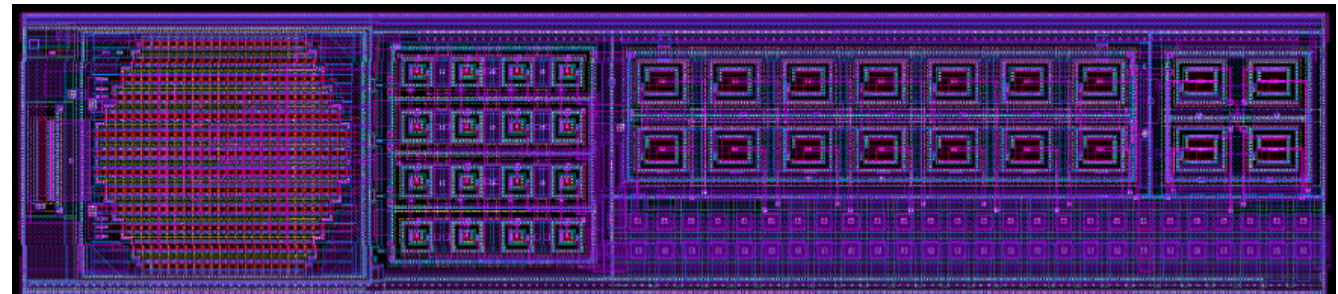

155 μm



**Comparator and
offset adjust
register**

35 μm

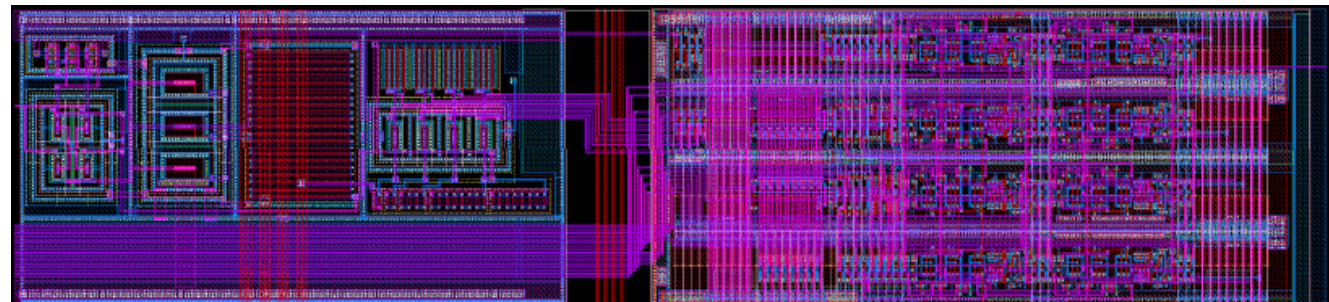

some other bits

I2C

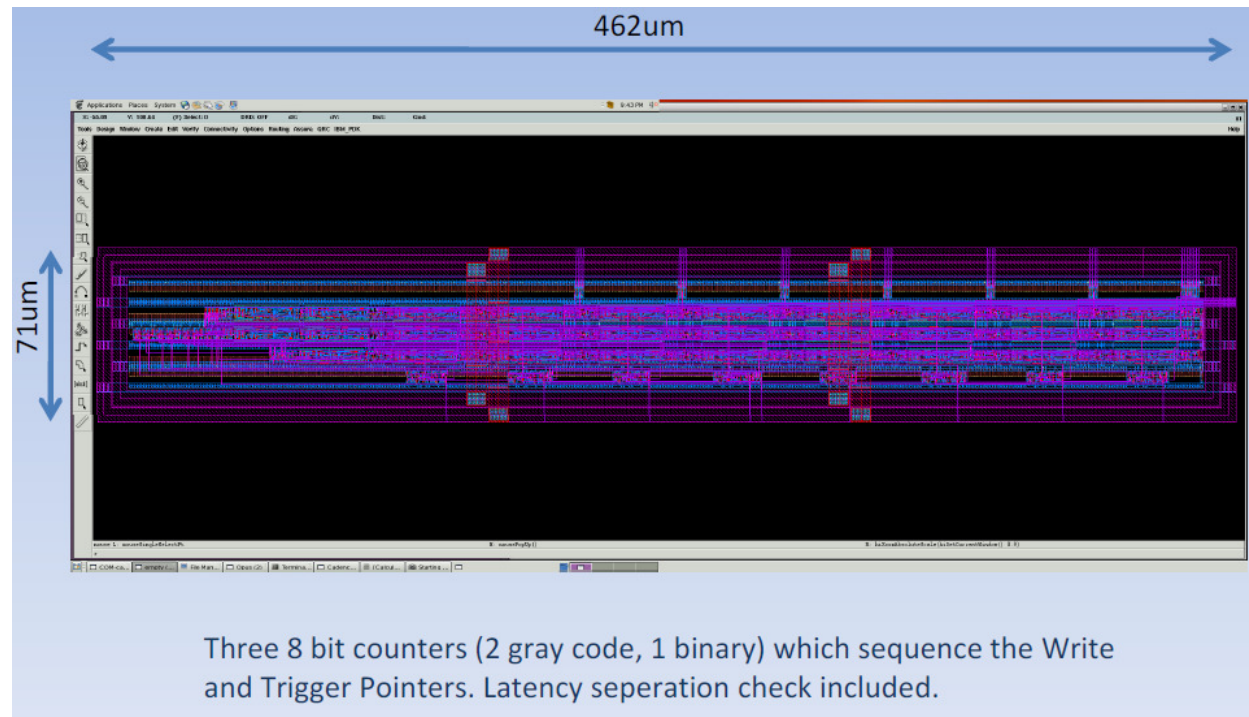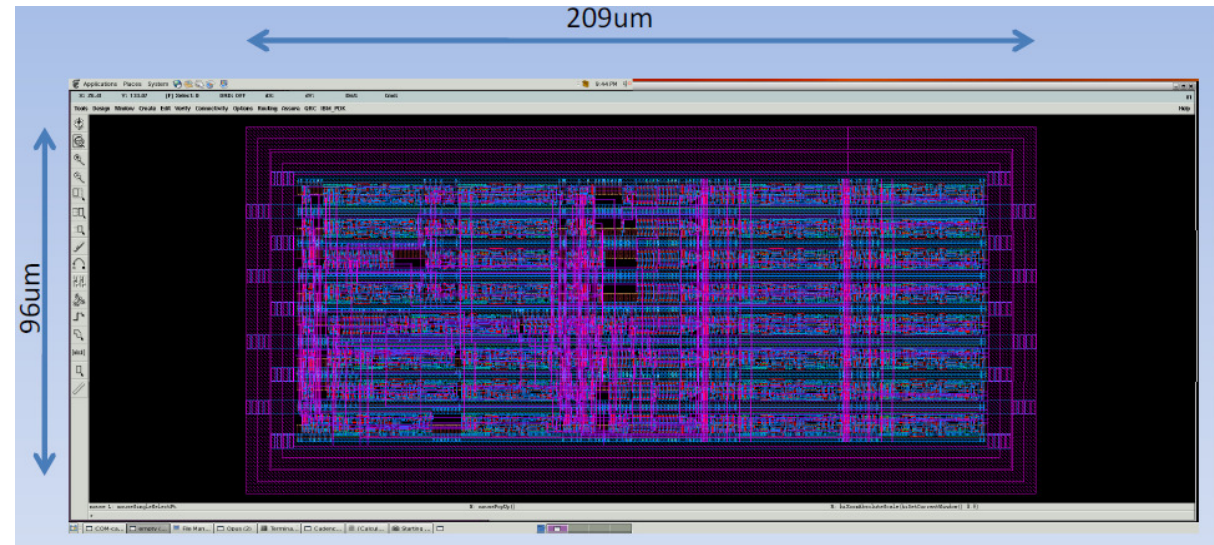

Pipeline control logic