

CBC3 progress (2)

front end progress
HIPs deadtime calculations
powering and voltage reference thoughts

systems meeting, 23rd September, 2015.

CBC3 design progress - previous presentations

preamplifier changes

http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3%20Progress_Apr_15%20.pdf

increased input FET bias current range, reg. cascode, 100k feedback resistor, electrons only

postamp changes

http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3_FE_status_June2015.pdf

electrons only, new feedback bias circuit

digital blocks

http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3_systems_July2015.pdf

progress through to layout & post layout simulations of:

- hit detect


- stub gathering logic

- data packet assembly & transmission

- output (PISO) shift register, L1 counter


- fast control interface

for reference

 


CBC3 comparator progress

CBC2 comparator

 


1 per chip

 


problem: when comparator switches overall current changes

not so good when lots of channels
switching at same time





CBC³ comparator

 

1 per chip

 

 
 
 
 
transient analysis: $T=0$, process=tt, $VDD=1.1$, $ICOMP=6u$



O/P stage modification solves the current switch problem
response shown here **without** the RC filter - some sharp
current spikes

— CBC2 circuit
— CBC3 circuit

    transient analysis: $T=0$, process=tt, $VDD=1.1$, $ICOMP=6u$




O/P stage modification solves the current switch problem
response shown here **with** the RC filter - sharp spikes
filtered out


— CBC2 circuit
— CBC3 circuit

front end design changes complete

CBC3

 


CBC2

 

new preamp cascode bias scheme will eliminate "shadow effect"

new postamp feedback scheme, as well as current neutral comparator will address CM effects observed when many channels fire

holes polarity response

 

(for info only - chip not designed for holes polarity)


HIPs effect calculations

details of electronics HIPs response shown last time


http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3_systems_July2015.pdf

will today show calculation of hit loss

 **probability/incident pion of depositing energy E
in $300\mu\text{m}$ Si layer**




 **postamp output response to 4pC
charge injected on centre channel**



HIPs energy spectrum - M.Huhtinen simulations

 
Probability/incident pion of depositing energy E in $300\mu\text{m}$ Si layer




use this distribution to be conservative
but should be lower for thinner sensor

HIPs energy spectrum - M.Huhtinen simulations

 Probability/incident pion of depositing energy E in 300 μ m Si layer



 
for calculations here, take numbers directly from graph





parameterizing hips deadtime

deadtime quantified (in simulation) by duration of saturation time

 
saturation taken to be signal over $\sim 1fC$ threshold



hit loss rate predictions - method

  
 
$$\times \frac{0.01}{25\text{ns}} = \times 10^{-6}$$



fraction of time channel is dead (in BX's)
= prob. of particle interacting x occupancy
x deadtime (in BX's) ← use 1%

sum bins to get
total hit loss probability

	Σbins	multiplier	result
centre	1.37e-4	x1	2.74e-4
NN	4.27e-4	x2	8.54e-4
NN+1	8.51e-5	x2	1.70e-4
NN+2	4.05e-6	x2	8.1e-6
NN+3	5.4e-9	x2	1.1e-8

1.31x10⁻³ is probability of losing a single hit on a track
because it has passed through a channel temporarily
disabled due to a previously occurring HIPs event
(in itself or neighbouring channels)

(remember that this is per % occupancy)

1.31e-3

current thinking on LDO and powering

previous thoughts:

http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3_powering_June2015.pdf
http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3_systems_July2015.pdf

discussed last time possibility to use PMOS based bandgap (Jan Kaplon)

more stable to radiation (ionizing and displacement)

but stronger process dependence
=> need mechanism to trim

possibility to use e-fuses to do this

also e-fuses can be used to provide unique chip identifier at wafer probe time

current thinking on LDO and powering

take Vref from PMOS bandgap

trim using I2C register (somehow)

use e-fuses to fix default value of I2C register during wafer test

(note: default I2C value could be overwritten later if so desired)


for example

set LDO gain to 2


choose (trim) Vref to be 0.5

=> VDDA = 1.0 V

 
VDDD > 1.1 V allows 100mV headroom for LDO



CBC2 LDO measurements

 

 analogue current consumption
 ~ 300uA / chan. for 5 cm strips
 => ~80 mA / chip
 => ~40 mV dropout => plenty of headroom




analogue current consumption
 ~ 700uA / chan. for 8 cm strips
 => ~180 mA / chip
 => ~80 mV dropout => just enough headroom

=> no need to change core LDO design (only feedback resistor tweaks)

BACKUP

multi-channel behaviour

 


simulations here for $C_{is} = 2.5\text{pF}$, $C_{bp} = 2\text{pF}$, $C_{stray} = 2\text{pF}$
 $\Rightarrow C_{tot} = 9\text{ pF}$

inject charge into central channel



look at postamp output for
central channel
nearest neighbour,
nearest neighbour +1
....

CBC3 front end progress

 details of changes to preamp/postamp circuits and performance shown last time*




  no time to present multi-channel and hips response simulations last time



* http://www.hep.ph.ic.ac.uk/~dmray/systems_talks/2015/CBC3_FE_status_June2015.pdf

interstrip crosstalk

 

2.5 fC charge injected

T=-20/+30






all corners

nominal biases





nearest neighbour peak

crosstalk ~ 5 %

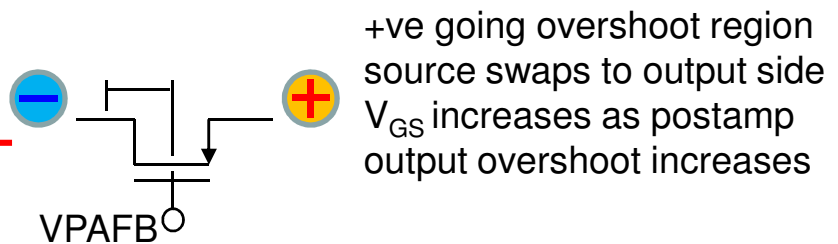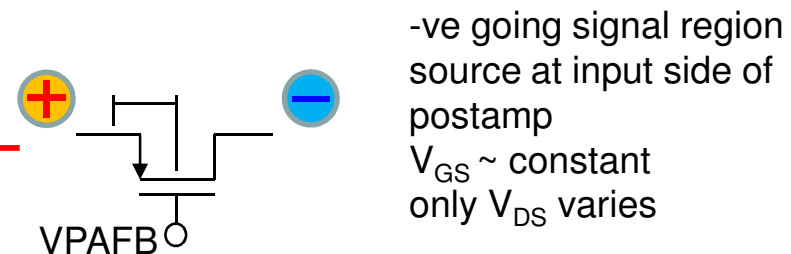  
 
postamp feedback characteristics reminder



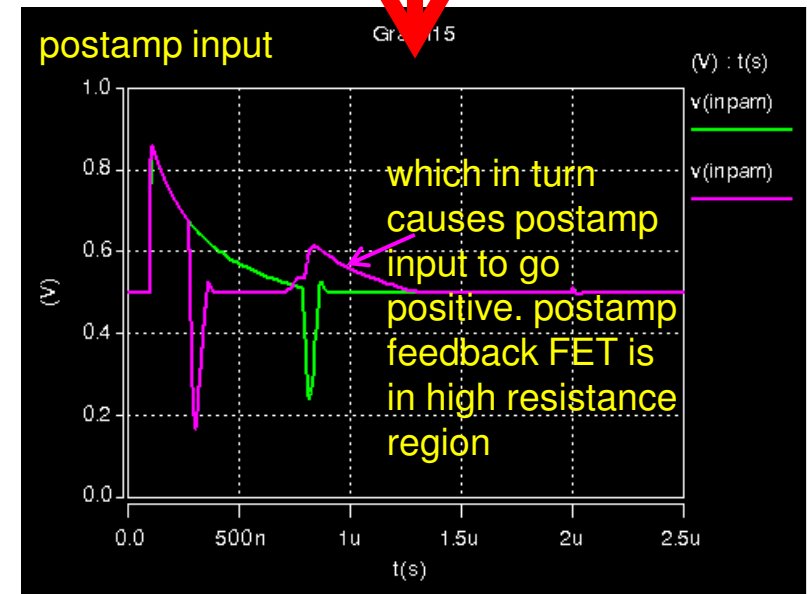   
why is nearest neighbour hips deadtime worse than centre chan?




CBC3 Preamp with regulated cascode

  

CBC3 Postamp

 

postamp bias (1 per chip)

 

CBC3 postamp feedback

